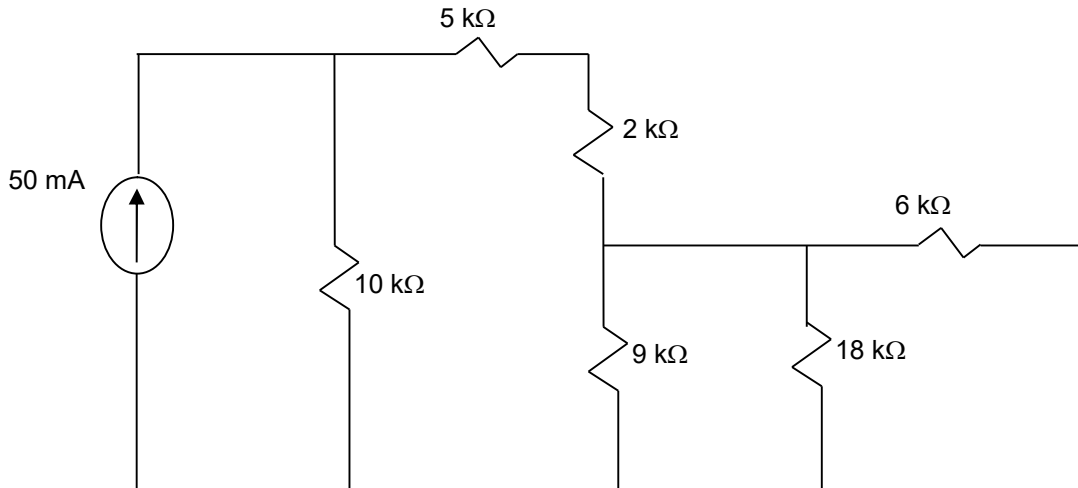


Fundamentals of Electrical Circuits - Chapter 3


- 1S. For the circuits shown below,
 a) identify the resistors connected in parallel
 b) Simplify the circuit by replacing parallel connect resistors with equivalent resistor.



Solution:


- a) Resistors in Parallel
 $9\text{ k}\Omega \parallel 18\text{ k}\Omega \parallel 6\text{ k}\Omega$

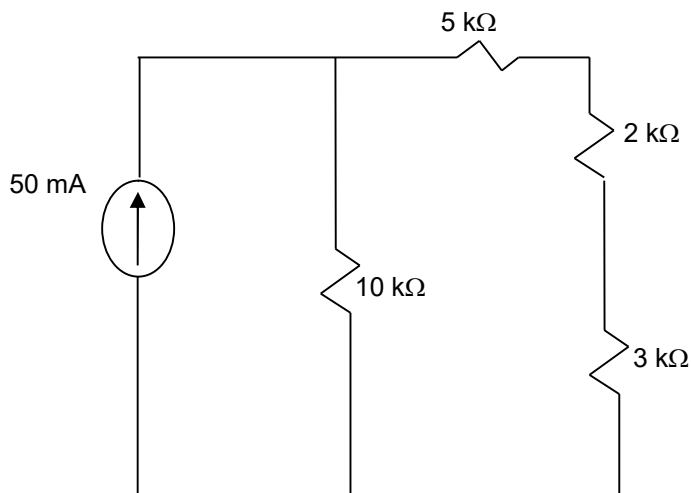- b) Simplify
 $\text{Req for parallel Resistors} = 1/(1/9 + 1/18 + 1/6) = 3$




- 1U. For the circuits shown below,
 a) identify the resistors connected in parallel

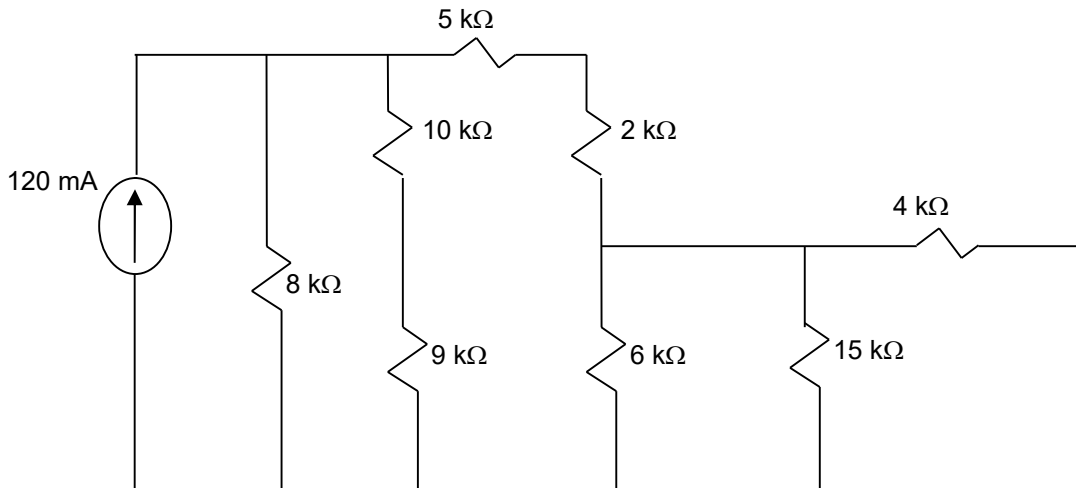b) Simplify the circuit by replacing all resistors with equivalent resistor.



Solution:

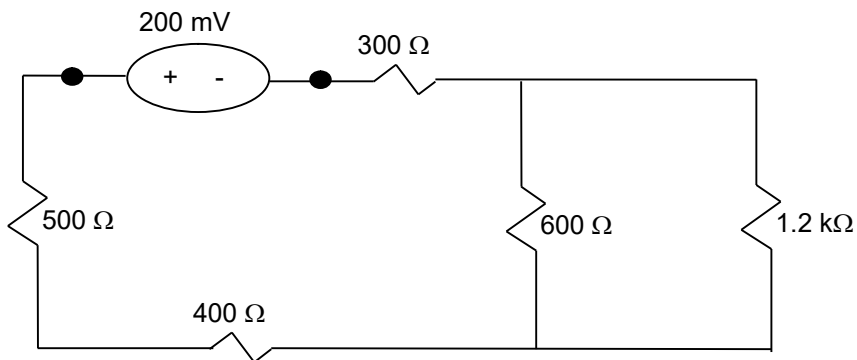
2S. Find the equivalent resistance seen by the source in the following circuit.




Solution:

Simplify?
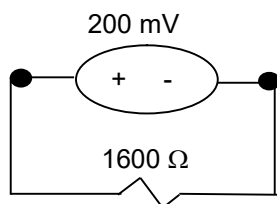
$$R_{eq} = (1200 \parallel 600) + 300 + 400 + 500 = 1 / (1/1200 + 1/600) + 1200 = 1600 \Omega$$




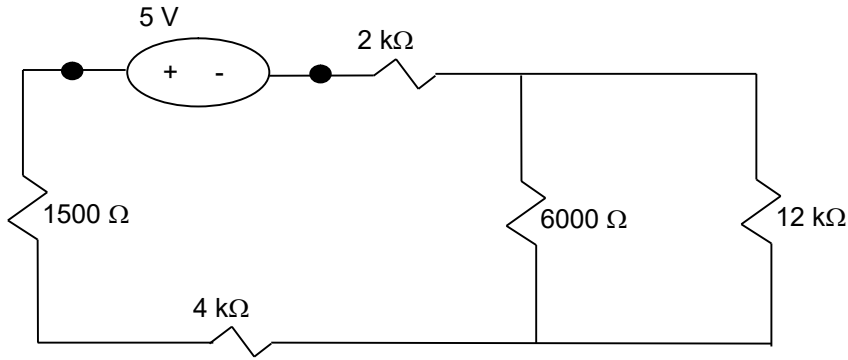2Ua. Find the equivalent resistance seen by the source in the following circuit.



Solution:

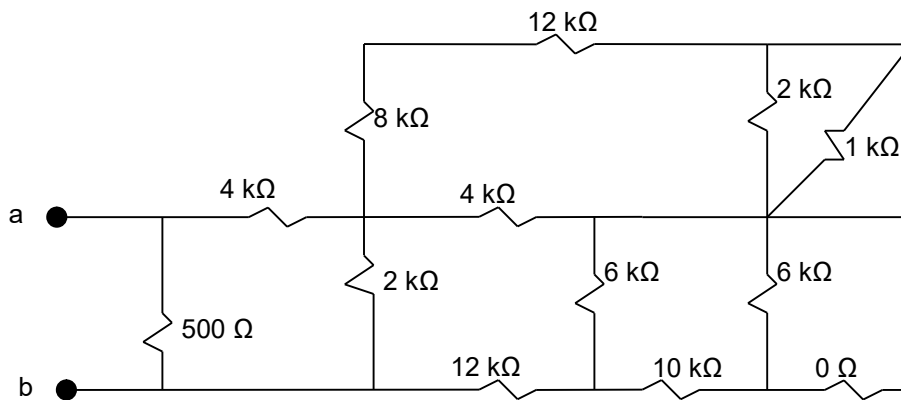
2Ub. Find the equivalent resistance (R_{ab}) in the following circuit with respect to terminals ab.



Solution:

3S. For the following circuit,

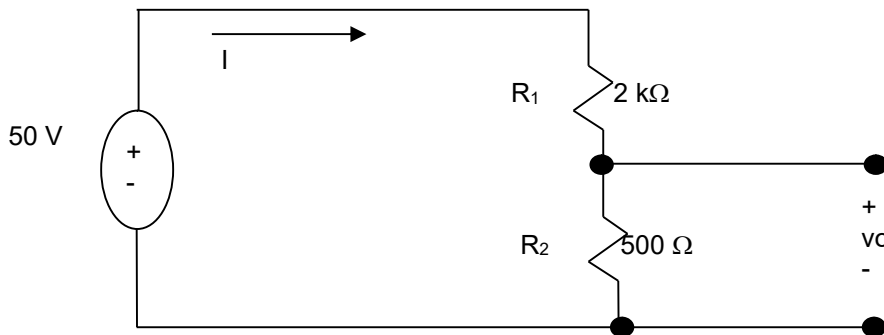- Calculate the no-load voltage v_o in the voltage-divider.
- Calculate the power dissipated in R_1 and R_2 .
- Assuming that only $1/4$ W resistors are available. The no-load voltage is to be the same as in (a). Specify the smallest value of R_1 and R_2 .



Solution:

- find no-load v_o ?
 $v_o = I R_2$

$$v_o = (50 / (R_1 + R_2)) * R_2 = (50 / (2000 + 500)) * 500 = 10 \text{ V}$$

b) Powers?

$$P_{R1} = R_1 * (50 / (R_1 + R_2))^2 = 2000 * (50 / 2500)^2 = 0.8 \text{ W}$$

$$P_{R2} = R_2 * (50 / (R_1 + R_2))^2 = 500 * (50 / 2500)^2 = 0.2 \text{ W}$$

c) Given: $P_{Max} \leq \frac{1}{4} \text{ W}$ & $v_o = 10 \text{ V}$; Find possible value of R_1 & R_2

$$v_o = 10 \text{ V} \rightarrow v_o = (50 / (R_1 + R_2)) * R_2 = 10 \rightarrow R_1 / R_2 = 4$$

$$P_{Max} \leq \frac{1}{4} \text{ W} \rightarrow v_o^2 / R_2 \leq \frac{1}{4} \text{ W} \rightarrow 10^2 / R_2 \leq \frac{1}{4} \text{ W} \rightarrow R_2 \geq 400 \Omega$$

$$P_{Max} \leq \frac{1}{4} \text{ W} \rightarrow v_o^2 / R_1 \leq \frac{1}{4} \text{ W} \rightarrow 40^2 / R_1 \leq \frac{1}{4} \text{ W} \rightarrow R_1 \geq 6400 \Omega$$

The values of R_1 & R_2 must satisfy 3 rules: $R_1 \geq 6400 \Omega$, $R_2 \geq 400 \Omega$ & $R_1 / R_2 = 4$


There fore the Minimum value $\rightarrow R_1 = 6400 \Omega \rightarrow R_2 = R_1 / 4 = 1600 \Omega$,

3U. For the following circuit,

a) Calculate the no-load voltage v_o for the voltage-divider.

b) Calculate the power dissipated in R_1 and R_2 .

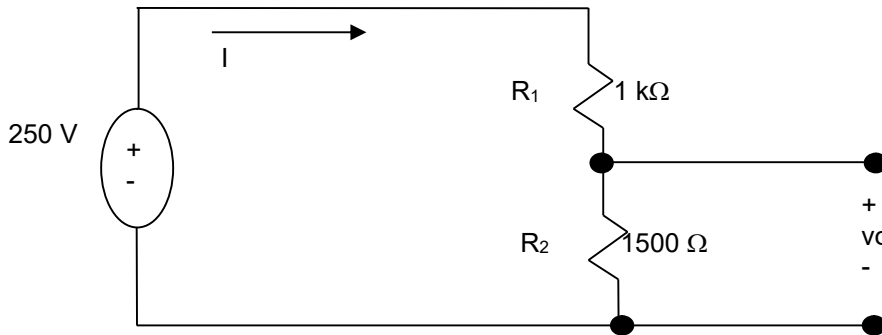c) Assuming that only 0.25 W resistor are available. The no-load voltage (V_o) is to be the same as in part (a). Specify the value of R_1 and R_2 that meets the limitations.



Solution: Not Provided


4S. Use voltage division or current division to find the specified voltages or currents:

a) Suppose the voltage drop across the 24Ω resistor in the following circuit A is 40 V , positive at the top of the resistor. What is the voltage drop across the 18Ω resistor?


b) Suppose the current in the 10Ω resistor in the following circuit A is 60 mA , flowing from left to right. What is the current flowing in the 30Ω resistor?

c) Suppose the current in the $1.2 \text{ k}\Omega$ resistor in the following circuit B is 9 mA , flowing from left to right. What is the current in the $30 \text{ k}\Omega$ resistor?

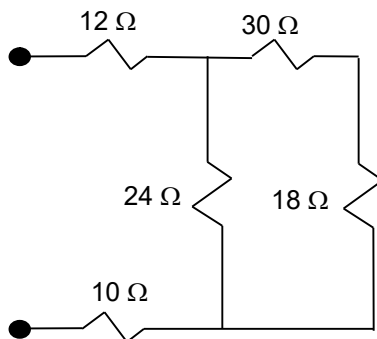d) Suppose the voltage drop across the $4 \text{ k}\Omega$ resistor in the following circuit B is 50 V , Positive at top of the resistor. What is the voltage drop across the $2.4 \text{ k}\Omega$ resistor?




(A)

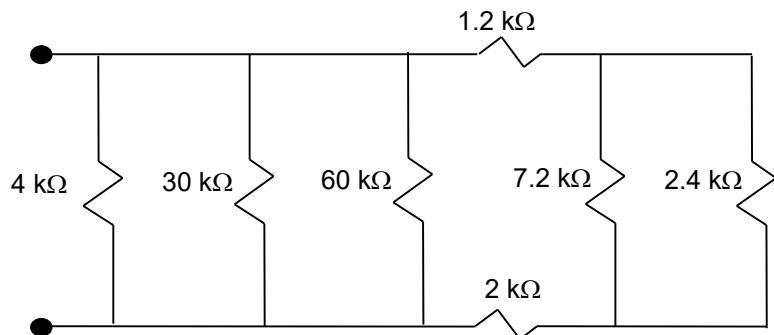

(B)


Solution:

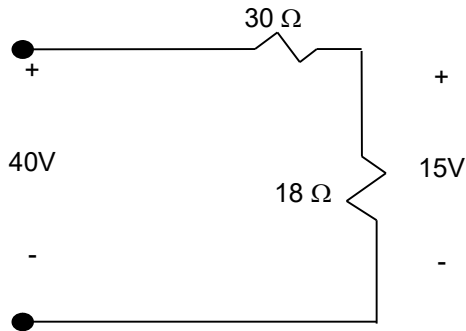a) Given $V_{24\Omega} = 40V$, Find $V_{18\Omega}$



$$V_{18\Omega} = IR = (40 / (30 + 18)) * 18 = 15 V$$

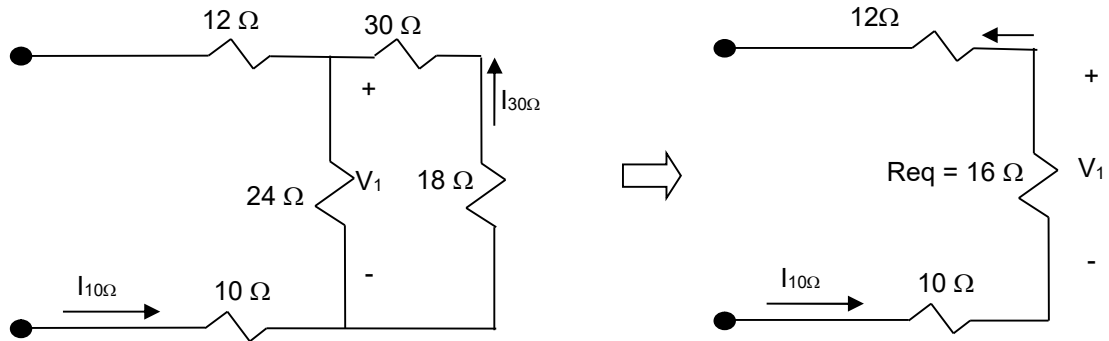
b) Given $I_{10\Omega} = 60 \text{ mA}$, Find $I_{30\Omega} = ?$



$$R_{eq} = 24 \parallel (18 + 30) = 16 \Omega \rightarrow V_1 = 16 * 60 = 960 \text{ mV}$$

$$I_{30\Omega} = V_1 / (30 + 18) = 960 / 48 = 20 \text{ mA}$$

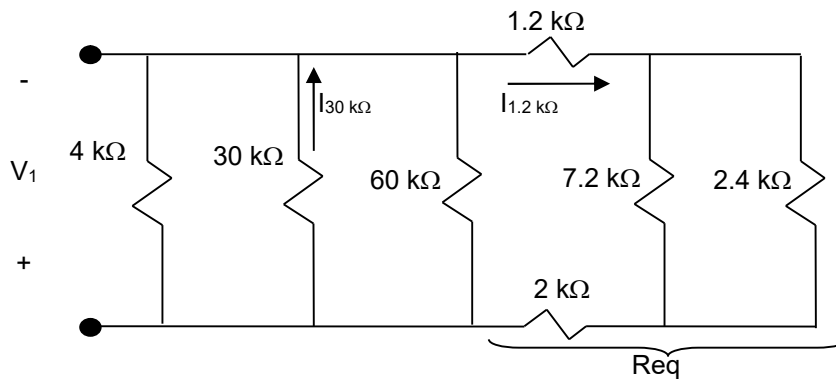c) Given $I_{1.2 \text{ k}\Omega} = 9 \text{ mA}$, Find $I_{30\Omega} = ?$




Current Divider

$$R_{eq} = (1.2 + 7.2 \parallel 2.4 + 2) = 5 \text{ k}\Omega$$

$$V_1 = (9 \text{ mA})(5 \text{ k}\Omega) = 45 \text{ V}$$

$$I_{30\Omega} = V_1 / 30 = 45/30 = 1.5 \text{ mA}$$

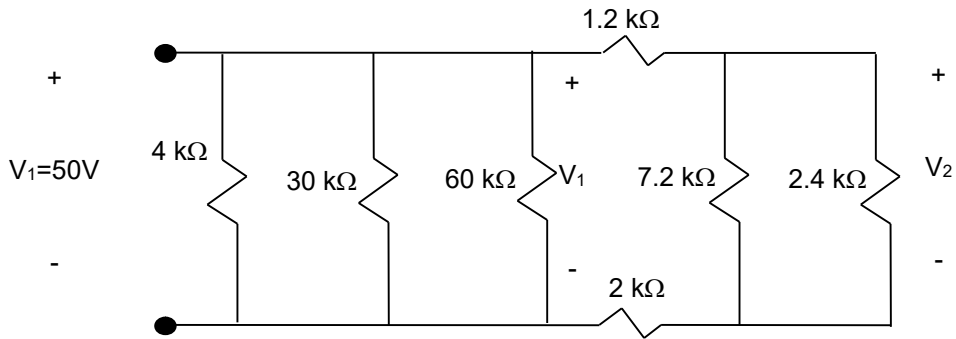d) Given $V_{30\text{k}\Omega} = 50 \text{ V}$, Find $V_{2.4\Omega} = ?$





$$R_{eq} = 7.2 \parallel 2.4 = 1 / (1/7.2 + 1/2.4) = 1.8 \text{ k}\Omega$$

$$V_2 = (V_1 / (1.2 + 1.8 + 2)) * 1.8 = (50/5) * 1.8 = 18 \text{ V}$$

4U. Use voltage division or current division to find the specified voltages or currents:

- Suppose the voltage drop across the 40 Ω resistor in the following circuit A is 40 V, positive at the top of the resistor. What is the voltage drop across the 10 Ω resistor?
- Suppose the current in the 10 Ω resistor in the following circuit A is 60 mA, flowing from left to right. What is the current flowing in the 30 Ω resistor?
- Suppose the current in the 2 k Ω resistor in the following circuit B is 10 mA, flowing from left to right. What is the current in the 60 k Ω resistor?
- Suppose the voltage drop across the 4 k Ω resistor in the following circuit B is 50 V, Positive at top of the resistor. What is the voltage drop across the 2.4 k Ω resistor?

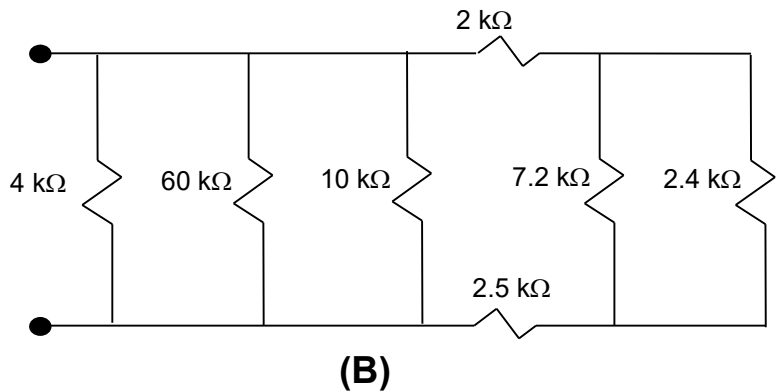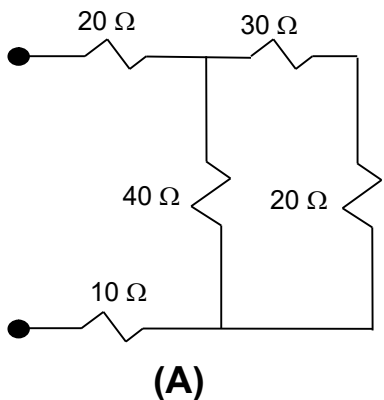


Solution:

5S. The Current in the 9 Ω resistor in the circuit shown below is 1A.

- Find v_g .

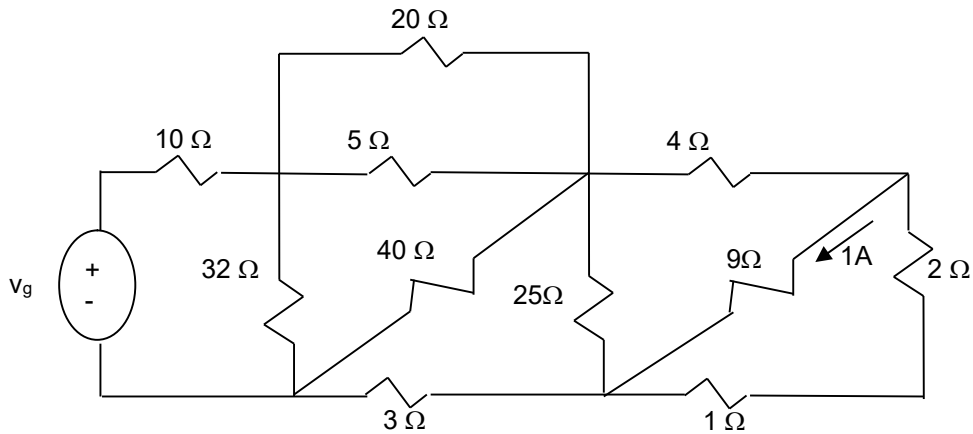b) Find the power dissipated in the $20\ \Omega$ resistor.




Solution:

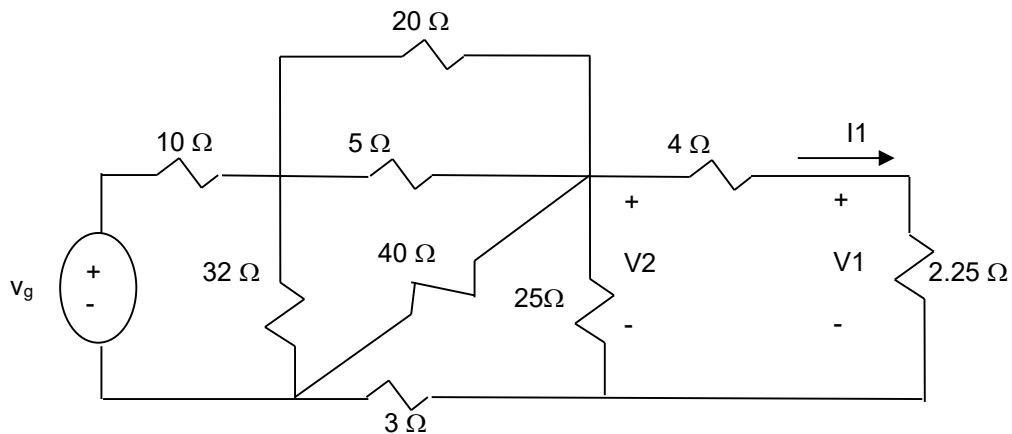a) $V_g = ?$

$$I_{9\Omega} = 1\text{ A} \rightarrow V_{9\Omega} = 9 * 1 = 9\text{ V}$$

$$Req1 = (1+2) \parallel 9 = 2.25\ \Omega$$




$$I1 = V1/2.25 = 9/2.25 = 4\text{ A}$$

$$V2 = I1 * (4+2.25) = 25\text{ V}$$

$$Req2 = (4 + 2.25) \parallel 25 = 5\ \Omega$$


$$Req3 = (20 \parallel 5) = 4\ \Omega$$

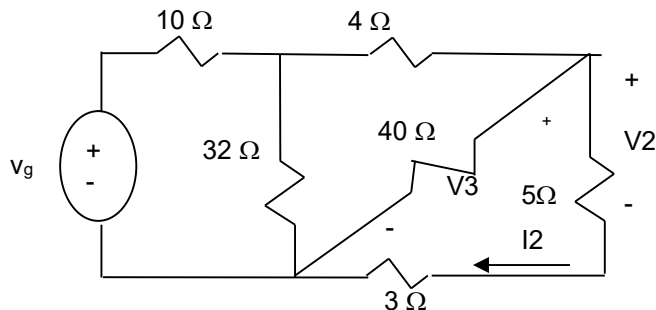

$$I2 = V2/5 = 25/5 = 5\text{ A}$$

$$V3 = I2 * (5 + 3) = 40\text{ V}$$
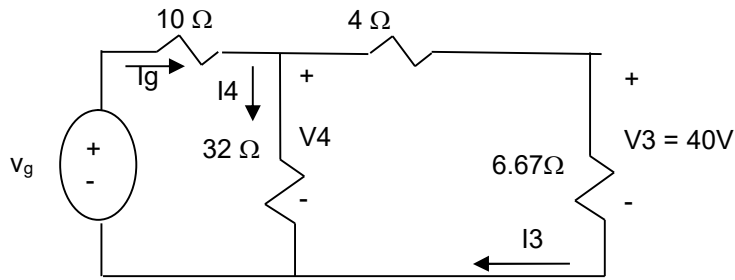
$$Req4 = ((5+3) \parallel 40) = 6.67\ \Omega$$



$$I_3 = V_3 / 6.67 = 40 / 6.67 = 6 \text{ A}$$

$$V_4 = I_3 * (4 + 6.67) = 6 * 10.67 = 64 \text{ V}$$

$$I_4 = (V_4) / 32 = 2 \text{ A}$$

$$\text{KCL} \rightarrow -I_g + I_4 + I_3 = 0 \rightarrow I_g = 8 \text{ A}$$

$$\text{KVL} \rightarrow -V_g + (10 * 8) + (32 * 2) = 0 \rightarrow V_g = 144 \text{ V}$$


b) $P_{20\Omega} = ?$

Using $I_3 \rightarrow V_{4\Omega} = 6 * 4 = 24 \text{ V}$ which is the same as $V_{20\Omega}$

$$P_{20\Omega} = (V_{20\Omega})^2 / 20 = (24)^2 / 20 = 28.8 \text{ W}$$


5U. The Current in the 5Ω resistor in the circuit shown below is 100 mA .

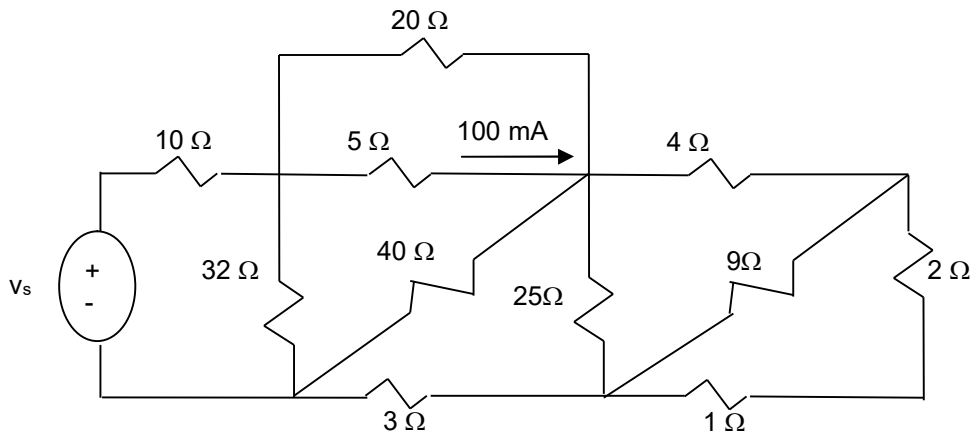- Find v_s .
- Find the power dissipated in the 40Ω resistor.




Solution:

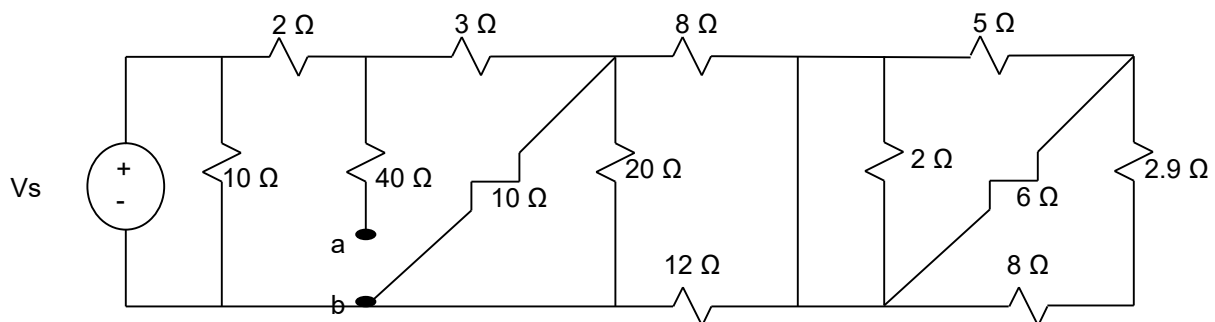5Ub. Find the power delivered by the source ($V_s = 10 \text{ Volts}$) in the following circuit.



Solution:

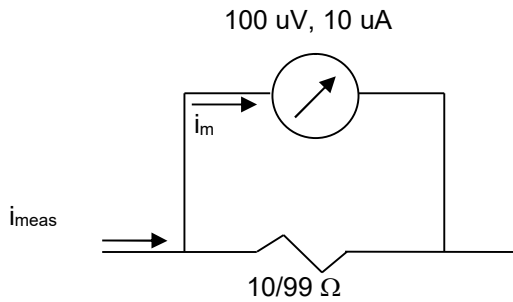
6S. a) For the following ammeter circuit, show that the current in d'Arsonval movement is always $1/100^{\text{th}}$ of the current being measured.



- b) What would the fraction be if the $50 \mu\text{V}, 2 \mu\text{A}$ movement were used in a 1A ammeter?
- c) Would you expect a uniform scale on a d'Arsonval Ammeter?

Solution:

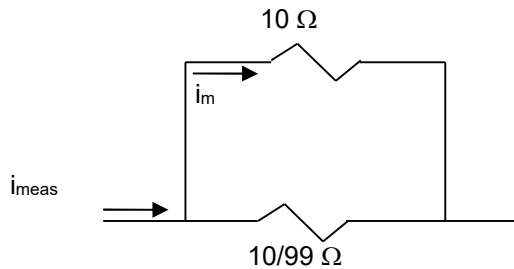a) Internal Resistance of d'Arsonval = $R_{DA} = 100 \mu\text{V} / 10 \mu\text{A} = 10 \Omega$ so we can redraw a ohmic equivalent:




Apply the current divider $\rightarrow i_m = i_{\text{meas}} (10/99 / (10/99 + 10)) \rightarrow i_m / i_{\text{meas}} = 1/100$

We

b) Ratio = $i_m / i_{\text{meas}} = 2 \mu\text{A} / 1\text{A} = 1/500,000$

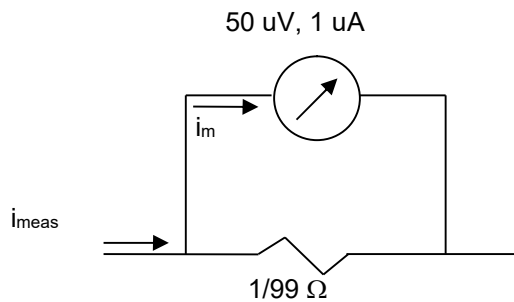c) Yes, if d'Arsonval is assumed to be ideal.

6U. a) For the following ammeter circuit, what is the ratio of current through d'Arsonval movement (i_m) to the current being measured (i_{meas}).




- b) What would the fraction be if the $80 \mu\text{V}, 10 \mu\text{A}$ movement were used in a 1A ammeter?
- c) Would you expect a uniform scale on a d'Arsonval Ammeter?

Solution:

7S. A d'Arsonval voltmeter is shown below. Find the value of R_v for each of the following full Scale Readings:

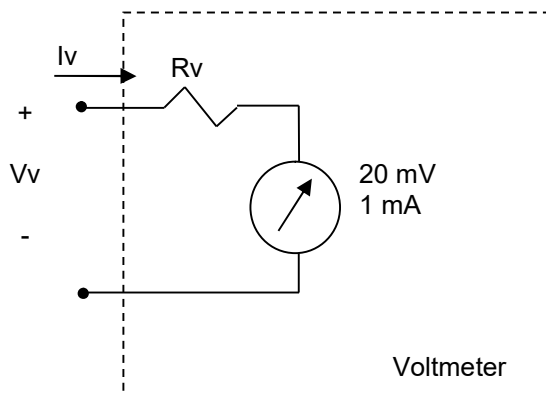- a) 50 V
- b) 5 V
- c) 250 mV
- d) 25 mV




Solution:

- * We know that d'Arsonval movement has $R_{am} = 20 \text{ mV} / 1\text{mA} = 20 \Omega$
- * In general we have $V_v = I_v (R_v + 20)$ Since Max V is given in the question, we should use $I = 1\text{mA}$ which is causes maximum movement as the I_v

- a) $V_v=50 \text{ V} \rightarrow 50 = .001(R_v + 20) \rightarrow R_v= 49,980 \Omega$
- b) $V_v=5 \text{ V} \rightarrow 5 = .001(R_v + 20) \rightarrow R_v= 4,980 \Omega$
- c) $V_v=250 \text{ mV} \rightarrow .250 = .001(R_v + 20) \rightarrow R_v= 230 \Omega$
- d) $V_v=25 \text{ mV} \rightarrow .025 = .001(R_v + 20) \rightarrow R_v= 5 \Omega$

7U. A d'Arsonval voltmeter is shown below. Find the value of R_v for each of the following full Scale Readings:

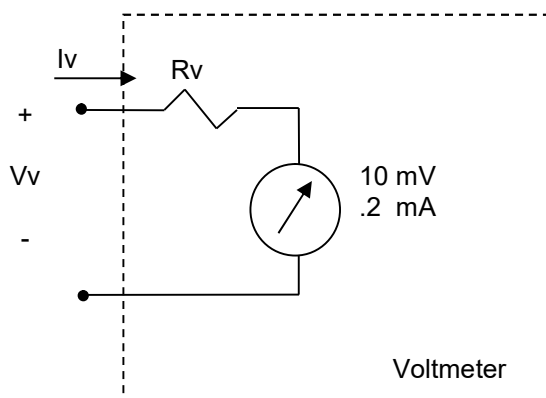- a) 100 V
- b) 25 V
- c) 500 mV
- d) 5 mV




Solution:

8S. The bridge circuit shown below is energized from a 6V dc source. The bridge is balanced when $R_1=200\Omega$, $R_2=500\Omega$ and $R_3=800\Omega$.

- a) What is the value R_x .
- b) How much current (in milliamperes) does the dc source supply?

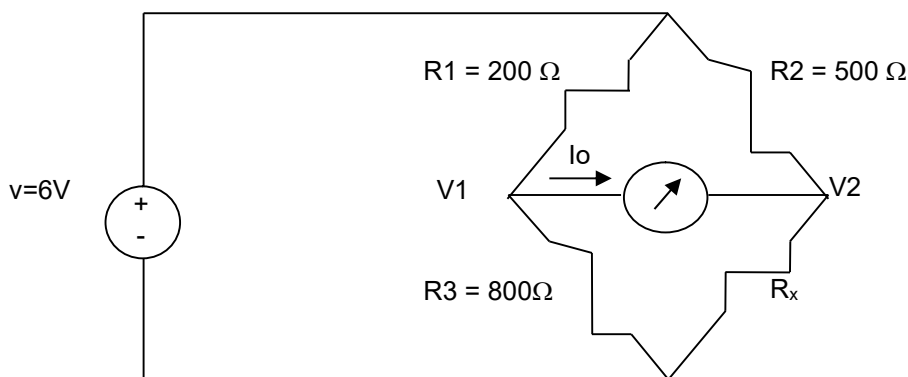- c) Which resistor in the circuit absorbs the most power? How much power does it absorb?
 d) Which resistor absorbs the least power? How much power does it absorb?



Solution:


- a) Balanced Bridge $\rightarrow I_o = 0$ and $V_1 = V_2$
 Currents through R_1 and R_3 are the same I_1
 Current through R_2 and R_x are the same I_2
 $V = 6 = I_1 \cdot (200 + 800) \rightarrow I_1 = 6 \text{ mA}$
 $V_1 = 800 \cdot 6 \text{ mA} = 4.8 \text{ V} = V_2$

 $V_{R1} = V_{R2} \rightarrow 200 \cdot I_1 = 500 \cdot I_2 \rightarrow 200 \cdot 6 = 500 \cdot I_2 \rightarrow I_2 = 2.4 \text{ mA}$
 $V_{R3} = V_{Rx} \rightarrow 800 \cdot I_1 = R_x \cdot I_2 \rightarrow 800 \cdot 6 = R_x \cdot 2.4 \rightarrow R_x = 2,000 \Omega$
- b) $I =$ current of dc source = ?
 $I = I_1 + I_2 = 6 + 2.4 = 8.4 \text{ mA}$
- c) Which resistor absorbs most power?
 $P_{R1} = (200) \cdot (6 \cdot 10^{-3})^2 = 7.2 \text{ mW}$
 $P_{R2} = (500) \cdot (2.4 \cdot 10^{-3})^2 = 2.88 \text{ mW}$
 $P_{R3} = (800) \cdot (6 \cdot 10^{-3})^2 = 28.8 \text{ mW}$
 $P_{Rx} = (2000) \cdot (2.4 \cdot 10^{-3})^2 = 11.5 \text{ mW}$

 $R_3 = 800 \Omega$ absorbs the most power equal to 28.8 mW
- d) Which resistor absorbs least power?
 $R_2 = 500 \Omega$ absorbs the most power equal to 2.88 mW


8U. The bridge circuit shown below is energized from a 10V dc source. The bridge is balanced when $R_1=100\Omega$, $R_2=200\Omega$ and $R_3=1200\Omega$.

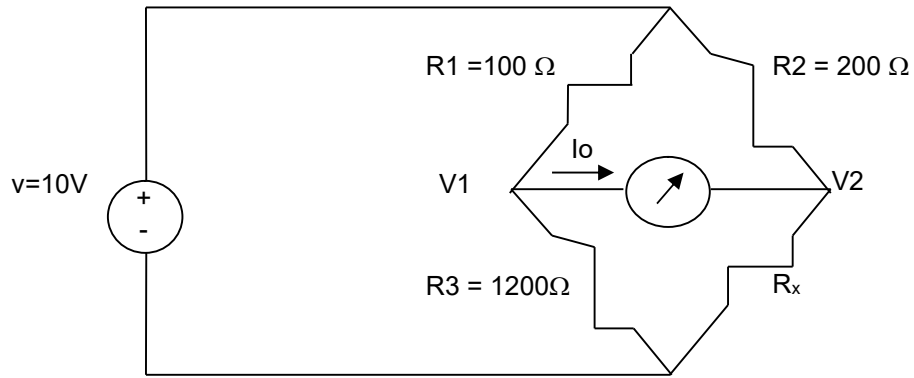- a) What is the value R_x .
 b) How much current (in milliamperes) does the dc source supply?
 c) Which resistor in the circuit absorbs the most power? How much power does it absorb?
 d) Which resistor absorbs the least power? How much power does it absorb?




Solution:

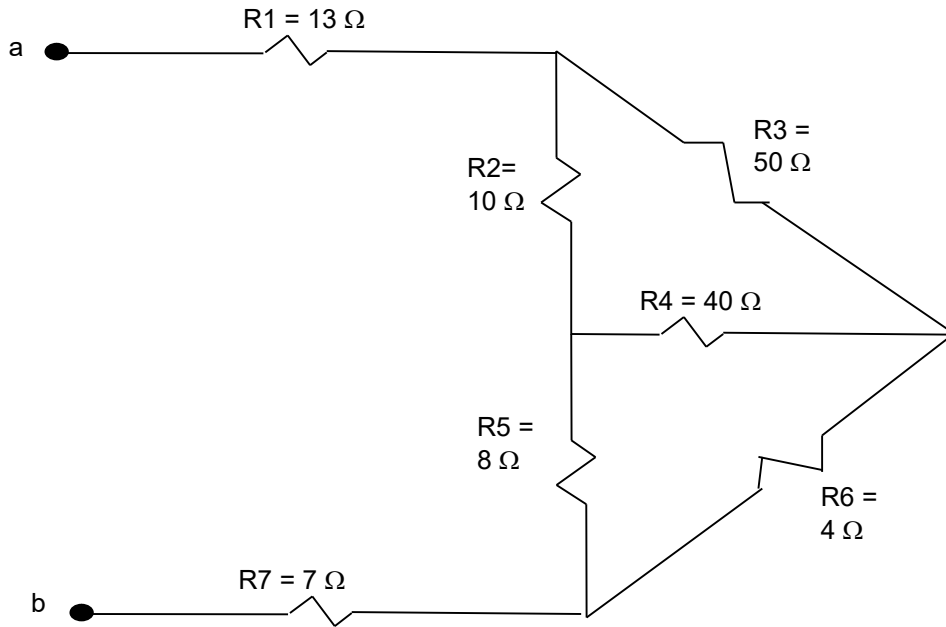- 9S. a) Find the equivalent resistance R_{ab} in the circuit shown below by using Δ -to- Y transformation involving the resistors R_2 , R_3 and R_4 .
 b) Repeat (a) using a Y -to- Δ transformation involving resistors R_2 , R_4 and R_5 .
 c) Give two additional Δ -to- Y or Y -to- Δ transformations that could be used to find R_{ab} .



Solution:

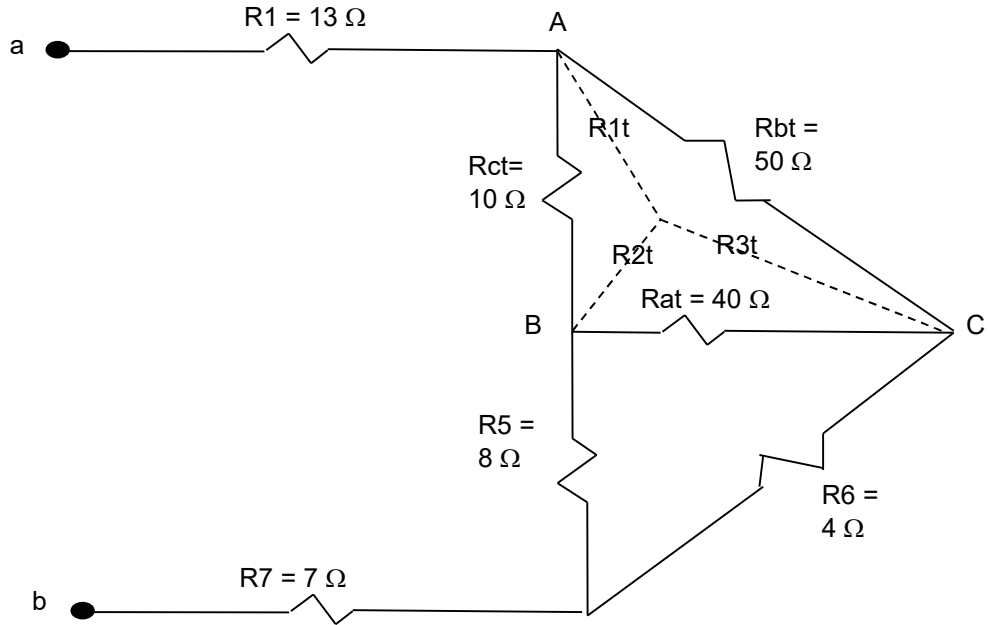a) Δ -to-Y transformation with R2, R3 and R4.




$$R_{1t} = \frac{R_{bt}R_{ct}}{R_{at} + R_{bt} + R_{ct}} = \frac{10 * 50}{40 + 10 + 50} = 5\Omega$$

$$R_{2t} = \frac{R_{at}R_{ct}}{R_{at} + R_{bt} + R_{ct}} = \frac{40 * 10}{40 + 10 + 50} = 4\Omega$$


$$R_{3t} = \frac{R_{at}R_{bt}}{R_{at} + R_{bt} + R_{ct}} = \frac{40 * 50}{40 + 10 + 50} = 20\Omega$$

New Circuit with Transformation

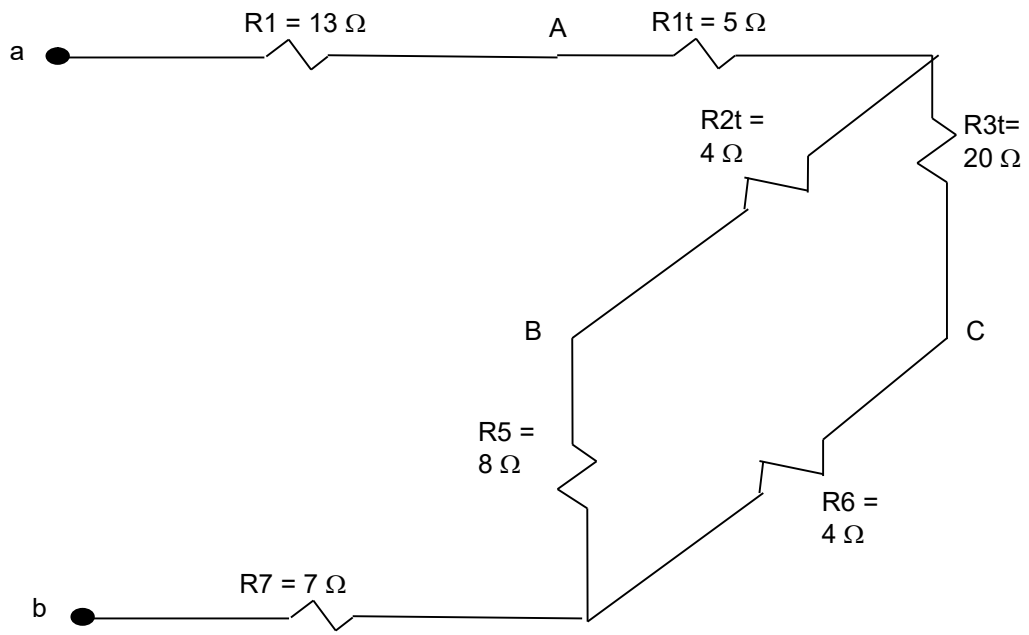

$$R_{eq}(ab) = 13 + 5 + ((8+4) || (20+4)) + 7 = 33 \Omega$$

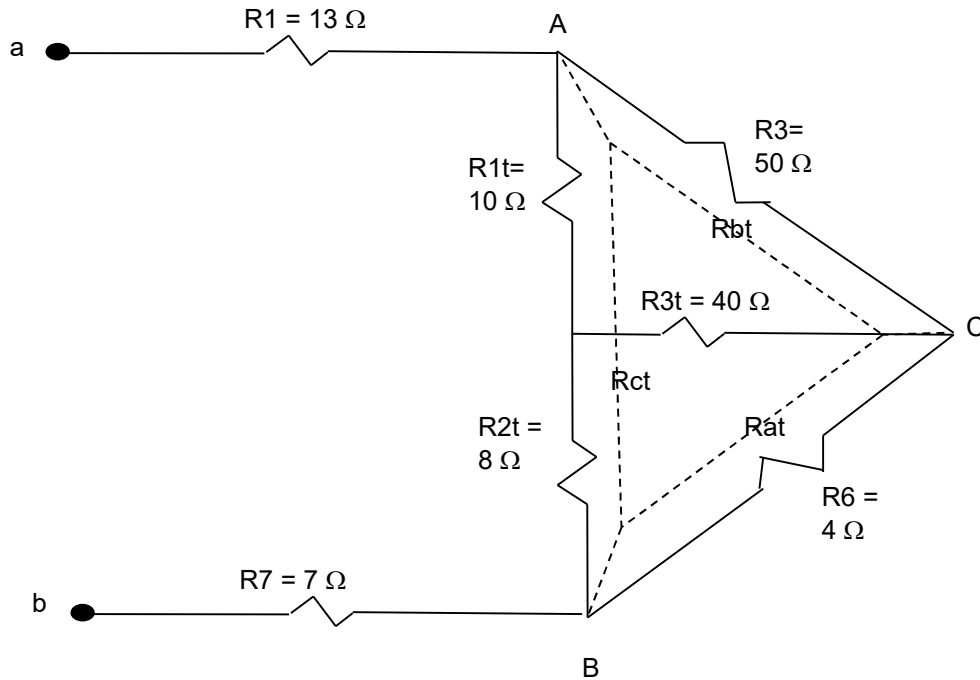b) Y-to- Δ transformation with R2, R4 and R5.



$$R_{at} = \frac{R_{1t}R_{2t} + R_{2t}R_{3t} + R_{3t}R_{1t}}{R_{1t}} = \frac{10 * 8 + 8 * 40 + 40 * 10}{10} = 80\Omega$$


$$R_{bt} = \frac{R_{1t}R_{2t} + R_{2t}R_{3t} + R_{3t}R_{1t}}{R_{2t}} = \frac{10 * 8 + 8 * 40 + 40 * 10}{8} = 100\Omega$$

$$R_{ct} = \frac{R_{1t}R_{2t} + R_{2t}R_{3t} + R_{3t}R_{1t}}{R_{3t}} = \frac{10 * 8 + 8 * 40 + 40 * 10}{40} = 20\Omega$$


New Circuit with Transformation

$$R_{eq}(ab) = 13 + 20 \parallel ((50 \parallel 100) + (4 \parallel 80)) + 7 = 33 \Omega$$

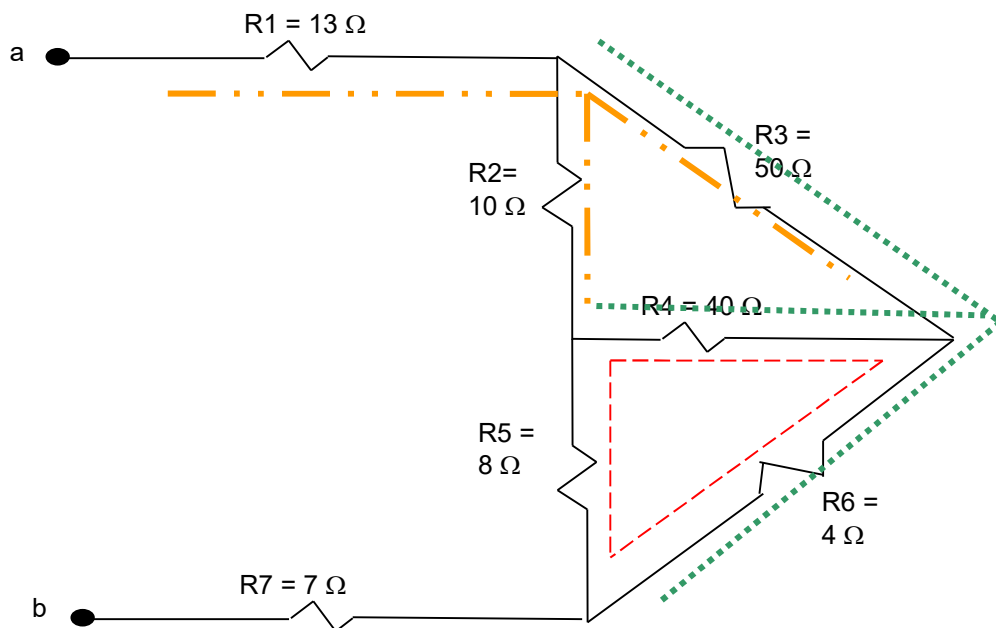c) Identify at least a couple of transforms



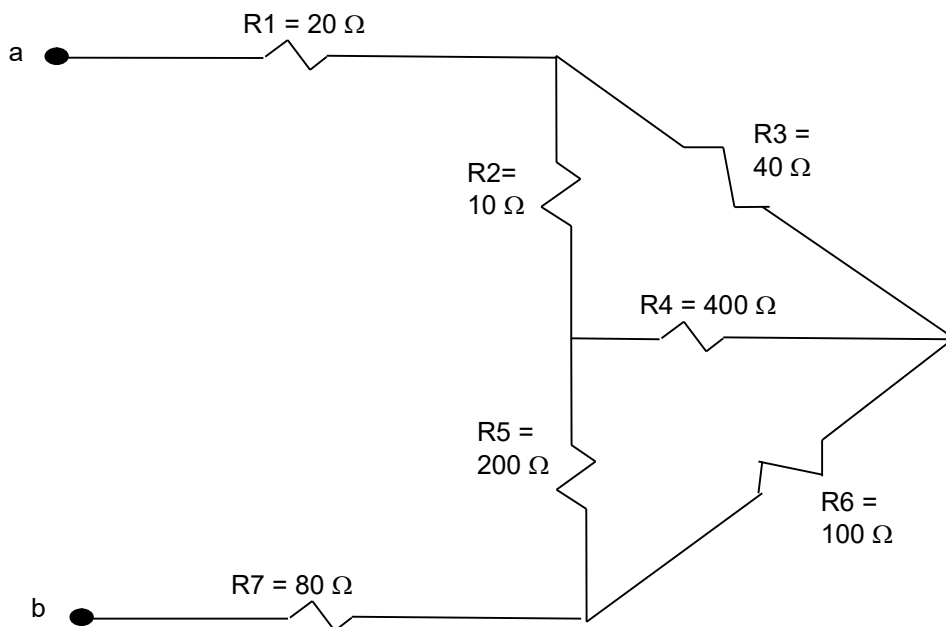- 9U. a) Find the equivalent resistance R_{ab} in the circuit shown below by using Δ -to- Y transformation involving the resistors R_2 , R_3 and R_4 .
 b) Repeat (a) using a Y -to- Δ transformation involving resistors R_2 , R_4 and R_5 .
 c) Give two additional Δ -to- Y or Y -to- Δ transformations that could be used to find R_{ab} .



Solution: