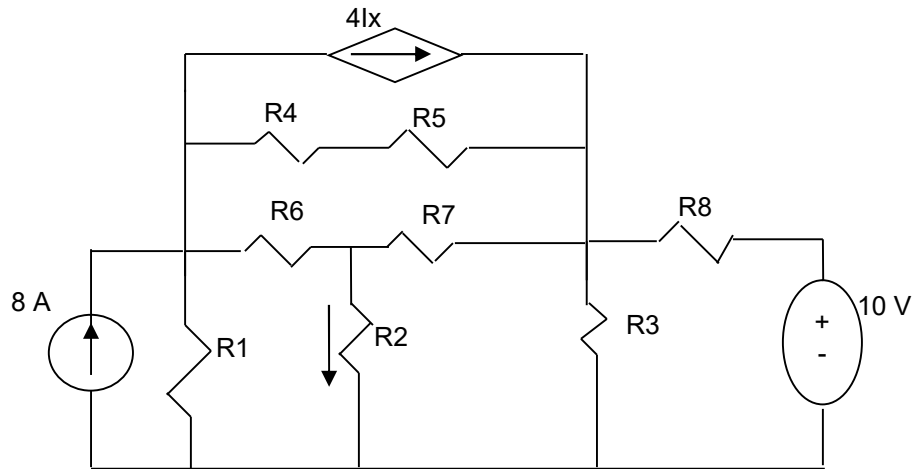


## Fundamentals of Electrical Circuits - Chapter 4

1S. For the following circuit find:

- Number of Branches
- Number of Branches with unknown current
- Number of Essential Branches
- Number of Essential Branches with unknown current
- Number of Nodes
- Number of Essential Nodes
- Number of Meshes




**Solution:**

- Number of Branches = 11
- Number of Branches with unknown current = 9
- Number of Essential Branches = 9
- Number of Essential Branches with unknown current = 7
- Number of Nodes = 6
- Number of Essential Nodes = 4
- Number of Meshes = 6


1U. For the following circuit:

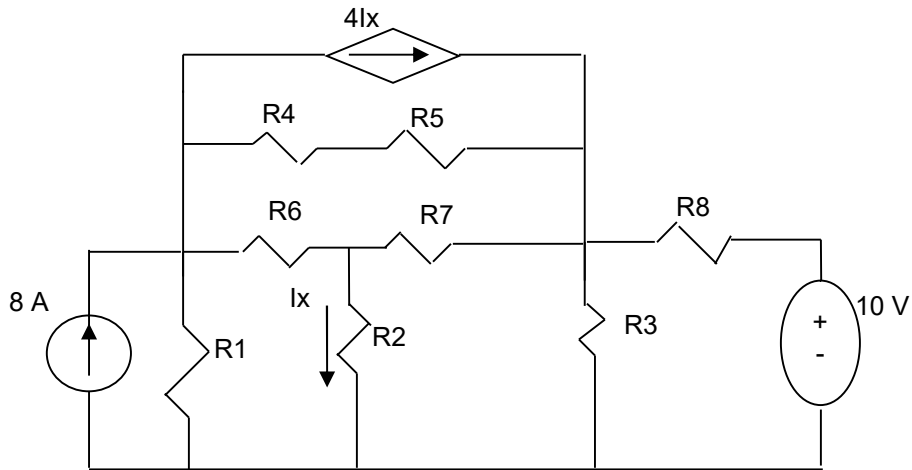- How many independent equations can be derived using Kirchhoff's Current Law (KCL)?
- How many independent equations can be derived using Kirchhoff's Voltage Law (KVL)?
- What two meshes should be avoided in applying Kirchhoff's Voltage Law (KVL)?



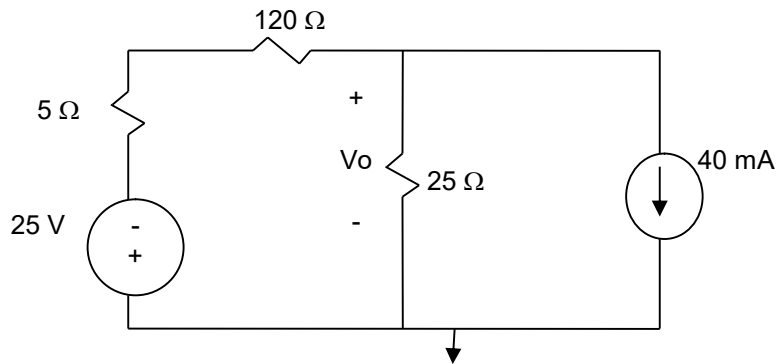**Solution:**

2S. Use the node-voltage method to find  $V_o$  in the circuit shown below.




**Solution:**

$$\frac{V_o - (-25)}{125} + \frac{V_o}{25} + 40 \cdot 10^{-3} = 0$$

$$6V_o = -30$$


$$V_o = -5$$

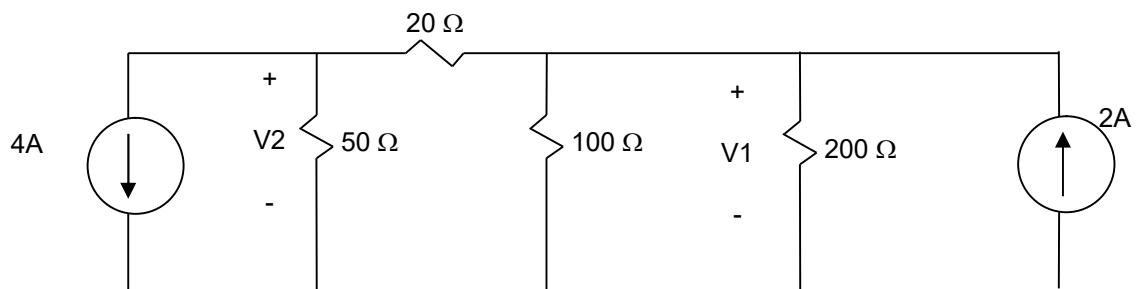2U. Use the node-voltage method to find  $V_1$  and  $V_2$  in the following circuit.



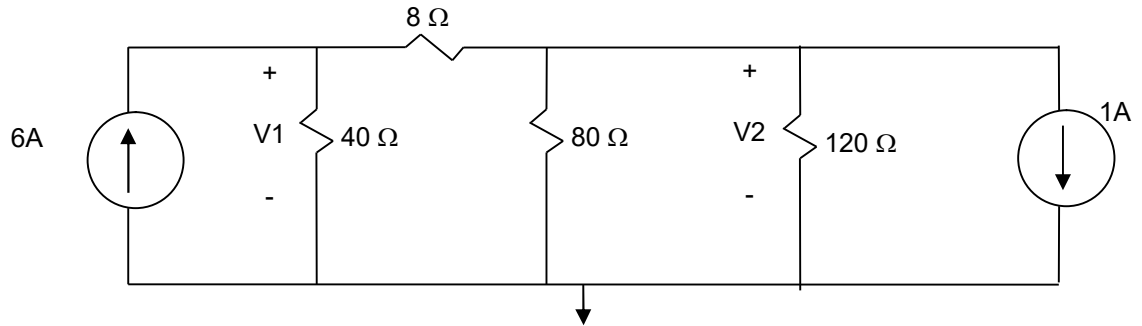**Solution:**

2Sb. Use the node-Voltage method to find  $V_1$  and  $V_2$  in the following circuit.



**Solution:**

Three Nodes so we need to write two Node-Voltage equations:

$$\text{Node } V_1 \rightarrow -6 + V_1/40 + (V_1 - V_2)/8 = 0$$

$$\text{Node } V_2 \rightarrow 1 + V_2/120 + V_2/80 + (V_2 - V_1)/8 = 0$$


Solve two unknowns, two equations

$$6V_1 - 5V_2 = 240$$


$$-30V_1 + 35V_2 = -240$$

$$V_1 = 120 \text{ V} \quad \text{and} \quad V_2 = 96 \text{ V}$$

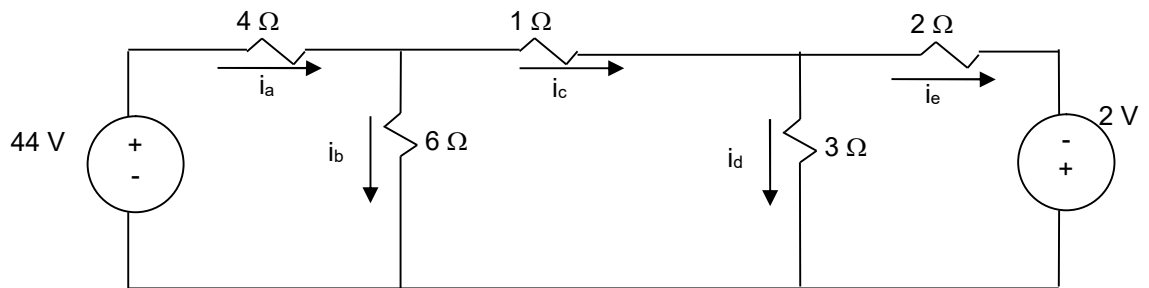2Sc. a) Use the node-voltage method to find the branch currents ( $i_a - i_e$ ) in the circuit shown below.  
 b) Find the total power developed in the circuit.



**Solution:**

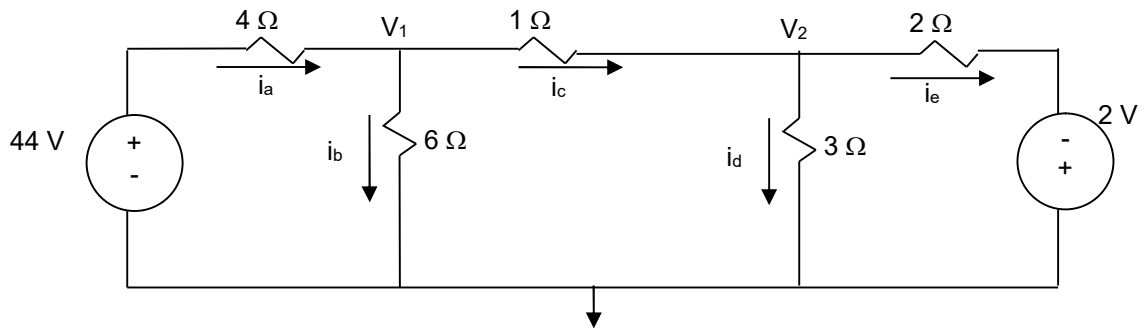

a) Three essential nodes so we can write 2 Node-Voltage Equations:

$$\frac{V_1 - 44}{4} + \frac{V_1}{6} + \frac{V_1 - V_2}{1} = 0$$

$$\frac{V_2 - (-2)}{2} + \frac{V_2}{3} + \frac{V_2 - V_1}{1} = 0$$

$$17V_1 - 12V_2 = 132$$

$$-6V_1 + 11V_2 = -6$$

$$V_1 = 12 \quad \text{and} \quad V_2 = 6$$

∴


$$i_a = 8A; \quad i_b = 2A; \quad i_c = 6A; \quad i_d = 2A; \quad i_e = 4A;$$

$$i_a - i_e = 8 - 4 = 4A$$

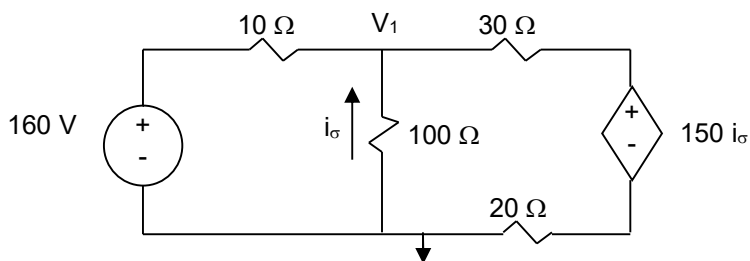b)  $P_{\text{total developed}} = ?$

$$P_{\text{total developed}} = -4*(8)^2 - 6*(2)^2 - 1*(6)^2 - 3*(2)^2 - 2*(4)^2 = -360W$$

3S. Use the node-voltage method to calculate the power delivered by the dependent voltage source in the following circuit.



**Solution:**

There is only one node and one reference node → one node-voltage equation

$$\frac{V_1 - 160}{10} + \frac{V_1}{100} + \frac{V_1 - 150i_\sigma}{50} = 0 \quad \text{and} \quad i_\sigma = -\frac{V_1}{100}$$


$$\text{Re place } i_\sigma \text{ in first equation} \Rightarrow \frac{V_1 - 160}{10} + \frac{V_1}{100} + \frac{V_1 + 1.5V_1}{50} = 0 \Rightarrow V_1 = 100V$$

$$\text{Dependent Voltage} = V_d = 150i_\sigma = -\frac{150V_1}{100} = -150V$$

$$50\Omega \text{ Current} = I_{50\Omega} = \frac{V_1 - V_d}{50} = \frac{100 - (-150)}{50} = 5$$


$$P_{\text{Dependent Source}} = V_d * I_{30\Omega} = (-150) * (5) = -750W \text{ delivered}$$

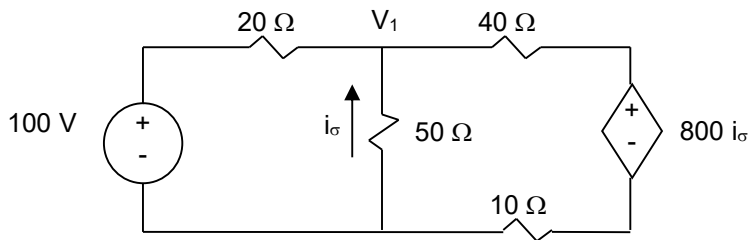3U. Use the node-voltage method to calculate the power delivered by the dependent voltage source in the following circuit.




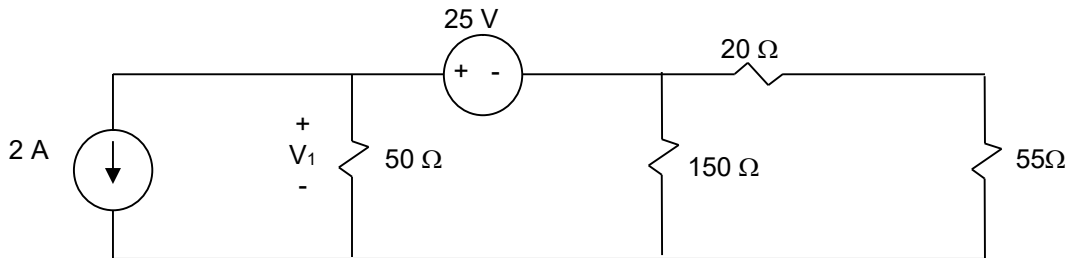**Solution:**

4S. Use the node-voltage method to find  $V_1$  and the power delivered by the 25 V voltage source in the following circuit,



**Solution:**  $P_{25V} = ?$

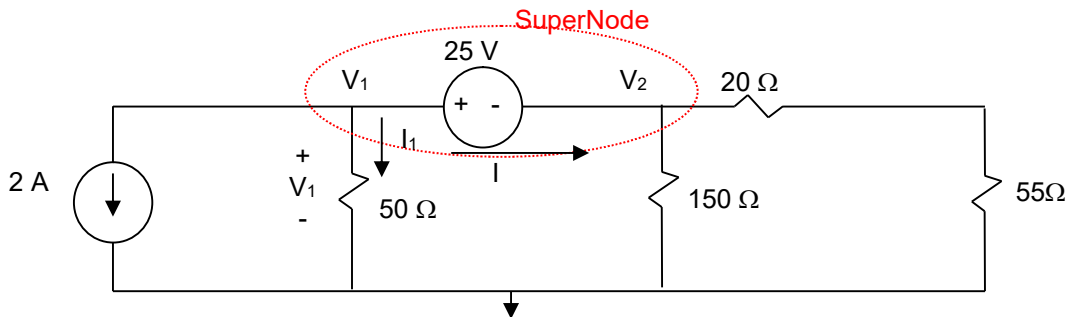

Use SuperNode technique ( $V_1$  &  $V_2$ ):

KCL for Super Node (all current out of supernode)  $\rightarrow 2 + V_1/50 + V_2/150 + V_2/75 = 0$

We also have the relationship between nodes in super node  $\rightarrow V_1 - V_2 = 25$


$$V_1 = -37.5 \text{ V}; \quad V_2 = -62.5 \text{ V};$$

$$I_1 = V_1/50 = -37.5/50 = -0.75 \text{ A}$$

$$\text{KCL at node } V_1 \rightarrow 2 - 0.75 + I = 0 \rightarrow I = -1.25 \text{ A}$$


$$P_{25V} = V_1 \cdot I = (25) \cdot (-1.25) = -31.25 \text{ W delivered.}$$

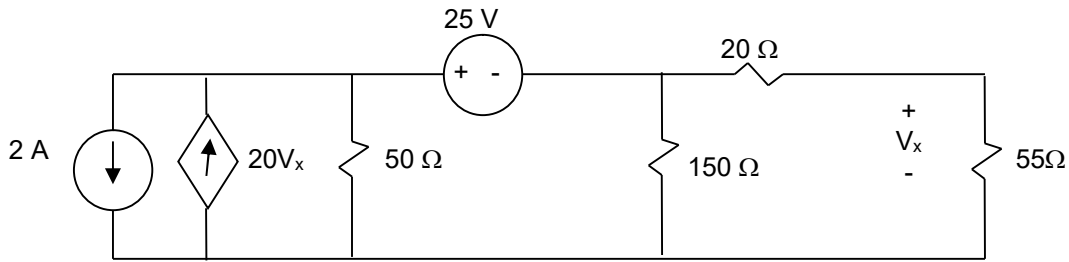4U. Use the node-voltage method to find  $V_x$  and the power consumed by the  $55 \Omega$  resistor in the following circuit:




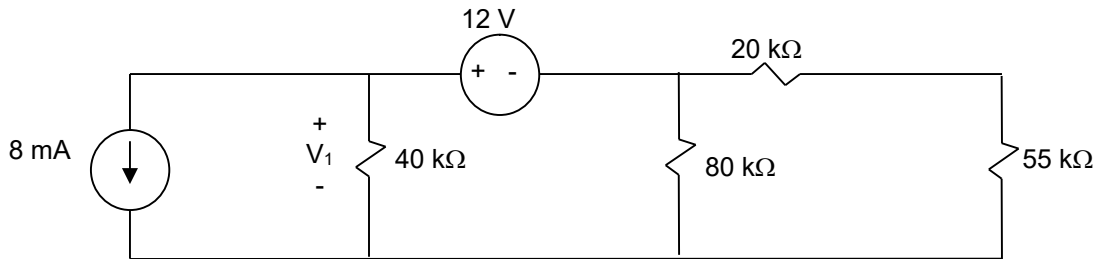**Solution:**

4Sb. Use the node-voltage method to find  $V_1$  in the following circuit,



**Solution:**

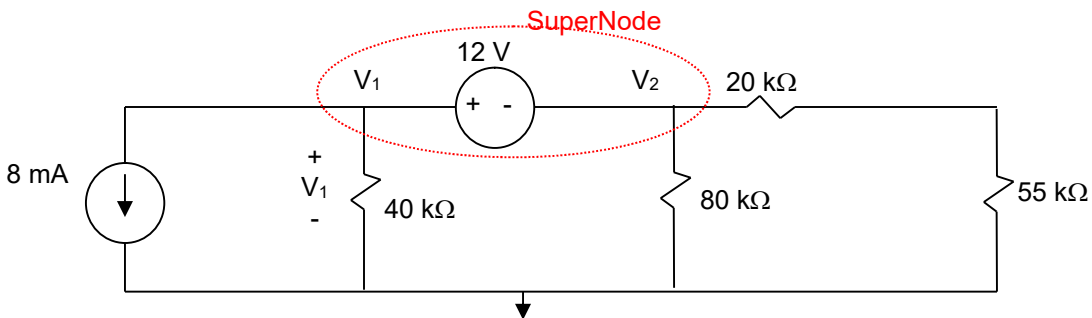

Use SuperNode technique ( $V_1$  &  $V_2$ ):


KCL for Super Node (all current out of SuperNode)  $\rightarrow .008 + V_1/40,000 + V_2/80,000 + V_2/75,000 = 0$

We also have the relationship between nodes in super node  $\rightarrow V_1 - V_2 = 12$

**$V_1 = -151.3 \text{ V}$** ;


5S. a) Use the mesh-current method to find the total power developed in the following circuit.

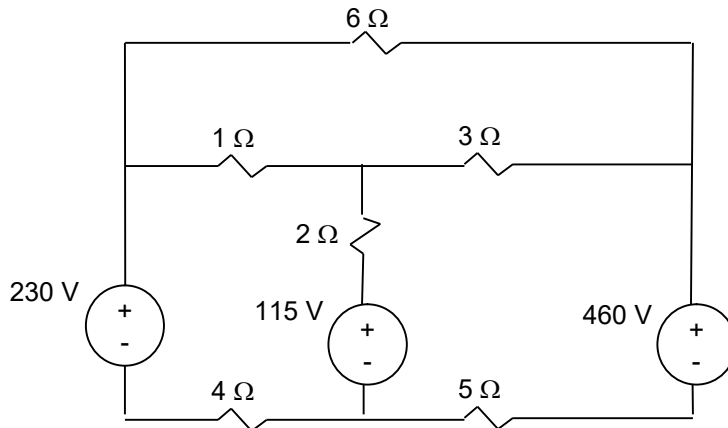b) Check your answer by showing that the total power developed equals the total power dissipated.



**Solution:**

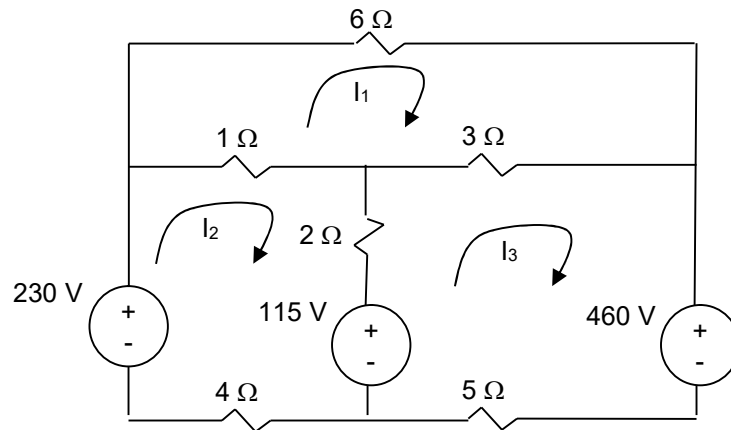a) Applu Mesh-Current to find total power developed



$$\text{Loop \#1 KVL} \rightarrow 6I_1 + 3(I_1 - I_3) + (I_1 - I_2) = 0$$

$$\text{Loop \#2 KVL} \rightarrow -230 + (I_2 - I_1) + 2(I_2 - I_3) + 115 + 4I_2 = 0$$

$$\text{Loop \#3 KVL} \rightarrow 460 + 5I_3 - 115 + 2(I_3 - I_2) + 3(I_3 - I_1) = 0$$

$$I_1 = -10.6\text{A}; \quad I_2 = 4.4\text{A}; \quad I_3 = -36.8\text{A};$$

$$P_{230\text{V}} = 230 \cdot I_2 = 230 \cdot (4.4) = -1,012 \text{ W Developed}$$

$$P_{115\text{V}} = 115 \cdot (I_2 - I_3) = 115 \cdot (4.4 - (-36.8)) = 4,738 \text{ W Consumed}$$

$$P_{460\text{V}} = 460 \cdot I_3 = 460 \cdot (-36.8) = -16,928 \text{ W Developed}$$

$$P_{\text{Total developed}} = P_{230\text{V}} + P_{460\text{V}} = -1,012 - 16,928 = -17,940 \text{ W}$$


b)  $P_{\text{Total developed}} = P_{\text{Total consumed}} ?$

$$\begin{aligned} P_{\text{Total consumed}} &= 6(I_1)^2 + 3(I_1 - I_3)^2 + (I_1 - I_2)^2 + 2(I_2 - I_3)^2 + 4(I_2)^2 + 5(I_3)^2 + P_{115\text{V}} \\ &= 6(-10.6)^2 + 3(-10.6 - (-36.8))^2 + (-10.6 - 4.4)^2 + 2(4.4 - (-36.8))^2 + 4(4.4)^2 + 5(- \\ &36.8)^2 + P_{115\text{V}} \end{aligned}$$

$$P_{\text{Total consumed}} = P_{\text{Total developed}} = 17940 \rightarrow \text{Answer checked.}$$


5U. a) Use the mesh-current method to find the total power developed in the following circuit.

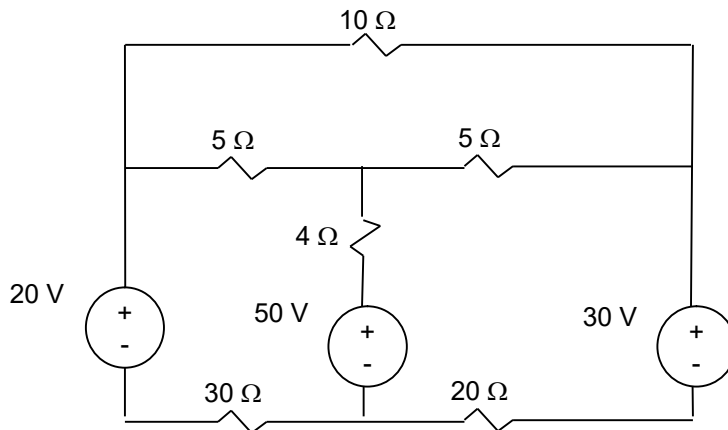b) Check your answer by showing that the magnitude of total power developed equals the total power dissipated.




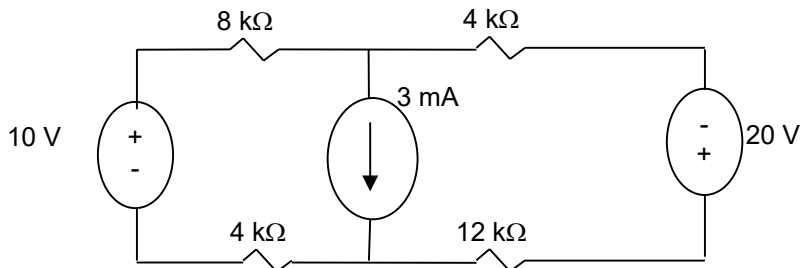**Solution:**

5Sb. Use the mesh-current method to find the total power consumed in the circuit shown below.



**Solution:**

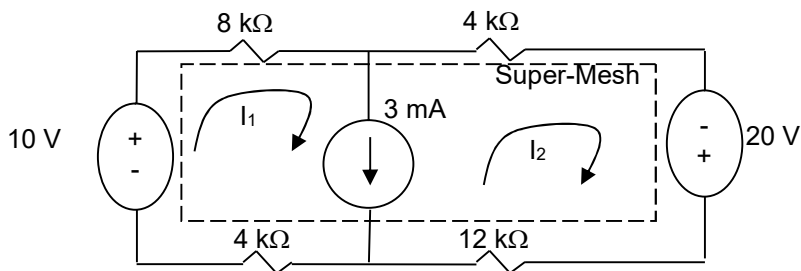

Super-Mesh KVL  $\rightarrow -10 + 8 I_1 + 4 I_2 - 20 + 12 I_2 + 4 I_1 = 0 \rightarrow 12 I_1 + 16 I_2 = 30$   
 Relationship of two mesh within super-mesh  $\rightarrow I_1 - I_2 = 3$

$I_1 = 2.8 \text{ mA}$ ;  $I_2 = -0.2 \text{ mA}$ ;


Resistors and the 20v Source are consuming power

$$\begin{aligned}
 P_{\text{Total Dissipated}} &= \sum(I^2R) + P_{20\text{v Source}} \\
 &= 8000 \cdot I_1^2 + 4000 \cdot I_2^2 + 12000 \cdot I_2^2 + 4000 \cdot I_1^2 + 20 \cdot 0.2 \times 10^{-3} \\
 &= 12000 \cdot (0.0028)^2 + 16000 \cdot (0.0002)^2 + 20 \cdot (0.0002) \\
 &= 0.099 \text{ W}
 \end{aligned}$$

6S. a) Use the mesh-current method to solve for  $I_\Delta$  in the following circuit.  
 b) Find the power delivered by the independent current source.




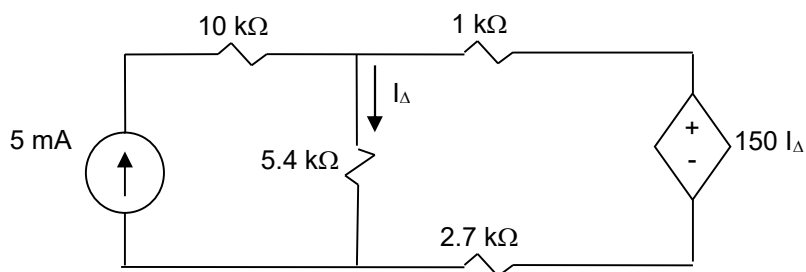c) Find the power delivered by the dependent voltage source.



**Solution:**

a) find  $I_{\Delta}$

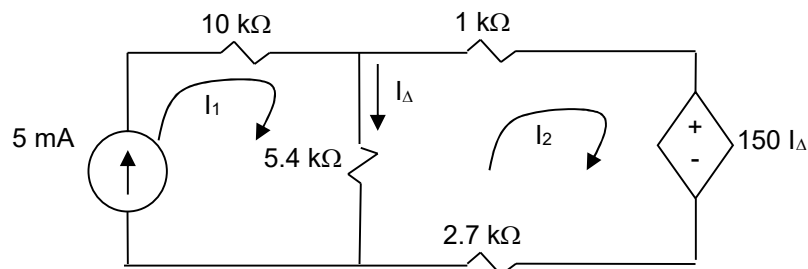

KVL @  $I_1 \rightarrow I_1 = 0.005 \text{ A}$

KVL @  $I_2 \rightarrow 5400 (I_2 - I_1) + 1000 I_2 + 150 I_{\Delta} + 2700 I_2 = 0$


Dep. Source Equation  $\rightarrow I_{\Delta} = I_1 - I_2$

Solve the above three equations  $\rightarrow I_1 = 0.0050 \text{ A}, I_2 = 0.0029 \text{ A}, I_{\Delta} = 0.0021 \text{ A}$

b)  $P_{0.005\text{A source}} = I_1 * V_{0.005\text{A source}} = (-0.005) * (10000 * 0.0050 + 5400 * 0.0021) = -0.307 \text{ W}$  "Generated"

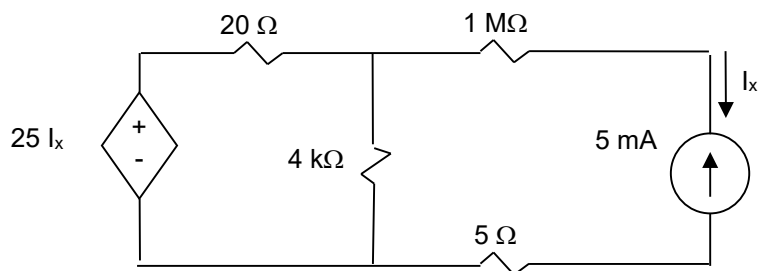c)  $P_{150I_{\Delta} \text{ dependent source}} = I_2 * V_{0.005\text{A source}} = (0.0029) * (150 * 0.0021) = 0.0009135 \text{ W}$  Consumed

6U. a) Use the mesh-current method to find  $I_x$  in the following circuit.




b) Find the power delivered by the independent current source.

c) Find the power delivered by the dependent voltage source.

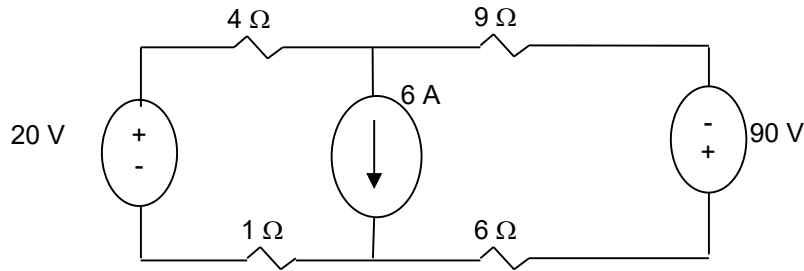
**Solution:**

7S. Use the mesh-current method to find the total power dissipated in the circuit shown below.



**Solution:**

a)

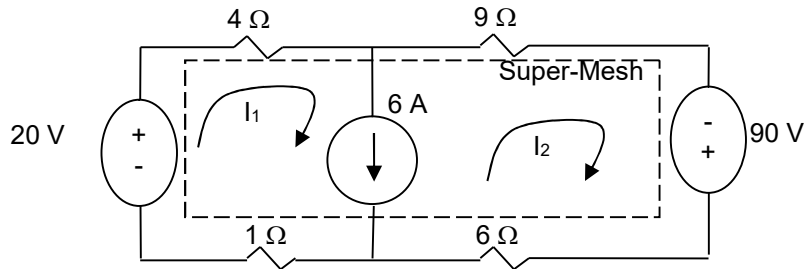


$$\text{Super-Mesh KVL} \rightarrow -20 + 4 I_1 + 9 I_2 - 90 + 6 I_2 + I_1 = 0 \rightarrow 5 I_1 + 15 I_2 = 110$$

$$\text{Relationship of two mesh within super-mesh} \rightarrow I_1 - I_2 = 6$$

$$I_1 = 10 \text{ A}; \quad I_2 = 4 \text{ A};$$

$$P_{\text{Total Dissipated}} = \Sigma(I^2 R) = 4 I_1^2 + 9 I_2^2 + 6 I_2^2 + I_1^2 = 4 \cdot 10^2 + 9 \cdot 4^2 + 6 \cdot 4^2 + 1 \cdot 10^2 = 740 \text{ W}$$

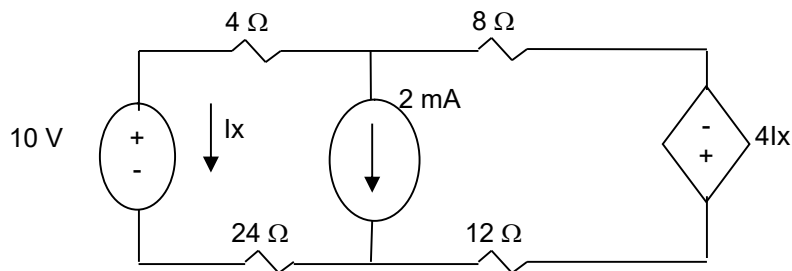7U. Use the mesh-current method to find the total power dissipated in the circuit shown below.




**Solution:**

8S. Assume you have been asked to find the power dissipated in the  $10 \Omega$  resistor in the following circuit.

- Which method of circuit analysis would you recommend? Explain why.
- Use your recommendation method of analysis to find the power dissipated in the  $10 \Omega$  resistor.
- Would you change your recommendation if the problem had been to find the power developed by the  $4 \text{ A}$  current source? Explain.

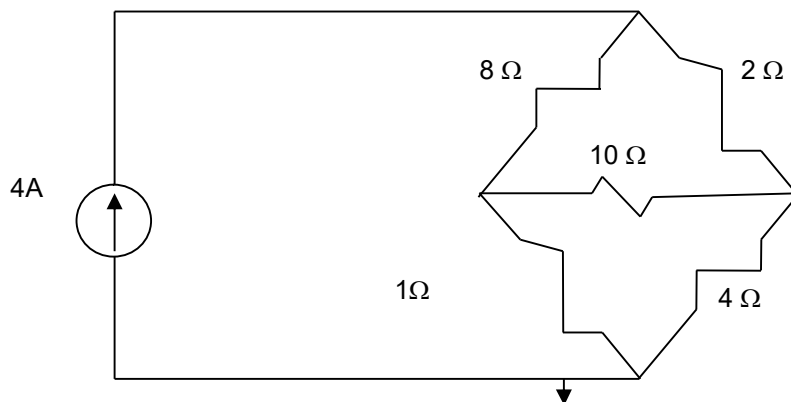d) Find the power delivered by the 4 A current source.



**Solution:**


a) Which method?

\* 4 Essential nodes      3 node-voltage equations

\* 6 Essential branches       $(6 - (4-1)) = 3$  current-mesh equations

Mesh-Current since one of the Mesh currents is known so there are only two mesh-current equations.

b)  $P_{10\Omega} = ?$

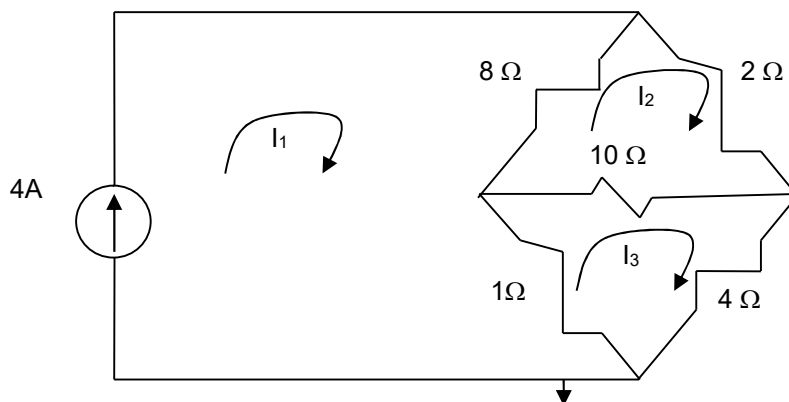

KVL for Mesh#1  $\rightarrow I_1 = 4 \text{ A}$

KVL for Mesh#2  $\rightarrow 8(I_2 - I_1) + 2I_2 + 10(I_2 - I_3) = 0$

KVL for Mesh#3  $\rightarrow (I_3 - I_1) + 10(I_3 - I_2) + 4I_3 = 0$

Inset  $I_1$  value into equations #2 & #3

$$20 I_2 - 10 I_3 = 32$$

$$-10 I_2 + 15 I_3 = 4$$

$$I_2 = 2.6; \quad I_3 = 2 \text{ A}$$

$$P_{10\Omega} = R \cdot I^2 = (10) \cdot (2.6 - 2)^2 = 3.6 \text{ W}$$


c) No, since it is straight forward to calculate the voltage drop across the current source from mesh currents.

d)  $P_{4A \text{ source}} = ?$

$$P_{4A \text{ source}} = I \cdot V = -4 \cdot (8 \cdot (I_1 - I_2) + 1 \cdot (I_1 - I_3)) = -4 \cdot (8 \cdot (4 - 2.6) + 1 \cdot (4 - 2))$$


$$P_{4A \text{ source}} = 52.8 \text{ W delivered}$$

- 8U. Assume you have been asked to find the power dissipated in the  $20\ \Omega$  resistor in the following circuit.
- Which method of circuit analysis would you recommend? Explain why.
  - Use your recommendation method of analysis to find the power dissipated in the  $20\ \Omega$  resistor.
  - Would you change your recommendation if the problem had been to find the power developed by the  $5\ \text{A}$  current source? Explain.
  - Find the power delivered by the  $5\ \text{A}$  current source.

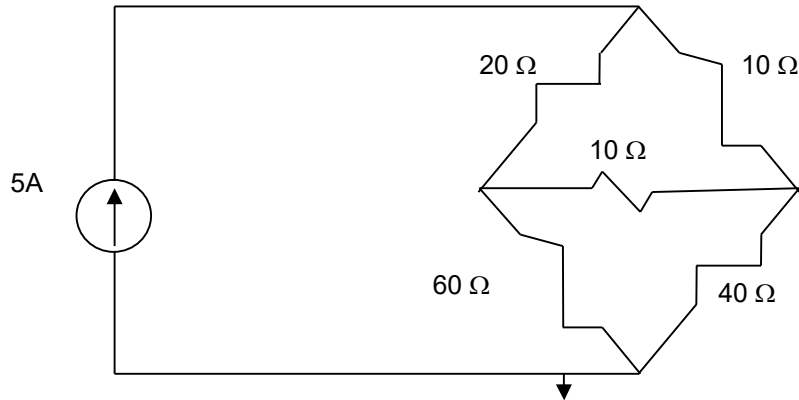

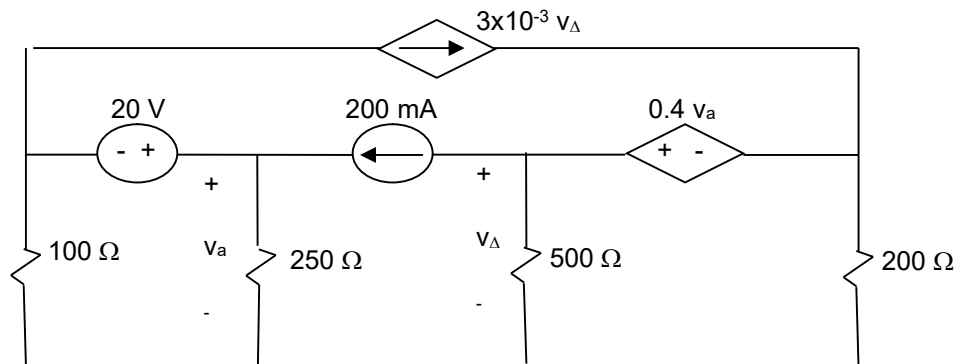**Solution:**


- 8Sb. a) Would you use the node-voltage or mesh-current method to find the power absorbed by the  $20\ \text{V}$  source in the following circuit? Explain your choice.
- b) Use the method your selected in (a) to find the power.



**Solution:**

- a) ) Which method?
- \* 5 Essential nodes      4 node-voltage equations
  - \* 8 Essential branches       $(8 - (5-1)) = 4$  mesh-current equations
- although number of equations are the same, Node-voltage is a better choice. This is driven by the fact that with the two super nodes and easier constraint equation formulation.

b)  $P_{20V \text{ sources}} = ?$

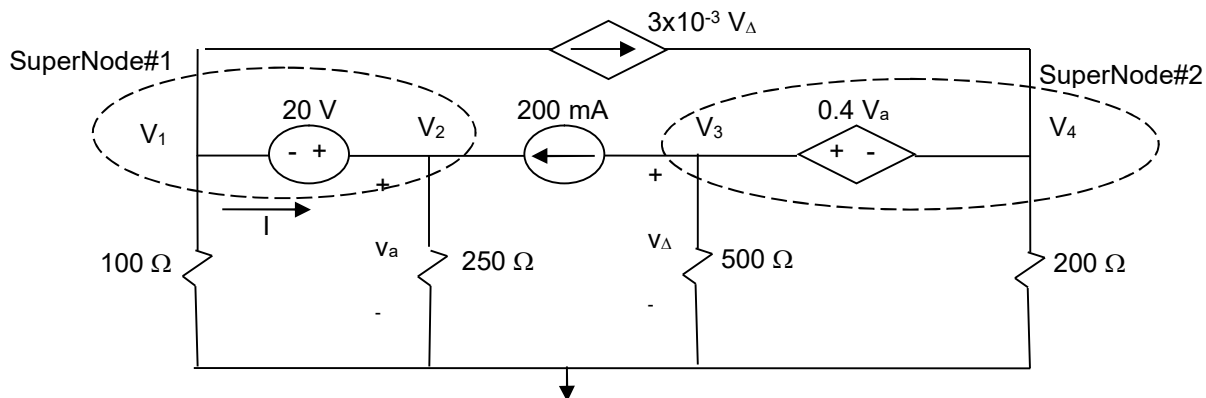

Super Node #1 KCL  $\rightarrow -0.2 + .003V_{\Delta} + V_1/100 + V_2/250 = 0$

Relationship  $\rightarrow V_2 - V_1 = 20$

Super Node #2 KCL  $\rightarrow +0.2 - .003V_{\Delta} + V_4/200 + V_3/500 = 0$

Relationship  $\rightarrow V_3 - V_4 = 0.4 V_a$

Constraint equations in term of node voltages

$V_a = V_2$

$V_{\Delta} = V_3$

Simplified equation:

$0.01 V_1 + 0.004 V_2 + 0.003V_3 = 0.2$

$-V_1 + V_2 = 20$

$-0.001 V_3 + 0.005 V_4 = -0.2$

$+0.4 V_2 - V_3 + V_4 = 0$


$V_1=15.48 \text{ V}; V_2=35.482 \text{ V}; V_3=-32.23 \text{ V}; V_4=-46.45\text{V};$

Note: I can be found by apply KCL at node  $V_1$

$P_{20V \text{ Source}} = - (20)*I = -20(V_1/100 + 0.003V_3) = -20(15.48/100 + 0.003*(-32.28)) = -1.16 \text{ W}$


9S. a) Use a series of source transformations to find  $i_o$  in the following circuit

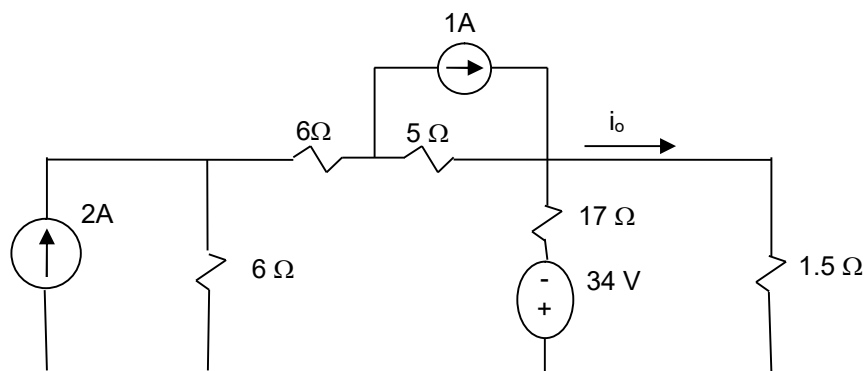b) Verify your solution by using the mesh-current method to find  $i_o$ .




**Solution:**

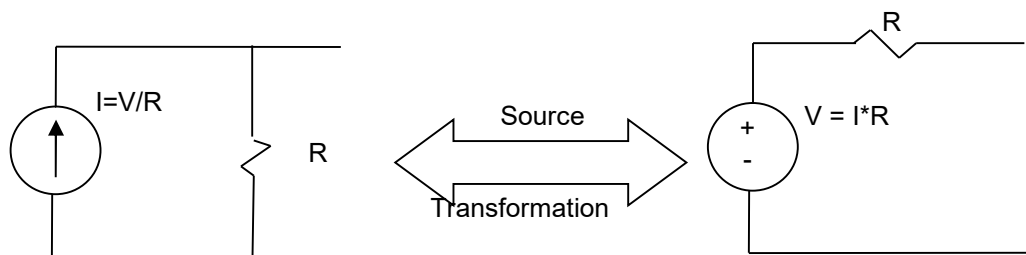
a) Use the following transformation rule:



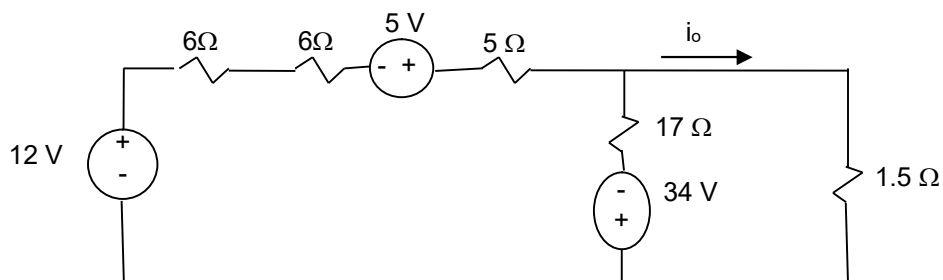
First Set of transformations ( $2A, 6\Omega \rightarrow 12V$ ;  $1A, 5\Omega \rightarrow 5V$ )



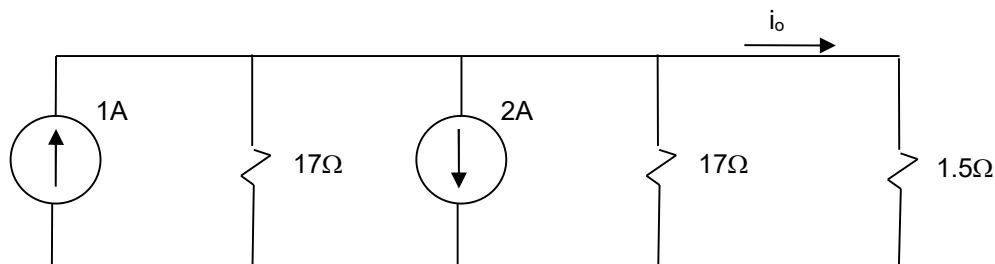Second Set of transformations  
 ( $12+5V, 12+5\Omega \rightarrow 1A$ ;  $34V, 17\Omega \rightarrow 2A$ ;) )




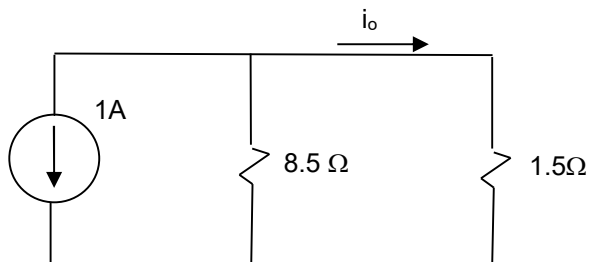Simplify by adding current source and Req for  $17 \parallel 17 = 8.5\Omega$



$$i_o = -1 * ( 8.5 / (1.5 + 8.5) ) = -0.85 A$$

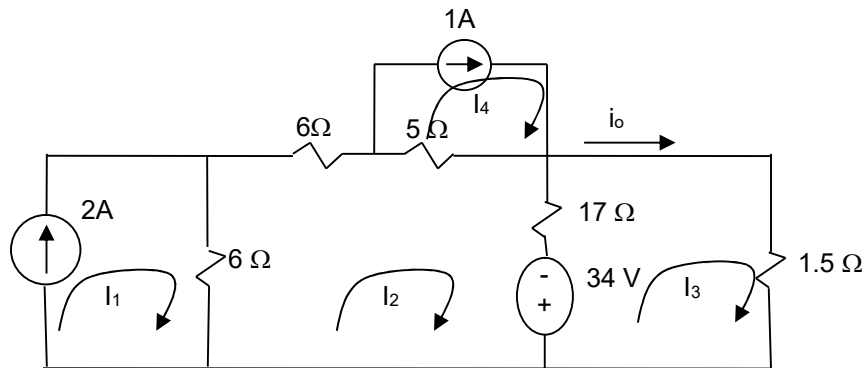b) Find  $i_o$  using mesh-current technique.



KVL for Mesh #1  $\rightarrow I_1 = 2 \text{ A}$

KVL for Mesh #2  $\rightarrow 6(I_2 - I_1) + 6 I_2 + 5(I_2 - I_4) + 17 (I_2 - I_3) - 34 = 0$

KVL for Mesh #3  $\rightarrow +34 + 17 (I_3 - I_2) + 1.5 I_3 = 0$


KVL for Mesh #4  $\rightarrow I_4 = 1 \text{ A}$

$$34I_2 - 17I_3 - 5I_4 = 46$$

$$-17 I_2 + 18.5I_3 = -34$$


$$I_3 = i_o = -0.85 \text{ A}$$

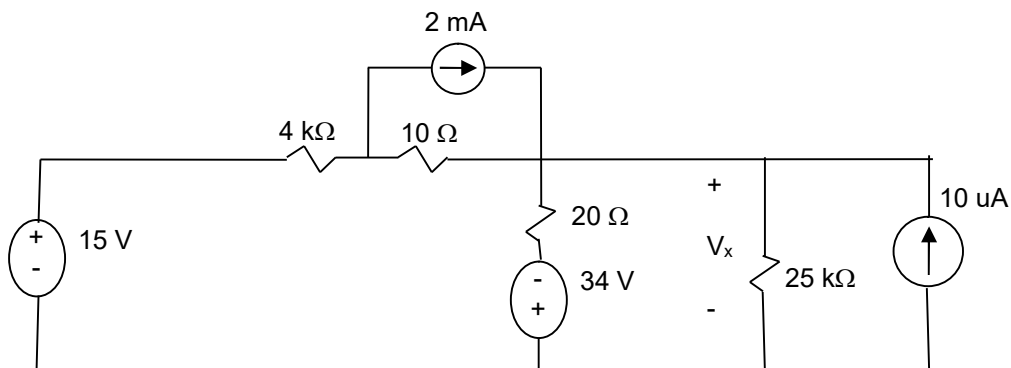- 9U. a) Use a series of source transformations to find  $V_x$  in the following circuit  
 b) Verify your solution by using the Node-Voltage method to find  $V_x$ .



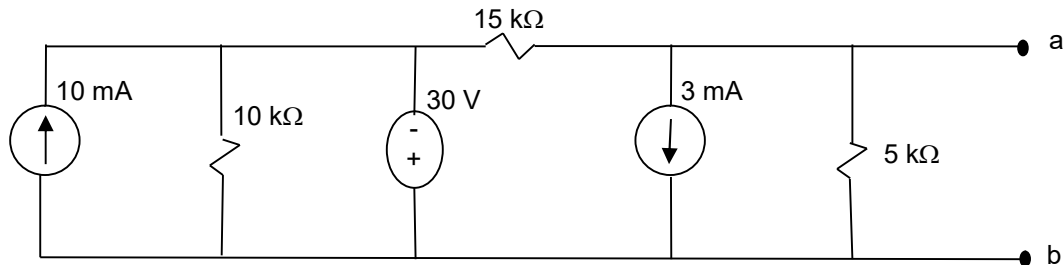
**Solution:**

- 10 S. Find the Norton equivalent with respect to the terminals a,b in the following circuit.




**Solution:**

Step 1 -- Find  $I_{sc}$  (a-b shorted)

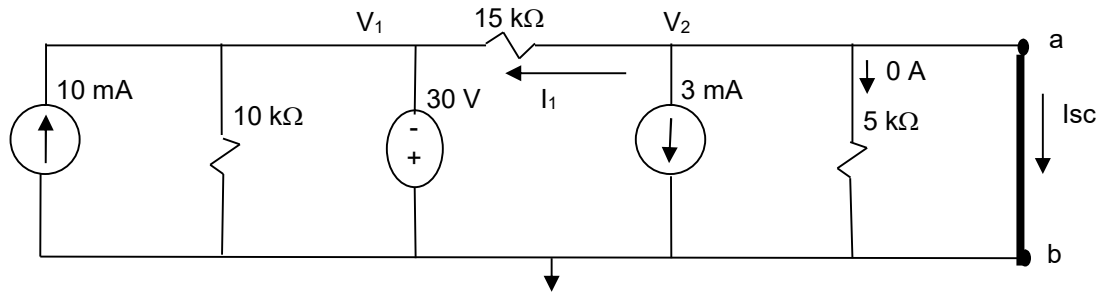


$V_1 = -30 \text{ V}$   
 $V_2 = 0 \text{ V}$   
 $I_1 = (V_2 - V_1) / 15\text{K} = 2 \text{ mA}$   
 KCL at  $V_2 \rightarrow I_{sc} + 0 + 3 + I_1 = 0 \rightarrow I_{sc} = -5 \text{ mA}$

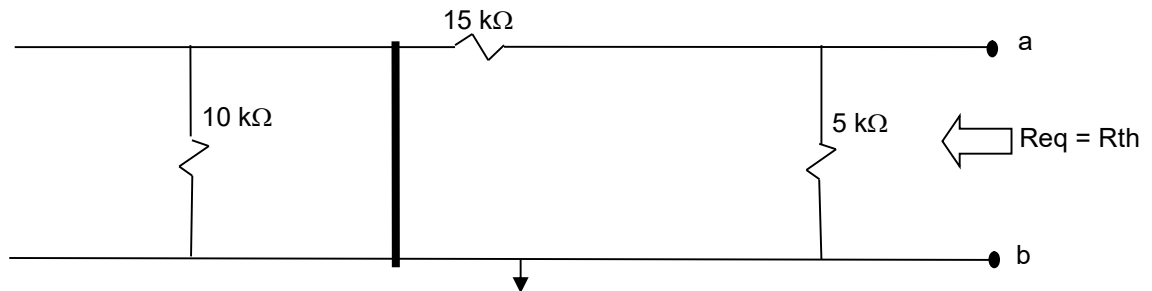Step 2 – Find  $R_{eq} = R_{th}$  by deactivating sources  
 (Current Source  $\rightarrow$  Open  $I=0$ ; Voltage Source  $\rightarrow$  short  $V=0$ )




$R_{th} = ((10 \parallel 0) + 15) \parallel 5 = 3.75 \text{ k}\Omega$

Step3 – Draw Norton Equivalent

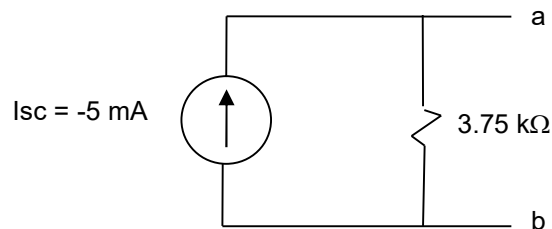

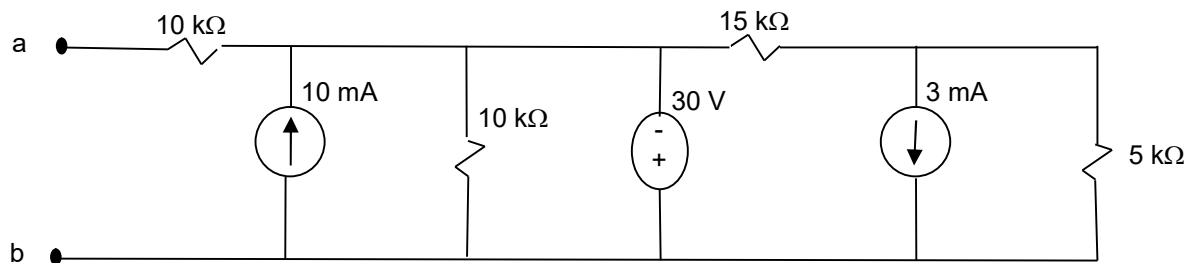
10U. Find the Norton equivalent with respect to the terminals a,b in the following circuit.



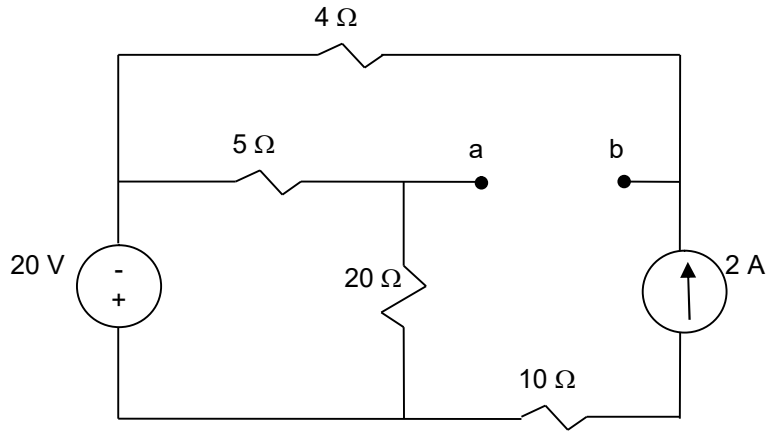**Solution:**



**10S.** Find and draw the Norton equivalent of the following circuit at terminals a and b.




**Solution:**

Deactivate sources to find  $R_{th} = R_{ab}$

$$R_{th} = R_{ab} = (4 + (5 \parallel 20)) = 8 \Omega$$

Find  $I_{sc} = I_{ab}$

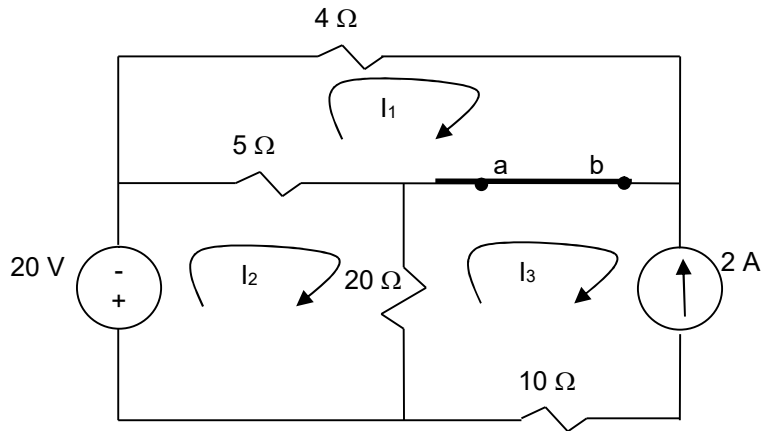

$$\text{Mesh \#1} \rightarrow 4I_1 + 5(I_1 - I_2) = 0 \rightarrow$$

$$9I_1 - 5I_2 = 0 \rightarrow I_2 = 9I_1/5$$


$$\text{Mesh \#2} \rightarrow +20 + 5(I_2 - I_1) + 20(I_2 - I_3) = 0$$

$$-5I_1 + 25I_2 = -60 \rightarrow -5I_1 + 45I_1 = -60 \rightarrow I_1 = -1.5$$

$$\text{Mesh \#3} \rightarrow I_3 = -2$$


$$\text{Find } I_{sc} = I_{ab} = I_3 - I_1 = -0.5$$

Norton Equivalent:

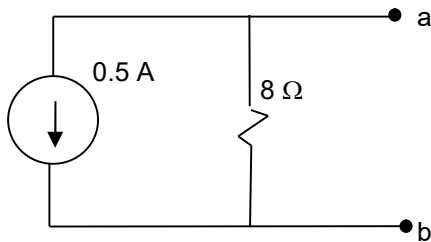

11S. The Wheatstone bridge in the circuit shown below, is balanced when  $R_3$  equals  $500\Omega$ . If the galvanometer had a resistance of  $50\Omega$ , how much current will the galvanometer detects when the bridge is unbalanced by setting  $R_3$  to  $501\Omega$ .

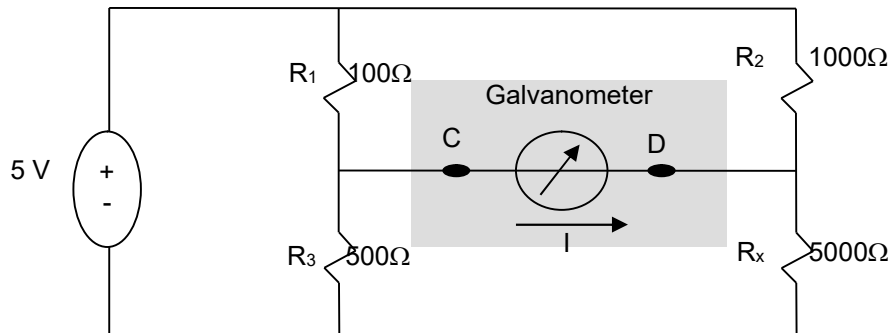*Hint: Find the Thevenin equivalent with respect to the galvanometer terminals when  $R_3=501\Omega$ . Note that once we have found this Thevenin equivalent, it is easy to find the amount of unbalanced current in the galvanometer branch for different galvanometer movements.*




**Solution:**

Given: Balanced  $I=0$  when  $R_3 = 500\Omega \rightarrow V_{CD} = 0$ ;  $R_g = 50\Omega$

Find:  $I$  if  $R = 501\Omega$

Step 1 – Find Thevenin Equivalent with respect to C and D

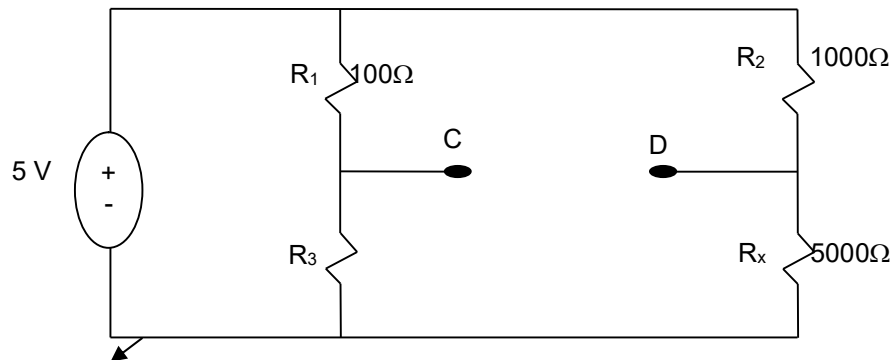A. Open CD and find  $V_{open\ CD} = V_{th}$




Use the voltage divider to find  $V_C$  and  $V_D$

$$V_C = 5 \cdot R_3 / (R_3 + 100)$$

$$V_D = 5 \cdot 5000 / (5000 + 1000) = 25/6$$


$$V_{th} = V_{CD} = V_C - V_D = 5 \cdot R_3 / (R_3 + 100) - 25/6$$

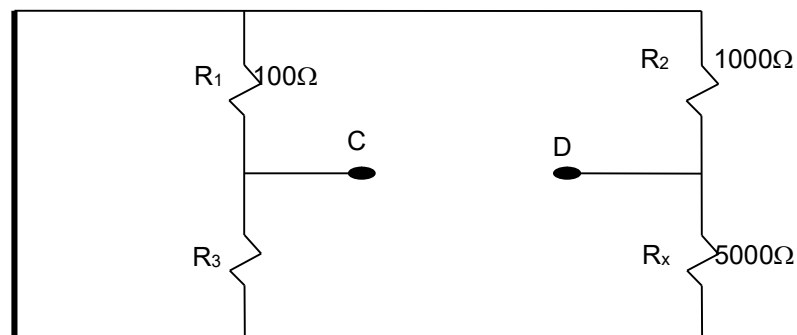B. Deactivate source ( $V=0$  short) and find  $R_{eq} = R_{th}$



$$R_{CD \text{ eq}} = R_{th} = (100 \parallel R_3) + (1000 \parallel 5000) = 100R_3/(100 + R_3) + 5000/6$$

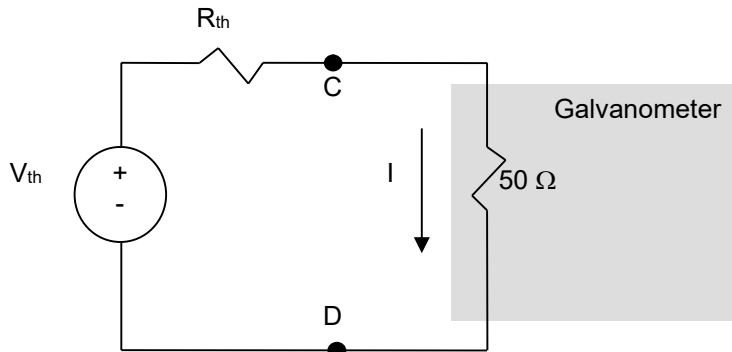
Step 2 – Use Thevenin Equivalent to find current through Galvanometer when  $R_3 = 501$



$$I = V_{th} / (R_{th} + 50) = (5 \cdot R_3 / (R_3 + 100) - 25/6) / ((5000/6 + 100R_3/(100 + R_3)) + 50) \text{ when } R_3 = 501$$


$$I = 1.43 \mu\text{A}$$

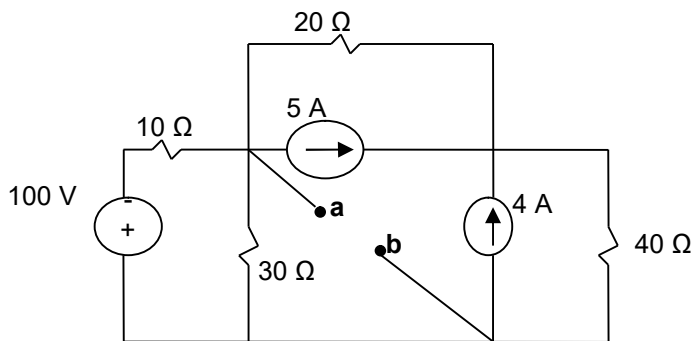11U. Draw and determine the value of components in the Thevenin Equivalent for the following circuit at terminals a and b.




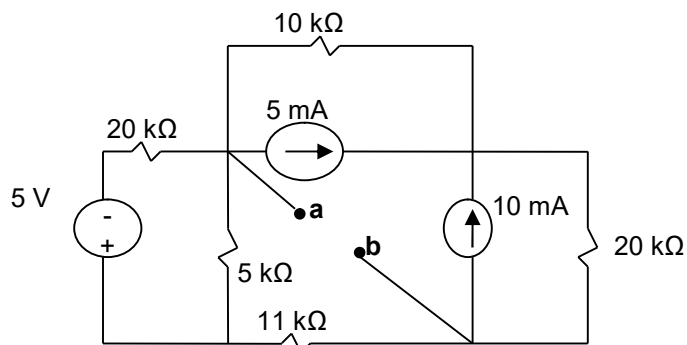
**Solution:**

11Sb. Draw and determine the value of components in the Thevenin Equivalent for the following circuit with respect to ab terminals. Use Superposition to find  $V_{th}$ .



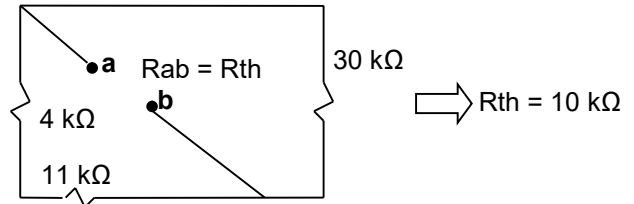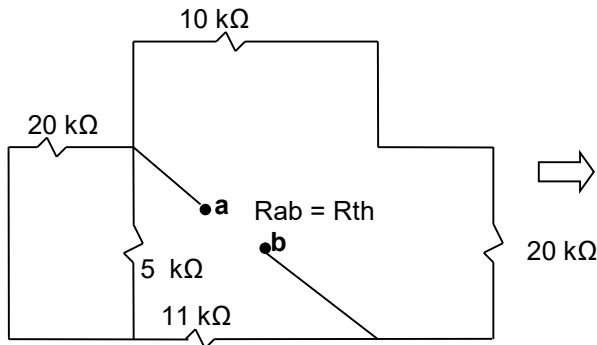**Solution:**



Since sources are all independent sources then deactivate all sources and find  $R_{th}$



Now find Open circuit voltage ( $V_{th}$ ):

Apply SuperPosition →



**Only 5V source is active:**

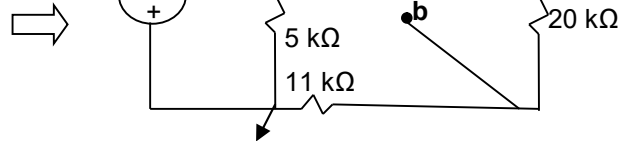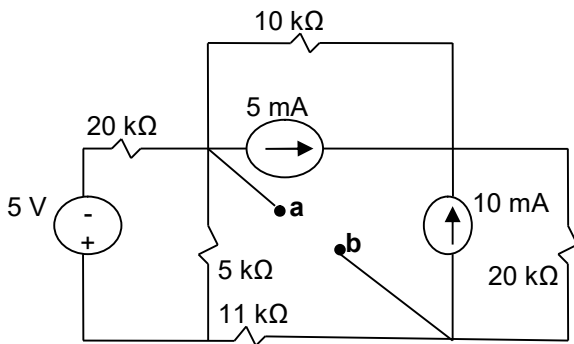

$$\begin{aligned} (V_a - (-5)) / 20 + (V_a - V_b) / 30 + V_a / 5 &= 0 & 17 V_a - 2 V_b &= -15 \\ (V_b - V_a) / 30 + V_b / 11 &= 0 & -11 V_a + 41 V_b &= 0 \end{aligned}$$

$V_a = -0.9, V_b = -0.2 \rightarrow V_{ab1} = -0.7 \text{ V for } 5\text{v Supply}$


**Only 5 mA source is active**

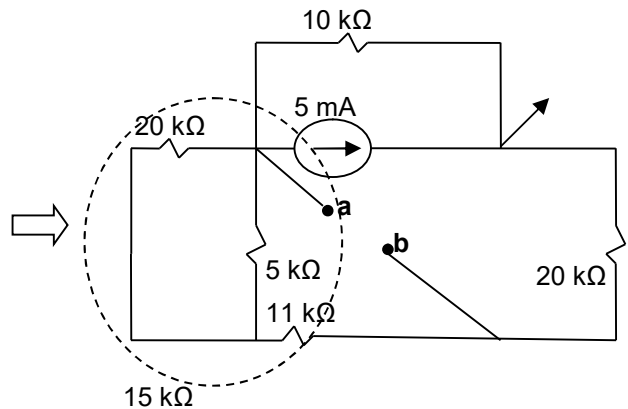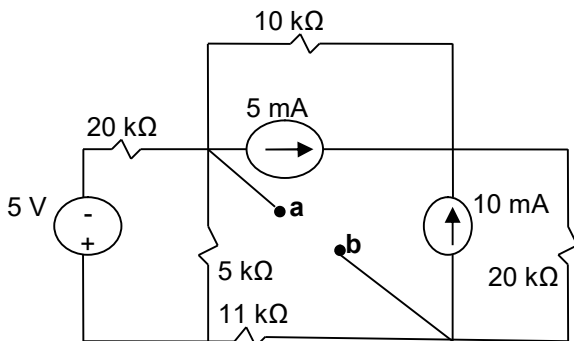

$$\begin{aligned} (V_a - V_b) / 15 + 5 + V_a / 10 &= 0 & \rightarrow 5 V_a - 2 V_b &= -150 \\ (V_b - V_a) / 15 + V_b / 20 &= 0 & \rightarrow -4 V_a + 7 V_b &= 0 \end{aligned}$$


Solve  $\rightarrow V_a = -38.9 \text{ \& } V_b = -22.2 \rightarrow V_{ab2} = (-38.9) - (-22.2) = -16.7 \text{ v}$

**Only 10 mA source is active**

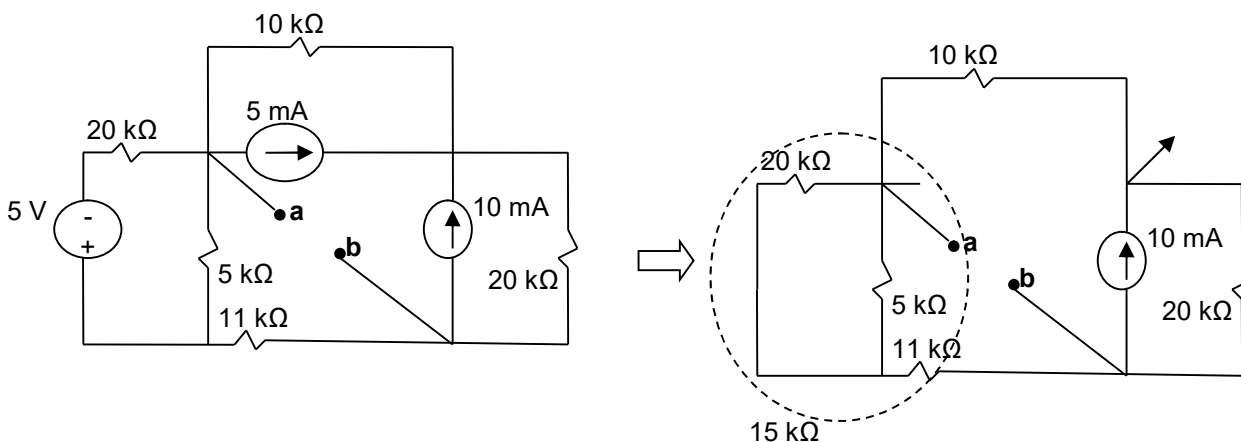


$$\begin{aligned} (V_a - V_b)/15 + V_a/10 &= 0 && \rightarrow 5V_a - 2V_b = 0 \\ (V_b - V_a)/15 + 10 + V_b/20 &= 0 && \rightarrow -4V_a + 7V_b = -600 \\ \text{Solve } \rightarrow V_a &= -44.4 \text{ \& } V_b = -111.1 && \rightarrow V_{ab3} = (-44.4) - (-111.1) = +66.7\text{v} \end{aligned}$$

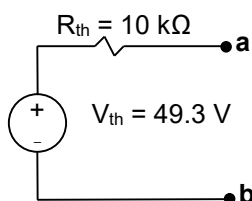Therefore  $V_{th} = V_{ab1} + V_{ab2} + V_{ab3} = -0.7 - 16.7 + 66.7 = 49.3\text{ v}$  and  $R_{th} = 10\text{ k}\Omega$



11Sc.

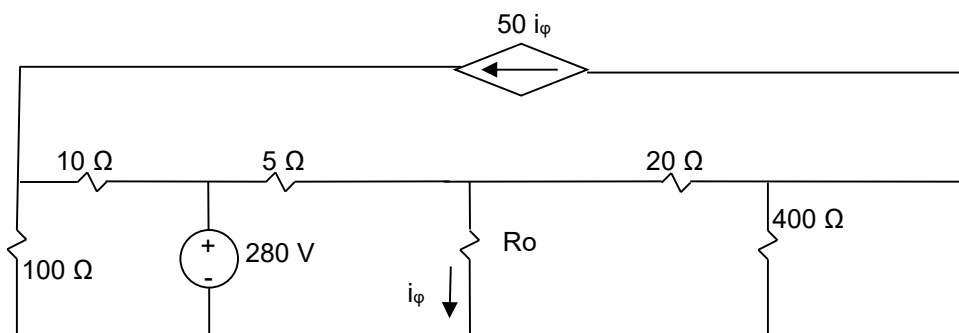


For the above circuit, find the Thevenin equivalent with respect to terminals of  $R_o$ .

**Solution:**

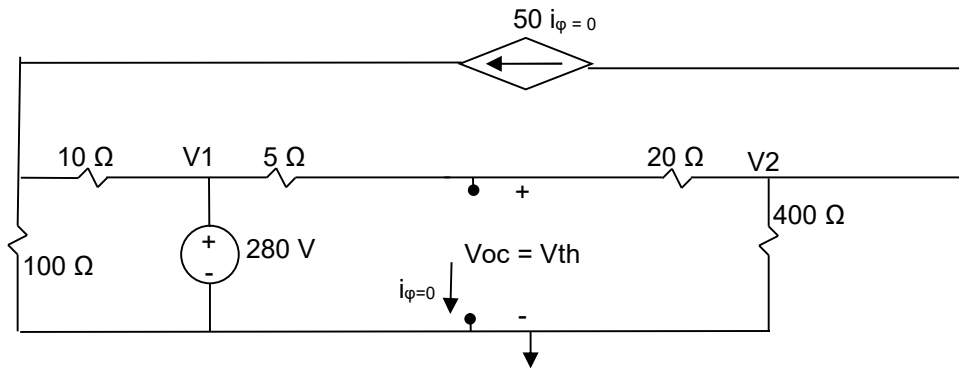a) Thevenin equivalent

Find  $V_{oc}$  (Open Circuit  $i_\phi=0$ )



From the circuit:


$$V1=280 \text{ V}$$

$$i_{\phi}=0$$

$$\text{KCL at } V2 \rightarrow (V2 - 280)/25 + V2/400 = 0 \rightarrow V2 = 264 \text{ V}$$

$$Voc = Vth = V1 - 5 \cdot (V1 - V2)/25 = 280 - 5 \cdot (280 - 264)/25 = 277 \text{ V}$$

Find Isc

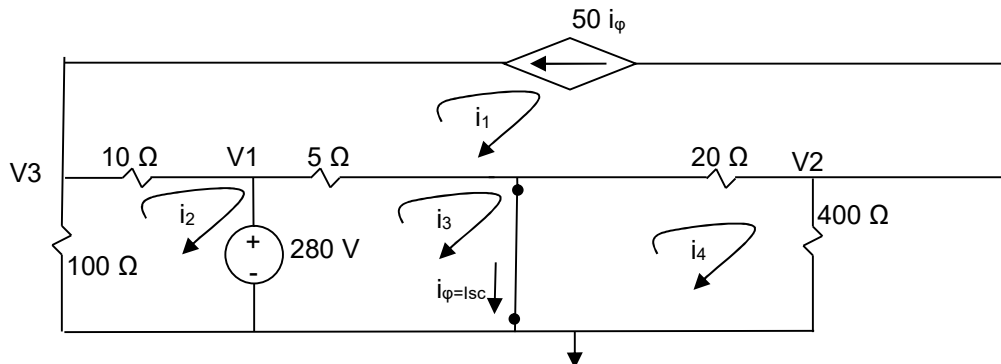

Mesh Current Analysis equations:

$$i_1 = -50 i_{\phi} = -50 (i_3 - i_4) = 50 i_4 - 50 i_3$$

$$+280 + 100 i_2 + 10 (i_2 - i_1) = 0$$

$$-280 + 5 (i_3 - i_1) = 0$$

$$20 (i_4 - i_1) + 400 i_4 = 0$$

Simplify to 4 equations and 4 unknowns:

$$i_1 + 50 i_3 - 50 i_4 = 0$$

$$-10 i_1 + 110 i_2 = -280$$


$$-5 i_1 + 5 i_3 = 280$$

$$-20 i_1 + 420 i_4 = 0$$

Solve the equations:


$$i_1 = -57.6 \text{ A}; i_2 = -7.8 \text{ A}; i_3 = -1.6; i_4 = -2.7; \rightarrow i_{sc} = i_3 - i_4 = -1.6 - (-2.7) = 1.1 \text{ A}$$
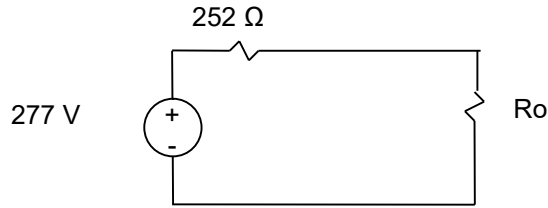
$$R_{th} = V_{oc} / I_{sc} = 277 / 1.1 = 252 \Omega$$



**11Sd.** Using Node-Voltage Method for the following circuit:

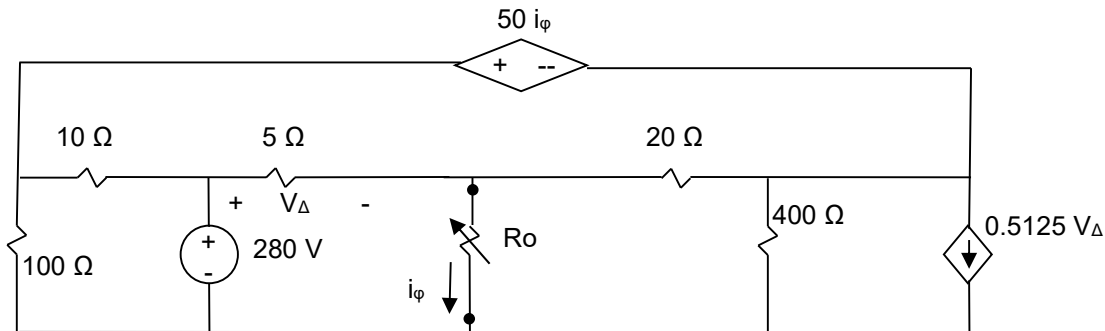
- Find the Thevenin equivalent with respect to terminals of  $R_o$ .
- Find the  $R_o$  value that results in maximum power delivery to  $R_o$ .



**Solution**

a) Thevenin equivalent

First find  $V_{oc}$

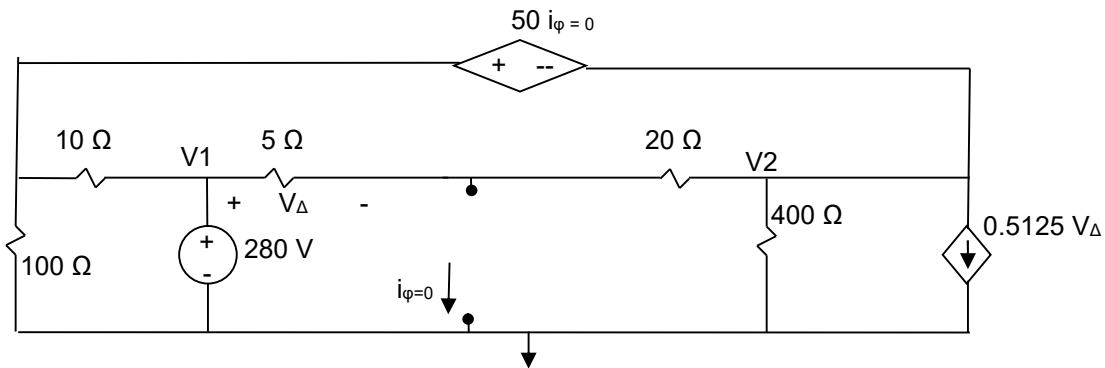

KCL at  $V_1 = 280$  V


$$\text{KCL at } V_2 \rightarrow (V_2 - 280)/25 + V_2/400 + (V_2 - 280)/10 + V_2/100 + 0.5125 V_\Delta = 0 \rightarrow V_2 = 257 \text{ V}$$

$$V_\Delta = (V_1 - V_2)/25 * 5 = (280 - 257)/5 = (280 - 257)/5 = 23/5 = 4.6 \text{ V}$$

$$V_\Delta = (280 - V_2)/5 = (280 - 257)/5 = 23/5 = 4.6 \text{ V}$$

$$V_{oc} = V_{th} = V_1 - V_\Delta = 275.4$$

First find  $I_{sc}$

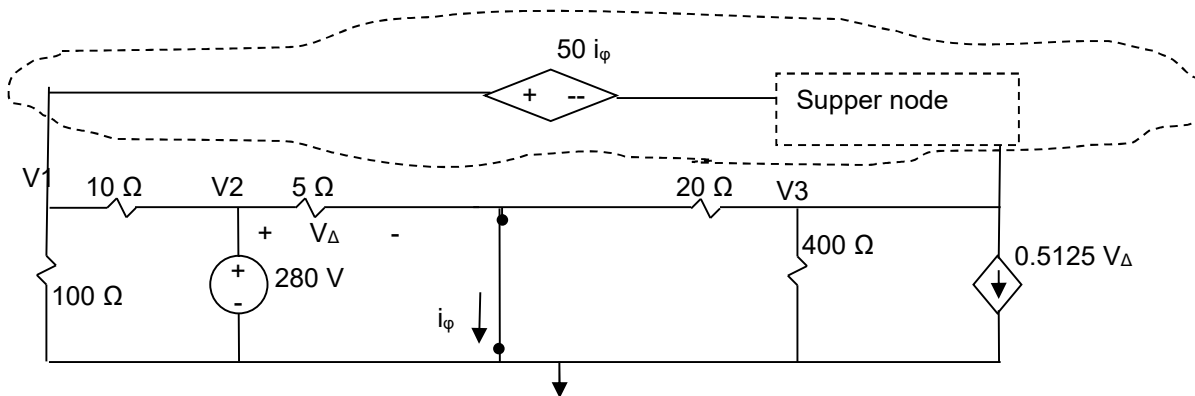

KCL at  $V_2=280\text{ V} \rightarrow V_2=V_\Delta=280\text{ V}$

$$i_\phi = (V_2) / 5 + (V_3) / 20$$

Supper Node Equation  $V_1 - V_3 = 50 i_\phi = (V_2) / 5 + (V_3) / 20 = 10 V_2 + 2.5 V_3 \rightarrow V_1 = 2800 + 3.5 V_3$

KCL at Supper Node  $\rightarrow V_3/400 + V_3/20 + 0.5125 V_\Delta + V_1/100 + (V_1 - V_2)/10 = 0$


Substitute known values  $\rightarrow$

$$V_3/400 + V_3/20 + 0.5125 * 280 + (2800 + 3.5 V_3)/100 + (2800 + 3.5 V_3 - 280)/10 = 0$$

Find  $V_3 = -945.14 \rightarrow V_1 = -508 \rightarrow I_{sc} = I_\phi = (V_1 - V_3)/50 = 8.7\text{ A}$


$$R_{th} = V_{oc} / I_{sc} = 275.4 / 8.7 = 31.65\ \Omega$$

$$V_{th} = V_{oc} = 266\text{ V}$$

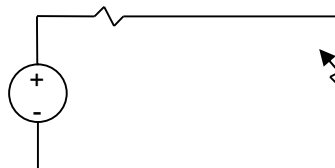

$R_o = R_{th}$  for Max Power

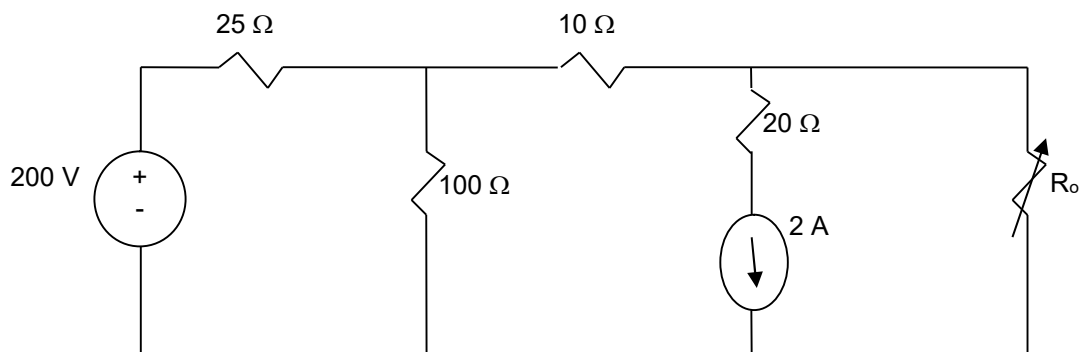
12S. The variable resistor ( $R_o$ ) in the following circuit is adjusted until the power dissipated in the resistor is 50 W. Find the values of  $R_o$  that satisfy this condition.



**Solution:**



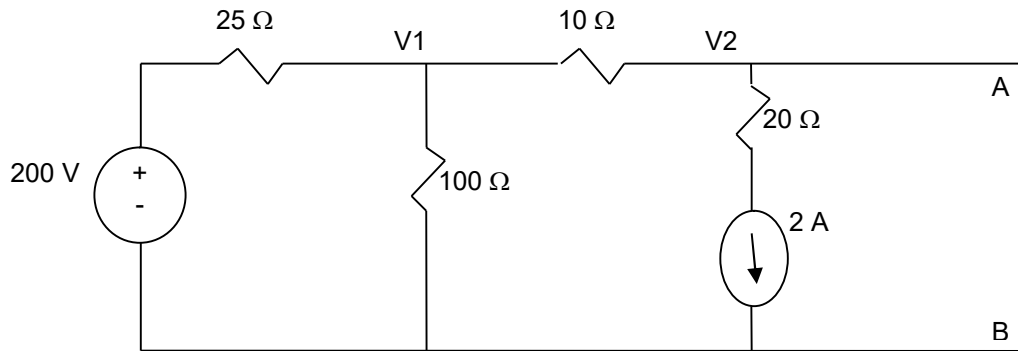1) Find Thevenin equivalent –  $V_{oc}=V_{th}$



$$\text{KCL at } V1 \rightarrow (V1 - 200)/25 + V1/100 + (V1 - V2)/10 = 0$$

$$\text{KCL at } V2 \rightarrow 2 + (V2 - V1)/10 = 0$$


→

$$15V1 - 10V2 = 800$$


$$V1 - V2 = 20$$

$$\rightarrow V_{th} = V_{oc} = V2 = 100 \text{ V}$$

2) Deactivate Sources to find  $R_{th}$

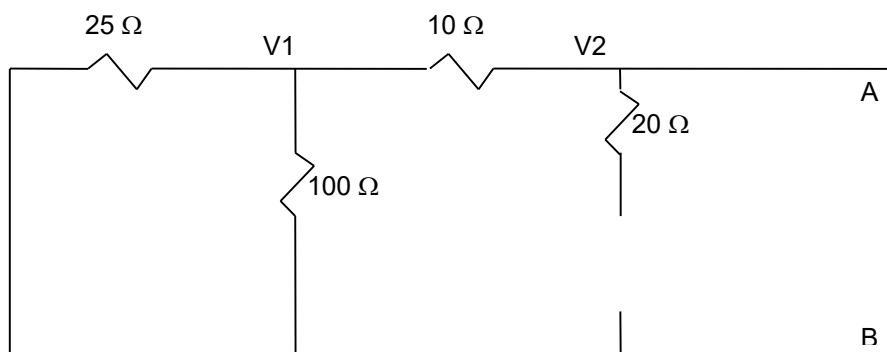
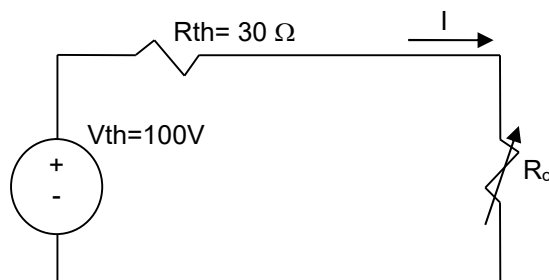
$$R_{th} = (25 \parallel 100) + 10 = 30 \Omega$$



$$P_{R_o} = 50 \text{ W} \rightarrow 50 = I^2 R_o \rightarrow R_o = 50/I^2$$

$$\text{KVL} \rightarrow -100 + 30I + I R_o = 0$$


$$\rightarrow -100 + 30I + 50/I = 0$$

$$\rightarrow 30I^2 - 100I + 50 = 0$$

$$I = \frac{100 \pm \sqrt{10,000 - 6,000}}{60} = 2.72 \text{ A} \quad \text{or} \quad 0.61 \text{ A}$$


$$R_o = 50/I^2 = 6.75 \Omega \quad \text{or} \quad 134.37 \Omega$$

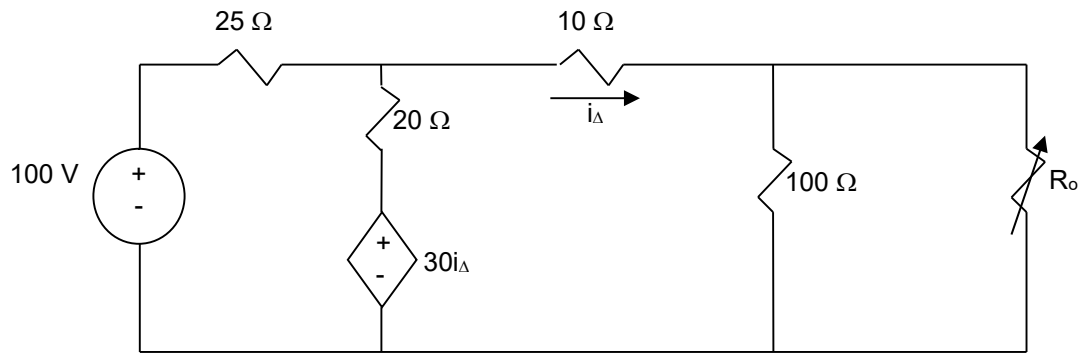12U. The variable resistor ( $R_o$ ) in the following circuit is adjusted until the power dissipated in the resistor is 25 W. Find the values of  $R_o$  that satisfy this condition.



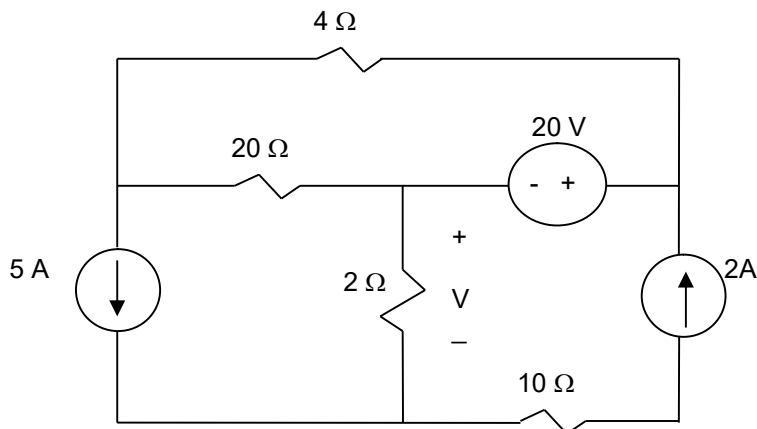
**Solution:**

13S. Use the principle of superposition to find the voltage  $v$  in the following circuit.




**Solution:**

1) Activate only 2A source

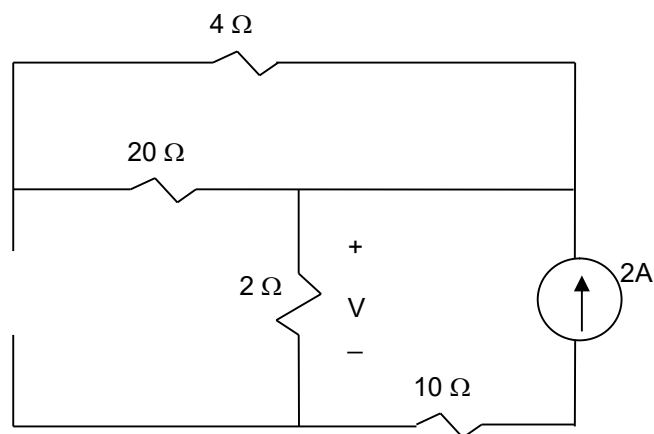


$$V_{2A} = 2 \times 2 = 4V$$

2) Activate only 5A source

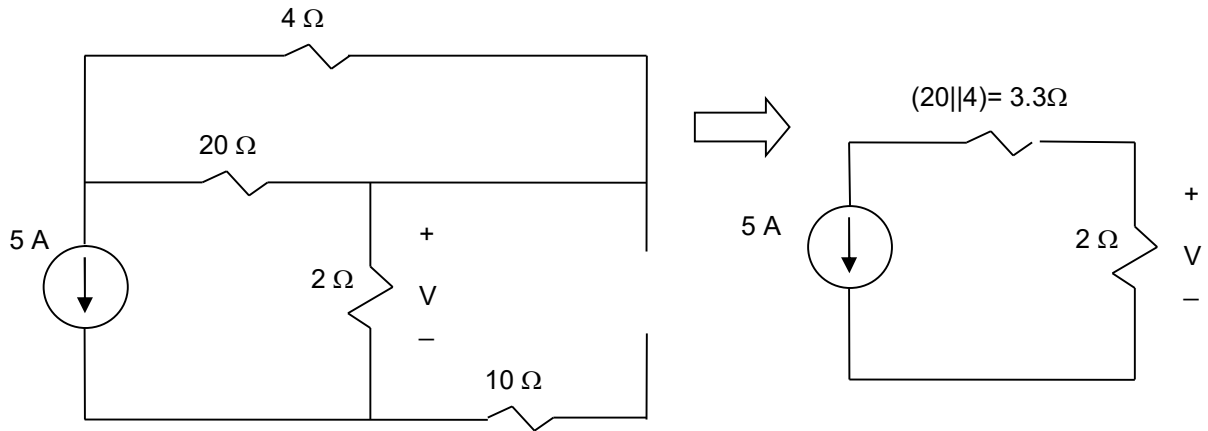

$$V_{5A} = -5 \times 2 = -10V$$


3) Activate only 20V source

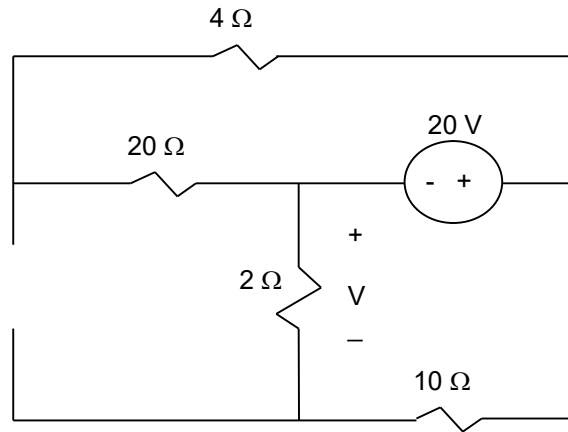

$$V_{20V} = -0$$


$$\text{Total response, } V = V_{2A} + V_{5A} + V_{20V} = 4 - 10 + 0 = -6V$$

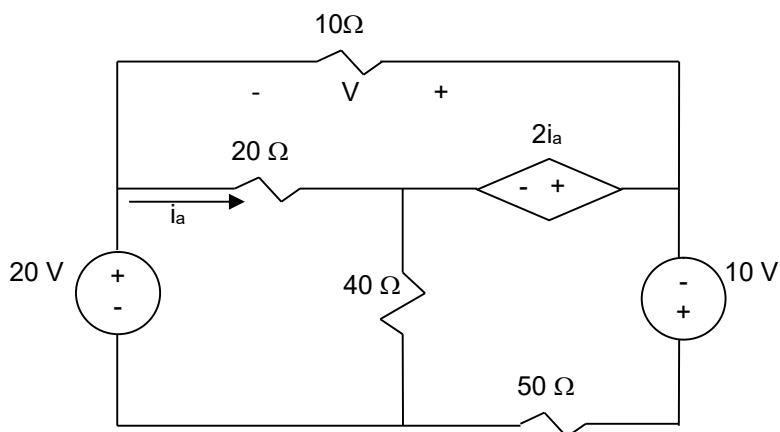13U. Use the principle of superposition to find the voltage  $V$  in the following circuit.



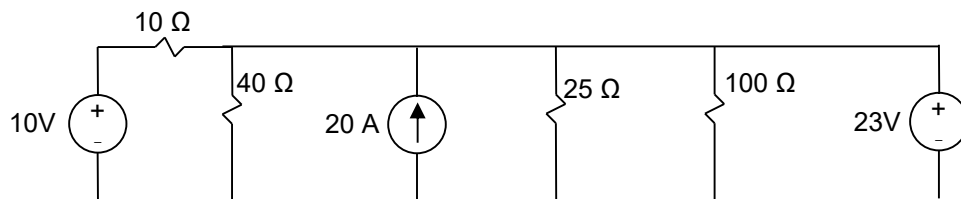
**Solution:**

13Sb. What is the value of current through  $40\ \Omega$  resistor that is directly attributable to the  $10\ \text{V}$  voltage source.




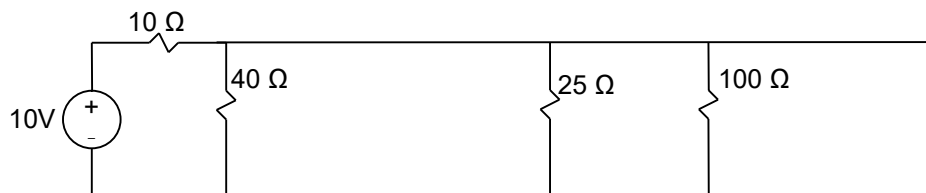**Solution:**

- De-activate all the sources except the 10v




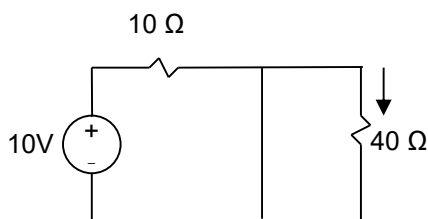- Simplify and find the current resulting from the 10v supply.



Current through the  $40\ \Omega$  is zero since all the current goes through the short.

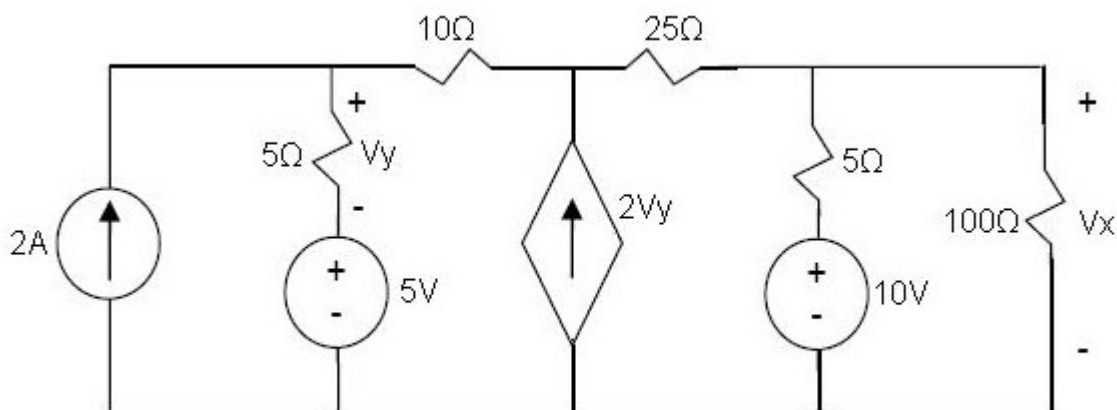
13Sc Use the Super-Position principle to find  $V_x$  in the following circuit.



**Solution:**

Deactivate all independent sources.

- 1) Activate 2A source and redraw:

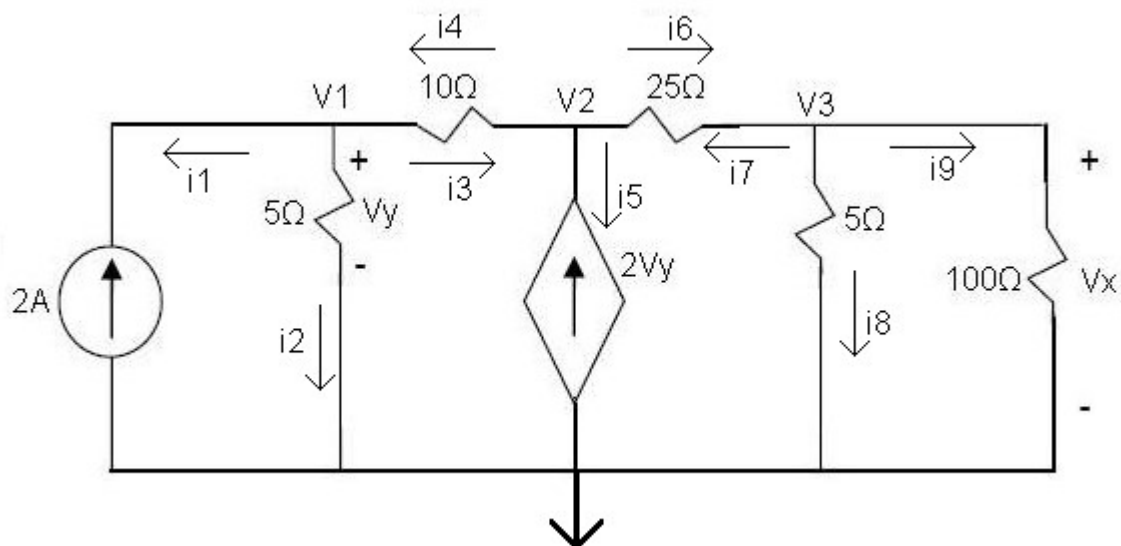

Use KCL to find  $V_x$ .

$$\text{KCL @ } V1 \rightarrow -2 + V1 / 5 + (V1 - V2) / 10 = 0$$


$$\text{KCL @ } V2 \rightarrow (V2 - V1) / 10 + (-2V_y) + (V2 - V3) / 25 = 0$$

$$\text{KCL @ } V3 \rightarrow (V3 - V2) / 25 + V3 / 5 + V3 / 100 = 0$$

$$\text{Dependent equation: } V_y = V1$$

$$V_x \leftarrow 2A = V3 = 0.4 \text{ V}$$

2) Activate 5V source and redraw:

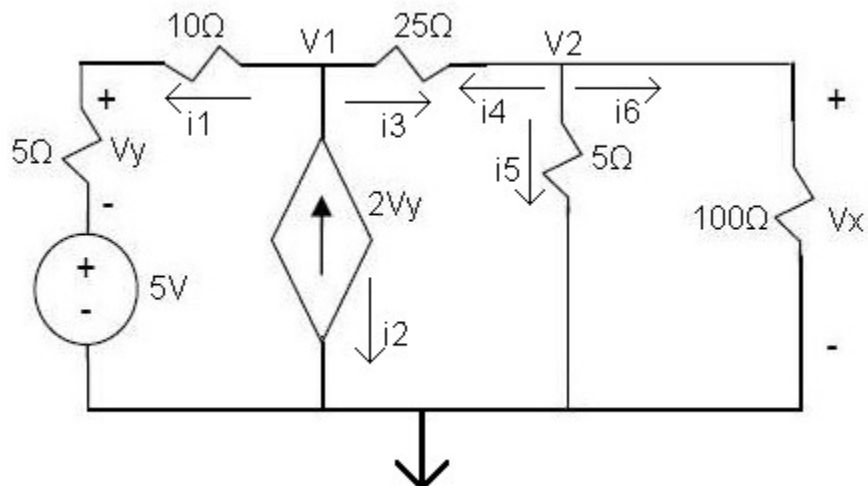

Use KCL to find  $V_x$ .


$$\text{KCL @ } V1 \rightarrow (V1 - 5) / (10 + 5) + (-2*V_y) + (V1 - V2) / 25 = 0$$

$$\text{KCL @ } V2 \rightarrow (V2 - V1) / 25 + V2 / 5 + V2 / 100 = 0$$

$$\text{Dependent equation: } V_y = (V1 - 5) / 3$$

$$V_x \leftarrow 5V = V2 = 0.7 \text{ V}$$

3) Activate 10V source and redraw:

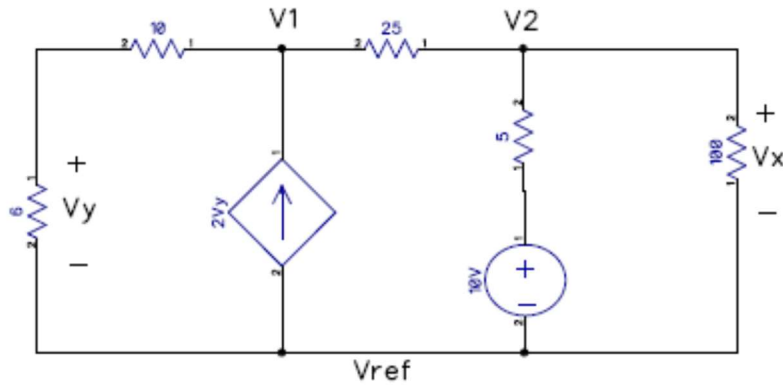


KCL @ V1  $\rightarrow V1/15 + (V1-V2)/25 - 2V_y = 0$   
 Dep. Source equation  $\rightarrow V_y = 5(V1/15) = V1/3$   
 KCL @ V2  $\rightarrow V2/100 + (V2-10)/5 + (V2-V1)/25 = 0$

$V_{x \leftarrow 10V} = 7.9 \text{ V}$

$V_{x \text{ total response}} = 0.4 + .7 + 7.9 = 9 \text{ V}$

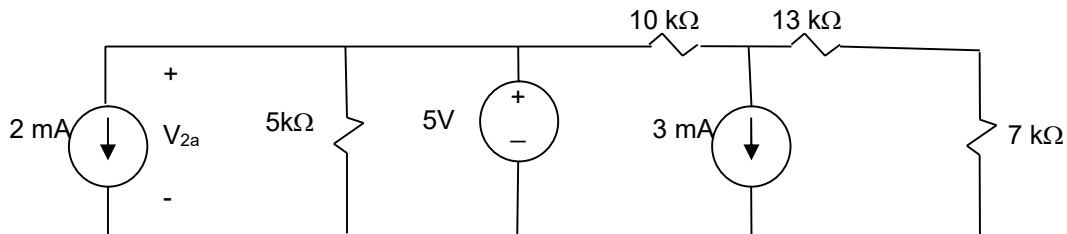
13Sc. Use the principle of superposition to find voltage  $V_{2a}$  in the following circuit:



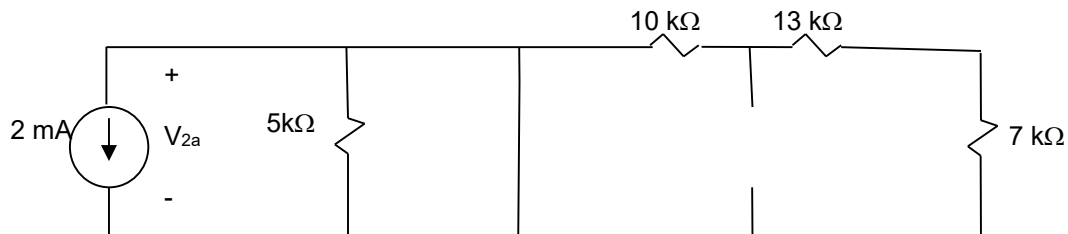**Solution:**


Deactivate all except 2 mA

Note: Voltage source deactivates when  $V=0 \rightarrow$  short; Current source deactivates when  $I=0 \rightarrow$  Open




$R_{eq} = 0 \text{ K}\Omega \rightarrow V_{2a} = 0 \text{ V}$

Deactivate all except 5V

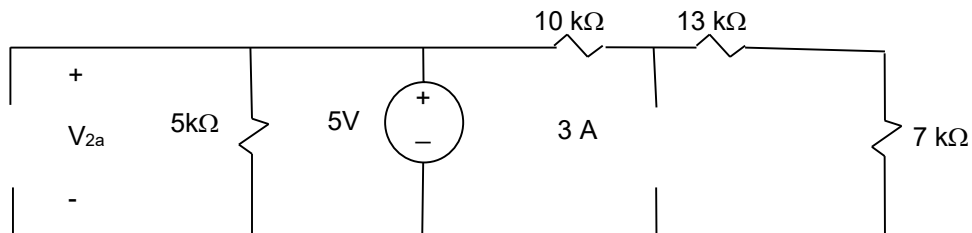

$V_{2a} = + 5 \text{ V}$


Deactivate all except 3 mA

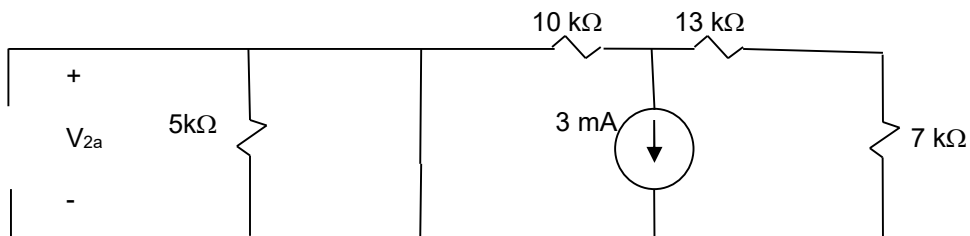

$$R_{eq} = 0 \text{ K}\Omega \rightarrow V_{2a} = 0 \text{ V}$$


Super positioned input (total Response) =  $0 + 5 + 0 = 5 \text{ V}$ .

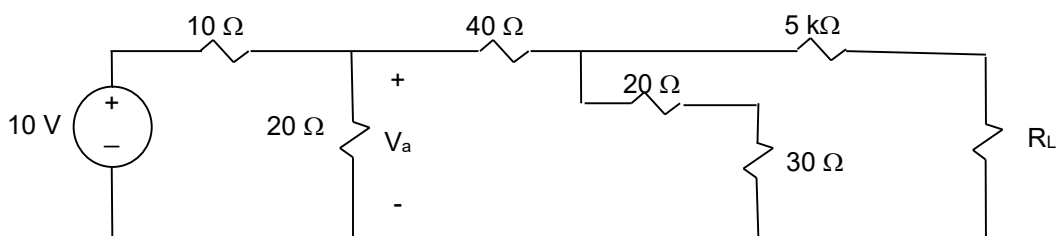14S. In the following circuit, find  $R_L$  value such that  $R_L$  consumes maximum power.



**Solution:**

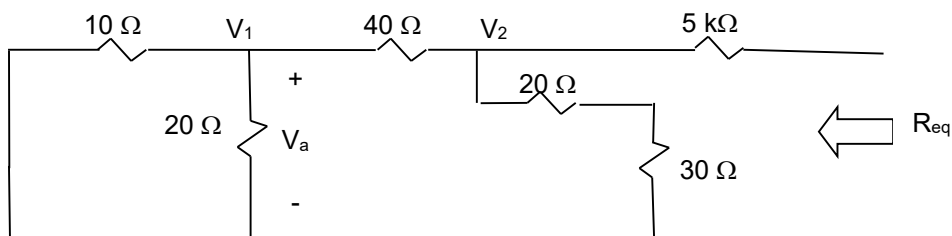
1) Find  $R_{th}$  by Deactivating source ( $v=0$  or open)



$$R_{eq} = (((10 \parallel 20) + 40) \parallel (20 + 30)) + 5000 = 5024.15 \text{ }\Omega$$

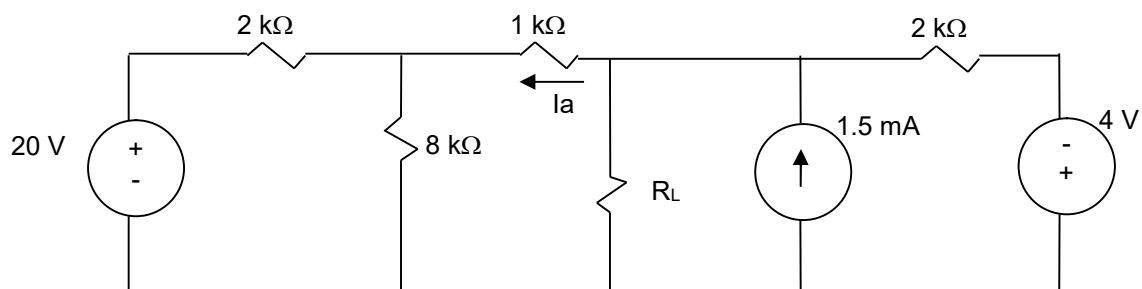2) Maximum power Requires  $R_L = R_{th} = 5024.15 \text{ }\Omega$


14U. In the following circuit, find  $R_L$  value such that  $R_L$  consumes maximum power..



*Hint: Find  $R_{th}$  with respect to  $R_L$  terminals First.*

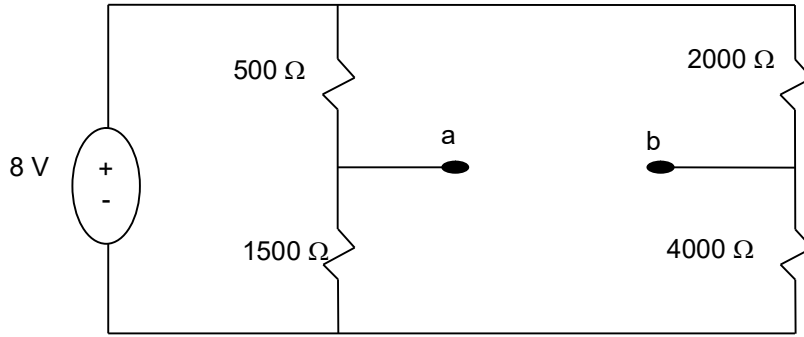
**Solution:**

14Sb. Find value of a resistor between terminals a and b such that it would consume maximum power:



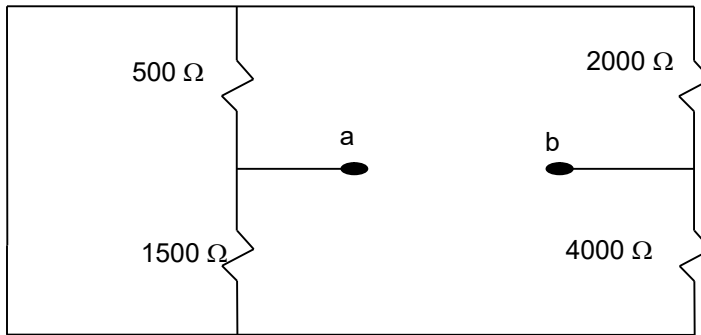**Solution:**

Find  $R_{th}$  with respect to terminals a and b by deactivating the independent voltage source



$$R_{th} = (500 \parallel 1500) + (2000 \parallel 4000) = 1708 \Omega$$

For Maximum power,  $R_{ab}$  must be equal to  $R_{th}$  or 1708 Ω