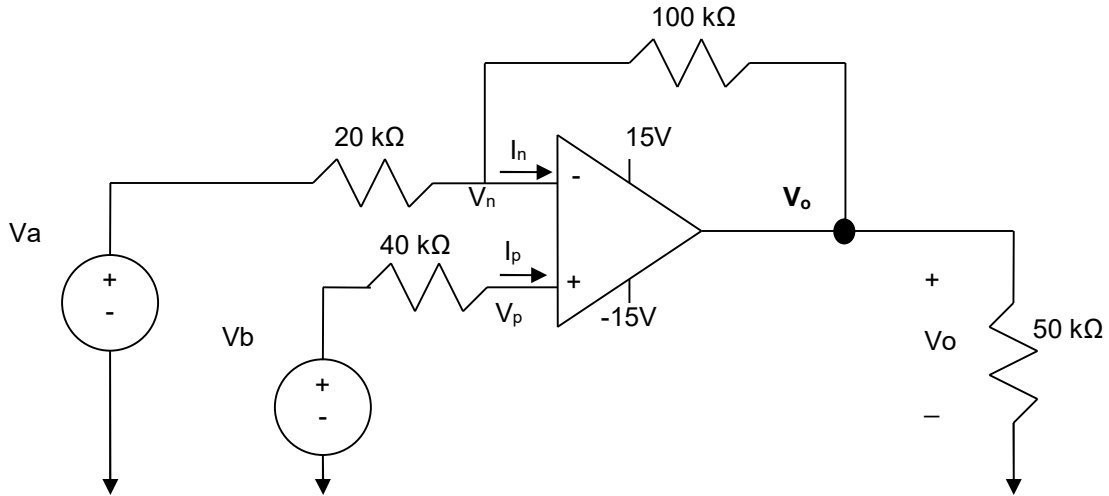


Fundamentals of Electrical Circuits - Chapter 5

1S. The Op Amp in the circuit shown below is ideal.

- Calculate V_o if $V_a = 4\text{ V}$ and $V_b = 0\text{ V}$.
- Calculate V_o if $V_a = 2\text{ V}$ and $V_b = 0\text{ V}$.
- Calculate V_o if $V_a = 2\text{ V}$ and $V_b = 1\text{ V}$.
- Calculate V_o if $V_a = 1\text{ V}$ and $V_b = 2\text{ V}$.
- If $V_b = 1.6\text{ V}$, specify the range of V_a such that the amplifier does not saturate.



Solution:

a, b, c and d)

$$\text{KCL at Node } V_n \rightarrow \frac{V_n - V_a}{20} + \frac{V_n - V_o}{100} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = V_b$$

$$\text{Apply to KCL equation} \rightarrow \frac{V_n - V_a}{20} + \frac{V_n - V_o}{100} = 0 \rightarrow \frac{V_b - V_a}{20} + \frac{V_b - V_o}{100} = 0$$

$$\rightarrow V_o = 6V_b - 5V_a$$

Use the above relationship to answer the problem parts a, b, c and d. Note that calculated value of V_o must be limited by the V_{CC} limits (-15 and +15)

Part	V_a (V)	V_b (V)	V_o (V)	Comment
a	4	0	-20	V_o will be limited to -15V due to saturation
b	2	0	-10	Linear Region
c	2	1	-4	Linear Region
d	1	2	7	Linear Region

e)


In order for the Op Amp not to saturate its output must satisfy $-15 \leq V_o \leq 15$
given $V_b = 1.6\text{ V}$

$$\rightarrow -15 \leq 6V_b - 5V_a \leq 15 \rightarrow -1.08 \leq V_a \leq 4.92$$

1U. The Op Amp in the circuit shown below is ideal.


- Calculate V_o if $V_a = 2\text{ mV}$ and $V_b = 0\text{ V}$.
- Calculate V_o if $V_a = 100\text{ mV}$ and $V_b = 20\text{ mV}$.

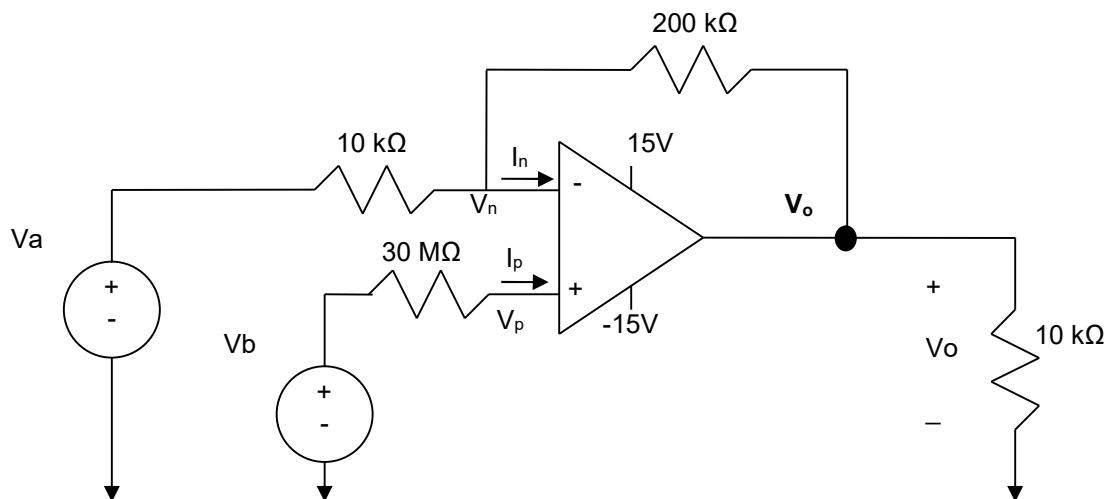- c) Calculate V_o if $V_a = 2\text{ V}$ and $V_b = 1\text{ V}$.
- d) Calculate V_o if $V_a = 2\text{ V}$ and $V_b = 2.1\text{ V}$.
- e) If $V_b = 1.2\text{ V}$, specify the range of V_a such that the amplifier does not saturate.




Solution:

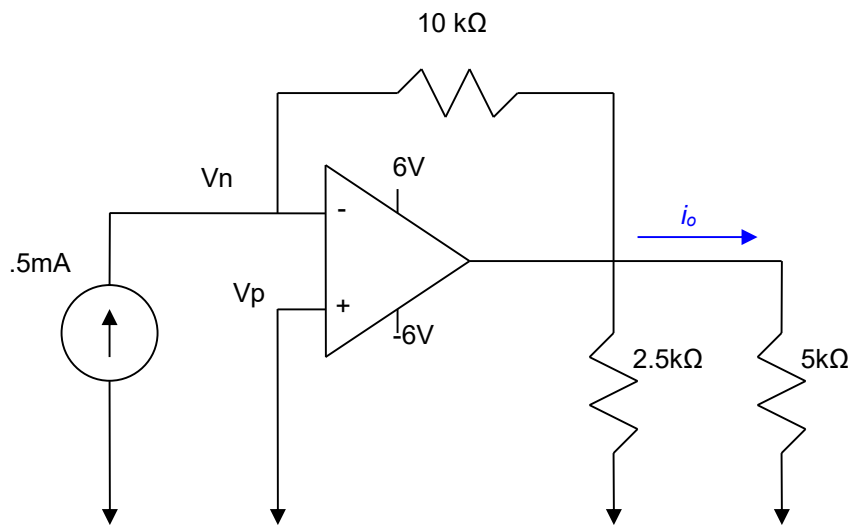2S. Find i_o in the following circuit if the Op Amp is ideal



Solution:

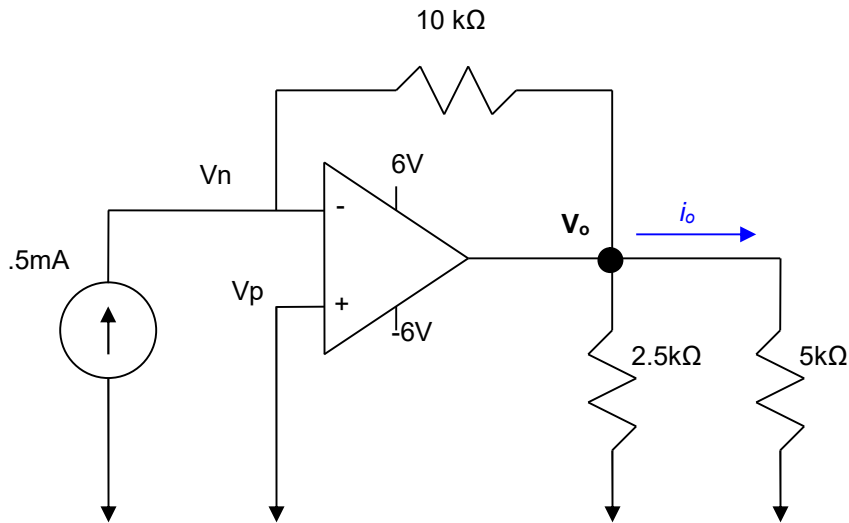


$$\text{KCL at Node } V_n \rightarrow -0.5 + \frac{V_n - V_o}{10} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 0$$

$$\text{Apply to KCL equation} \rightarrow V_o = -5 \text{ V}$$

$$\rightarrow I_\sigma = \frac{V_o}{R} = \frac{-5}{5} = -1 \text{ mA}$$

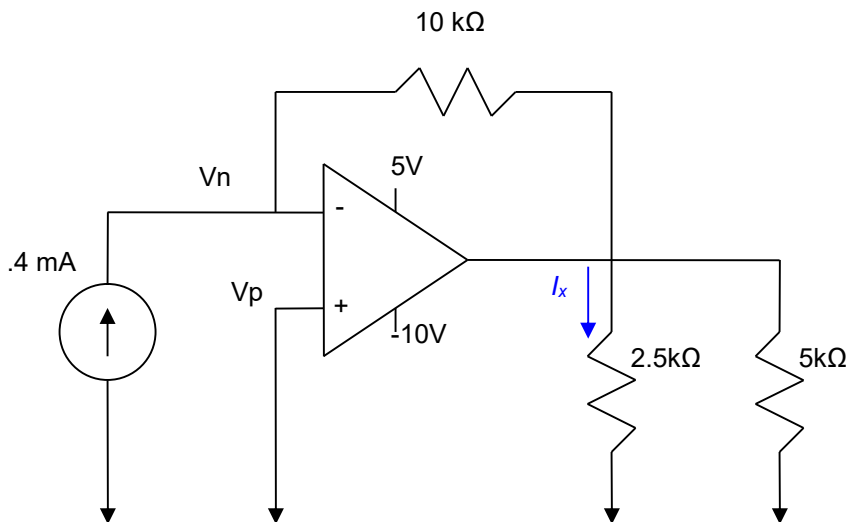
2U. Find I_x in the following circuit if the Op Amp is ideal



Solution:

3S. The Op Amp in the following circuit is ideal
a) What Op Amp circuit configuration is this?

b) Calculate V_o

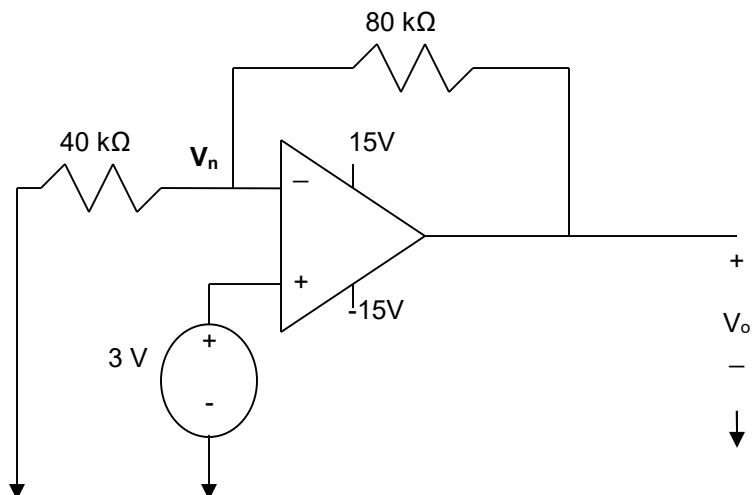

Solution:

a) non-Inverting amplifier – Source is connected to positive input terminal

b) $V_o = ?$

$$\text{KCL at Node } V_n \rightarrow \frac{V_n}{40} + \frac{V_n - V_o}{80} = 0$$


$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 3$$

$$\text{Apply to KCL equation} \rightarrow \frac{3}{40} + \frac{3 - V_o}{80} = 0 \rightarrow V_o = 9 \text{ V}$$

3U. The Op Amp in the following circuit is ideal

a) What Op Amp circuit configuration is this?

b) Calculate V_o

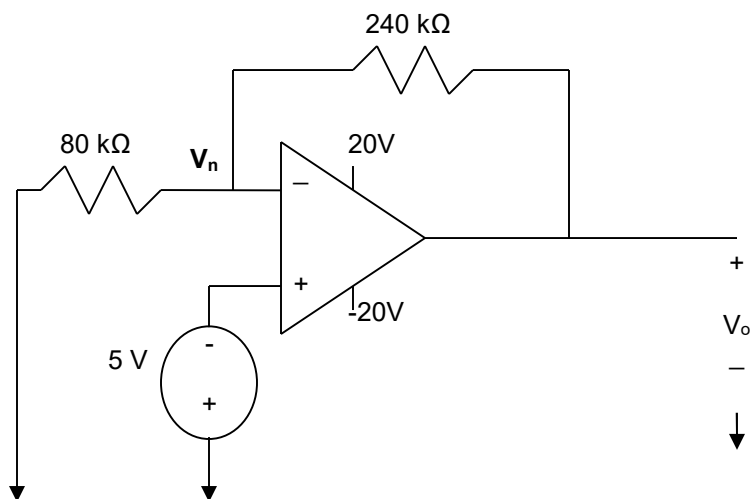

Solution:


4S. The Op Amp in the following figure is ideal.

a) What circuit configuration is shown in the figure?

b) Find V_o if $V_a = 1.2 \text{ V}$, $V_b = -1.5 \text{ V}$ and $V_c = 4 \text{ V}$.

c) The voltage V_a and V_c remain at 1.2 V and 4 V , respectively. What are the limits on V_b if the Op Amp

operates within its linear region?

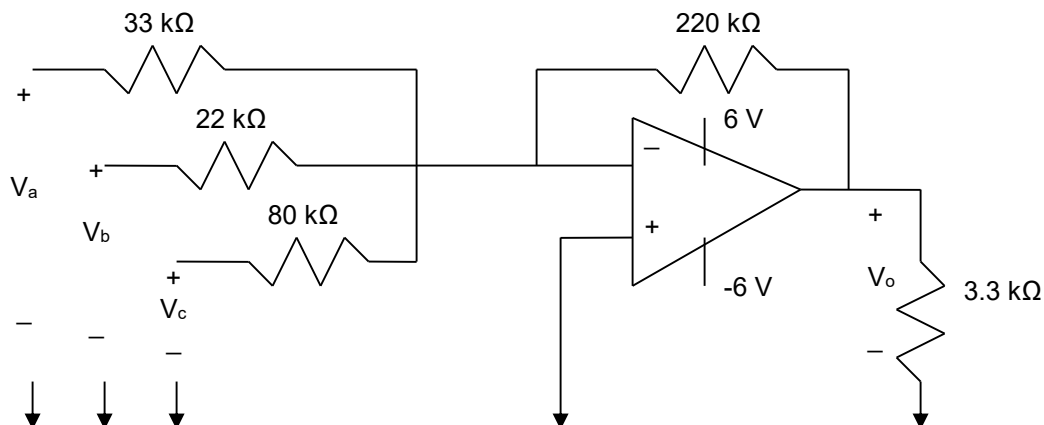

Solution:

a) Inverting summing amplifier – Multiple sources are connected to negative input terminal

b) Find Vo?

$$KCL \text{ at Node } V_n \rightarrow \frac{V_n - V_a}{33} + \frac{V_n - V_b}{22} + \frac{V_n - V_c}{80} + \frac{V_n - V_o}{220} = 0$$

$$Ideal \text{ Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 0$$

$$Apply \text{ to KCL equation} \rightarrow -\frac{V_a}{33} - \frac{V_b}{22} - \frac{V_c}{80} - \frac{V_o}{220} = 0 \rightarrow V_o = -220\left(\frac{V_a}{33} + \frac{V_b}{22} + \frac{V_c}{80}\right)$$

$$V_o = -4 \text{ V}$$

c) Limits of Vb if Va and Vc remain unchanged

We can rewrite Vo and set it to Vcc limit to ensure linearity

$$-6 \leq V_o \leq 6$$

$$-6 \leq -220\left(1.2/33 + V_b/22 + 4/80\right) \leq 6$$

$$-6 \leq -10V_b - 19 \leq 6$$


$$-2.5 \leq V_b \leq -1.3$$

4U. The Op Amp in the following figure is ideal.

a) What circuit configuration is shown in the figure?

b) Find Vo if Va = 2 V, Vb = -2 V and Vc = 4 V.

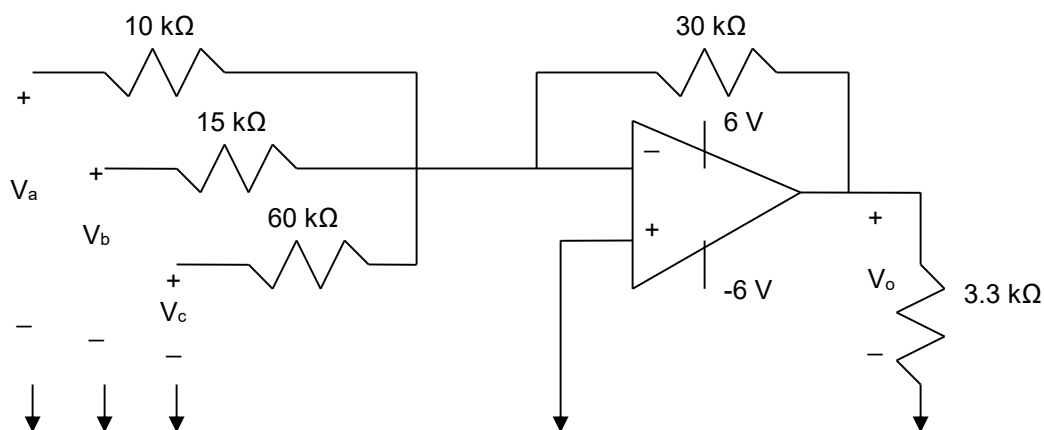
c) The voltage Va and Vc remain at 2 V and 4 V, respectively. What are the limits on Vb if the Op Amp operates within its linear region?



Solution:

4Sb.

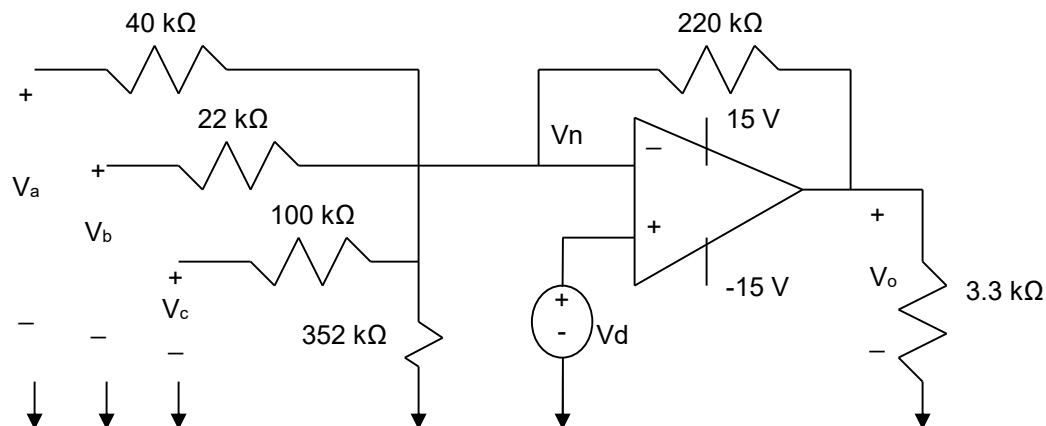- a) The Op Amp in the following circuit is ideal. Find V_o if $V_a=4V$, $V_b=9V$, $V_c=13V$ and $V_d=8V$.
 b) Assume V_b , V_c , V_d retain their values from part (a). Specify the range V_a such that the Op Amp operates within its linear region.



Solution:

- a) Find V_o where $V_a=4V$, $V_b=9V$, $V_c=13V$, $V_d=8V$

$$KCL \text{ at Node } V_n \rightarrow \frac{V_n - V_a}{40} + \frac{V_n - V_b}{22} + \frac{V_n - V_c}{100} + \frac{V_n}{352} + \frac{V_n - V_o}{220} = 0$$

$$Ideal \text{ Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 8$$

$$Apply \text{ to KCL equation} \rightarrow \frac{8-4}{40} + \frac{8-9}{22} + \frac{8-13}{100} + \frac{8}{352} + \frac{8-V_o}{220} = 0$$

$$V_o = 14V$$

- c) Range of V_a so Op Amp is in linear region if all else stay the same as (a)
 We can rewrite V_o in term of V_a and set it to V_{cc} limit to ensure linearity

$$\frac{8-V_a}{40} + \frac{8-9}{22} + \frac{8-13}{100} + \frac{8}{352} + \frac{8-V_o}{220} = 0$$


$$V_o = 36 - 5.5V_a$$

$$-15 \leq V_o = 36 - 5.5V_a \leq 15 \quad \text{for linearity}$$

$$3.8 \leq V_a \leq 9.3$$

5S. The Op Amp in the following circuit is ideal.

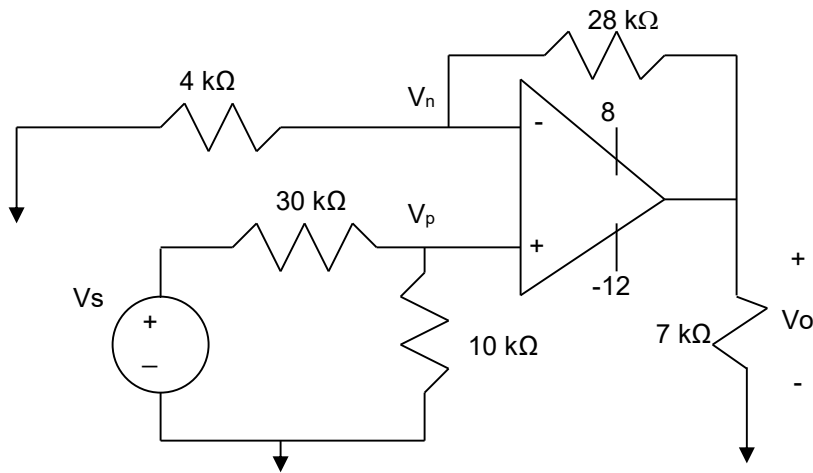- a) What Op Amp circuit configuration is this?
 b) Find V_o in term of V_s .
 c) Find the range of values for V_s such that V_o does not saturate and the Op Amp remains in its linear region of operation.



Solution:

a) Non-inverting, source is connected to positive input terminal

b) Find V_o in-terms of V_s

$$\text{KCL at Node } V_n \rightarrow \frac{V_n}{4} + \frac{V_n - V_o}{28} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p$$

$$\text{Voltage divider} \rightarrow V_p = \left(\frac{V_s}{30 + 10} \right) * 10 = \frac{V_s}{4} = V_n$$


$$\text{Apply to KCL equation} \rightarrow \frac{V_s}{16} + \frac{\frac{V_s}{4} - V_o}{28} = 0 \rightarrow V_o = 2 V_s$$

c) Range of V_s so Op Amp is in linear region (not saturated)

$$-12 \leq V_o = 2V_s \leq 8 \quad \text{for linearity}$$


$$-6 \leq V_s \leq 4$$

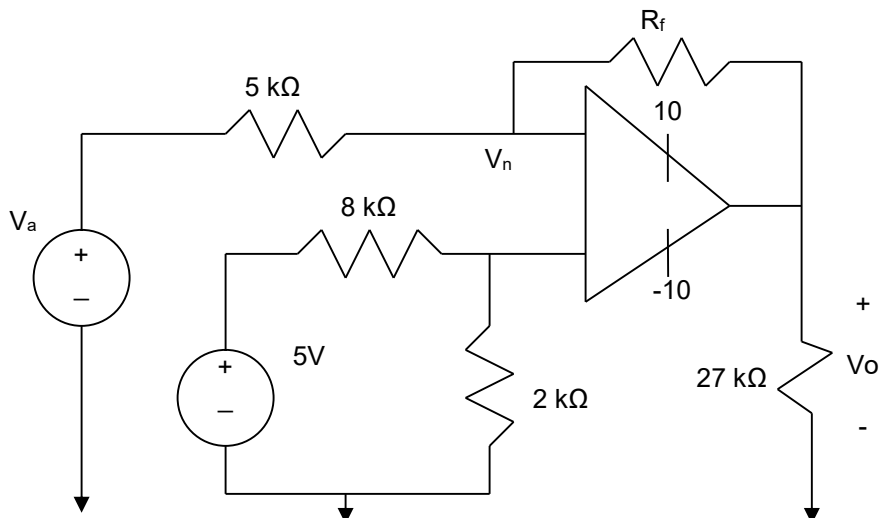5U. The Op Amp in the circuit shown below is ideal. What value of R_f will give the equation $\{V_o = 5 - 4V_a\}$ for this circuit.



Solution:

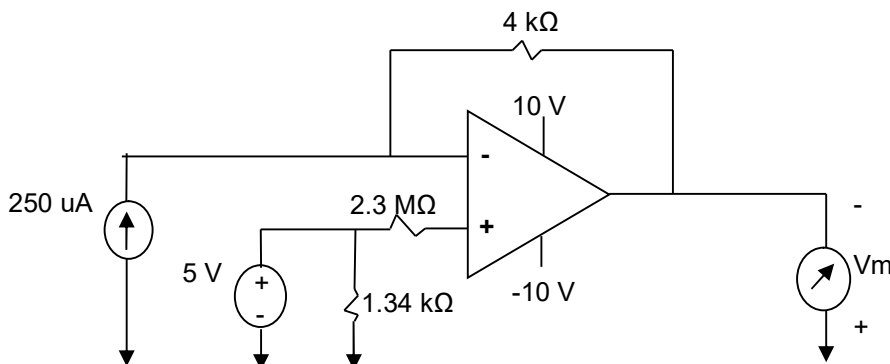6S. A voltmeter with a full-scale reading of 20 V and 10 MΩ internal resistances is used to measure the output voltage in the following circuit. Assuming the Op Amp is ideal, what is the reading of the voltmeter (Vm)?



Solution:


KCL at $V_n \rightarrow -250 \times 10^{-6} + (V_n - (-V_m))/4000 + I_n = 0$
 Ideal Op Amp $\rightarrow I_n = I_p = 0; V_n = V_p = 5V$.

Combine the above two equations
 $-250 \times 10^{-6} + (5 + V_m)/4000 + 0 = 0 \rightarrow V_m = -4 V$

Voltmeter Reads -4 V.

6U. Suppose the strain gage resistors in the bridge shown in following figure have the value of $120 \Omega \pm 1\%$ ($\Delta R = 1.2 \Omega$). The power supplies to the Op Amp $\pm 10 V$, and the reference voltage, V_{ref} , is taken from the positive power supply.

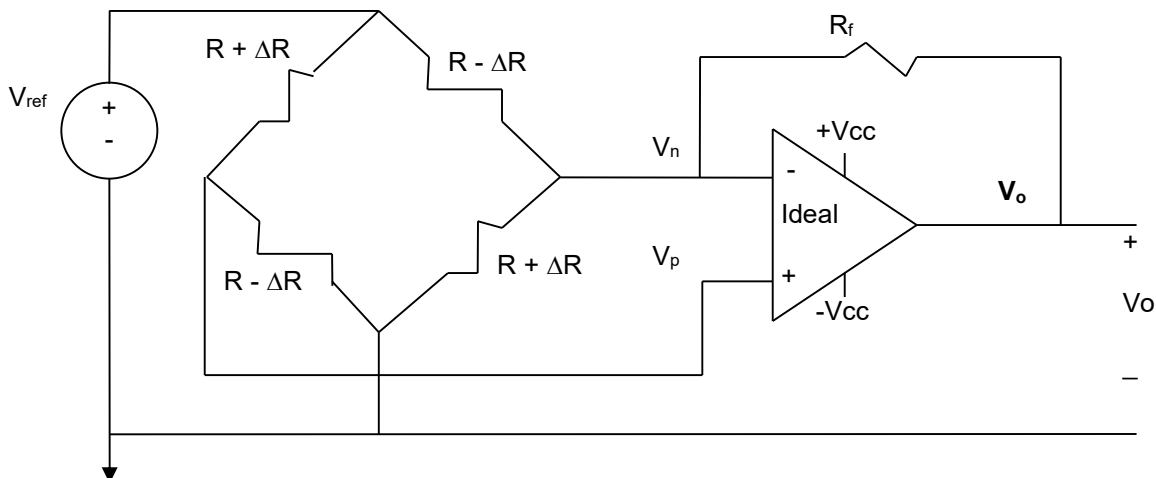- a) Calculate the value of R_f so that when the strain gage that is lengthening reaches its maximum length, the output voltage is -5 V.
- b) Suppose that we can accurately measure 50 mV changes in the output voltage. What change in strain gage resistance can be detected in milliohms?



Solution:


6Sb. Strain gage (SG) resistance is 350 ohms and is layed out on flat surface about 18 mm long SG's resistance increases by 10% when stretched by 1 mm and conversely, its resistance decreases by 10% when shrunk by 1 mm. Two SGs are attached to left and right side of a column at point of deflection.

a) Design a circuit using resistors, 12 v battery, Op Amps (Ideal), LEDs and SGs to turn on a red LED when the column is bending to the right and turn the green LED when the column is bending to the left.


b) For the the designed circuit, calculate V_{og} (Voltage at the Green LED) and V_{or} (Voltage at the Red LED) when the column is deflect at point of SG attachment by 1 mm.

Solution:

One Possible solution:

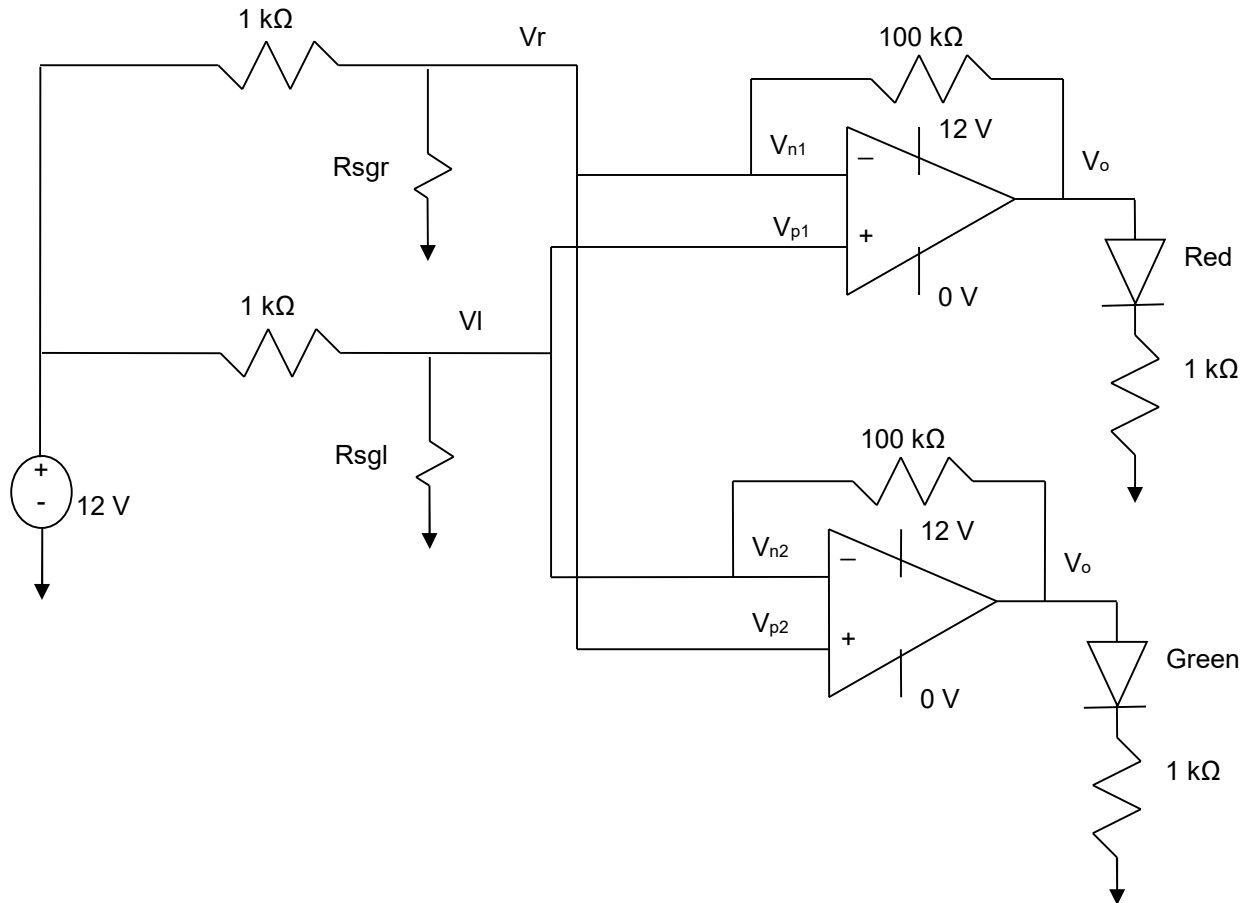

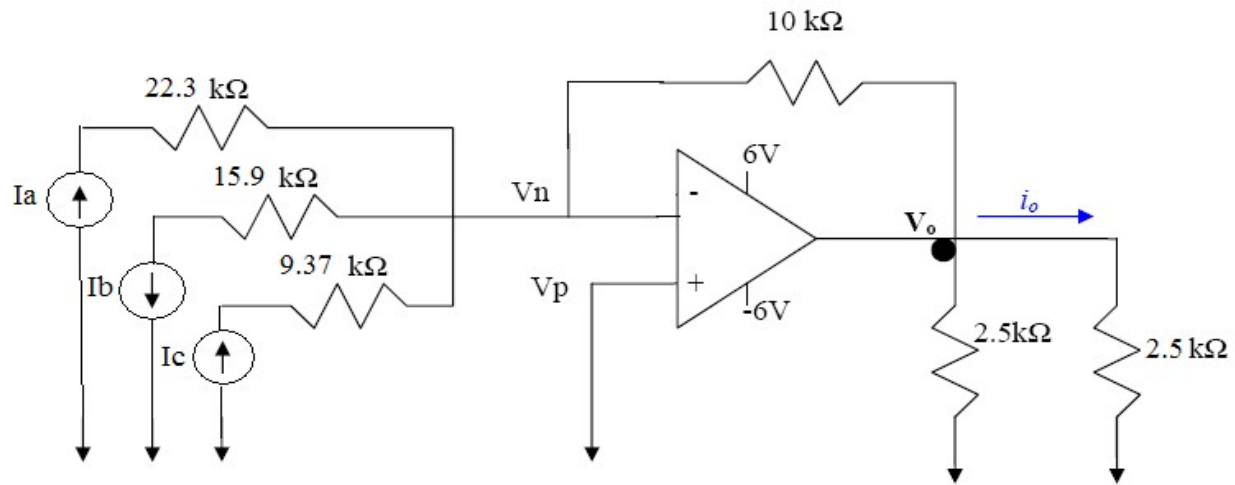6Sc. Find i_o in the following circuit. Assume an Ideal Op Amp. Current at $I_a = 0.55\text{mA}$, at $I_b = 0.75\text{mA}$, and at $I_c = 0.25\text{mA}$.




Solution:

KCL @ V_n $-0.55 + 0.75 - 0.25 + (V_n - V_o)/10 = 0$
 Ideal Op Amp states: $I_n = I_p = 0$ & $V_n = V_p = 0$
 $-0.05 = V_o/10$
 $V_o = -0.5 \text{ V}$

$I_o = V_o/R = -0.5/2.5 = -1/5 = -0.20 \text{ mA}$

7S. For the following circuit and using ideal OpAmp Model:

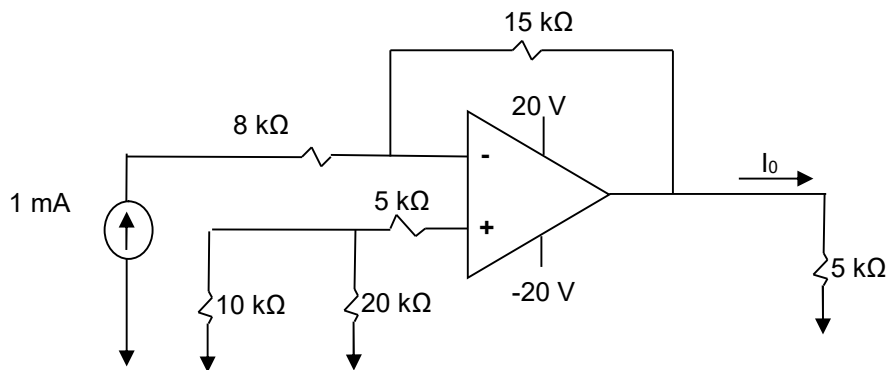- What Op Amp configuration is this?
- Find i_o .



Solution:

a) The circuit is an inverting amplifier, because the source is connected to the negative input terminal.


b) KCL at V_n : $-1 + (V_n - V_o)/15 + I_n = 0$

Apply Ideal Op Amp: $I_p = I_n = 0$ and $V_n = V_p = 0$

So, $-V_o/15 = 1 \rightarrow V_o = -15\text{V}$


Now, $I_o = V_o/5 = -15/5 \rightarrow \underline{I_o = -3\text{mA}}$

7U. Find V_o assuming an Ideal Op Amp.

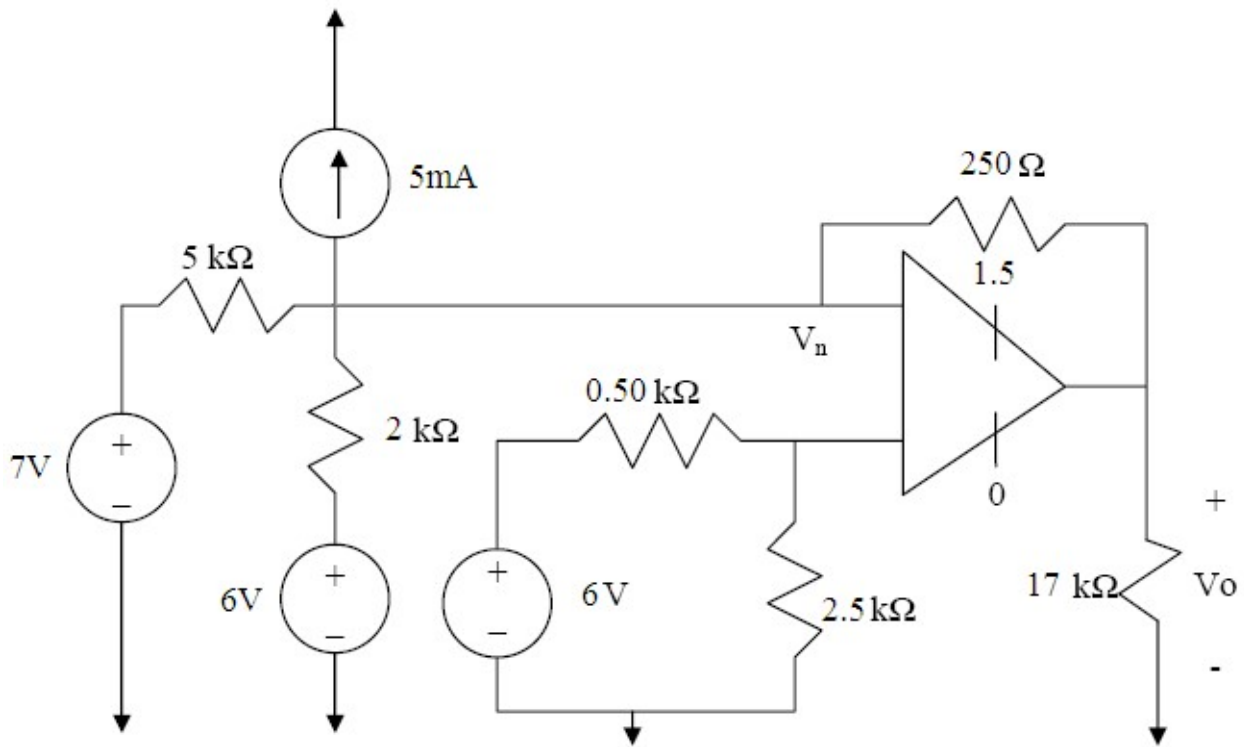

Solution:

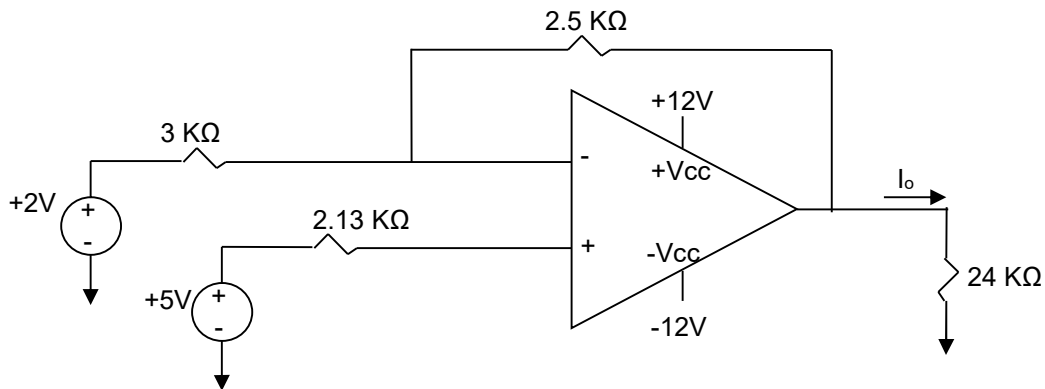7Sc. Calculate the value of I_o for the difference-amplifier circuit shown below (Idea Op Amp).




Solution:

$$\text{KCL @ } V_n \rightarrow \frac{V_n - 2}{3} + \frac{V_n - V_o}{2.5} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \text{ \& } V_n = V_p = 5$$

Therefore: $\frac{5-2}{3} + \frac{5-V_o}{2.5} = 0 \rightarrow V_o = 7.5 \rightarrow I_o = V_o / 24 \text{ K} = 0.3125 \text{ mA}$

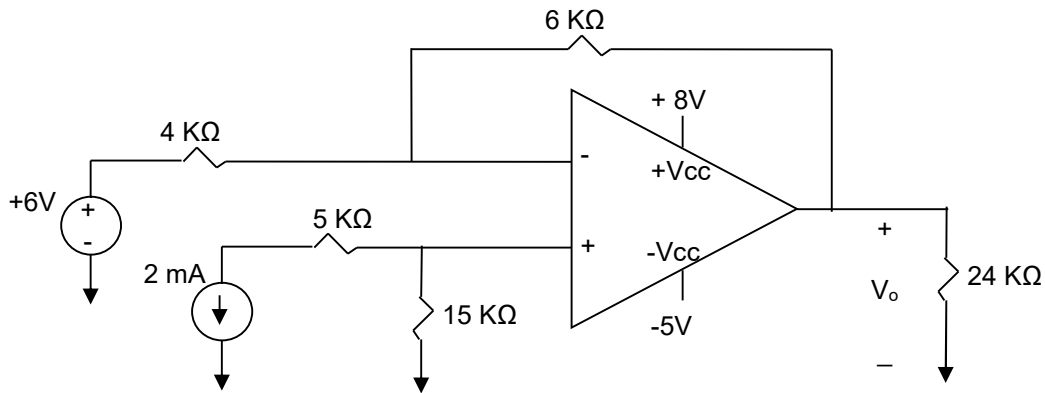7Sd. Calculate the value of V_o for the difference-amplifier circuit shown below (Using Ideal OpAmp Model):



Solution

KCL @ $V_n \rightarrow \frac{V_n - 6}{4} + \frac{V_n - V_o}{6} = 0$


Ideal Op Amp $\rightarrow I_p = 0, I_n = 0$ & $V_p = V_n \rightarrow V_p = -15 \times 2 = -30 \text{ V}$

Therefore: $\frac{-30 - 6}{4} + \frac{-30 - V_o}{6} = 0 \rightarrow V_o = -84 \text{ V}$

The OpAmp saturates at $-5 \text{ V} \rightarrow V_o = -5 \text{ V}$

7Se. In the following circuit, using ideal Op Amp model:

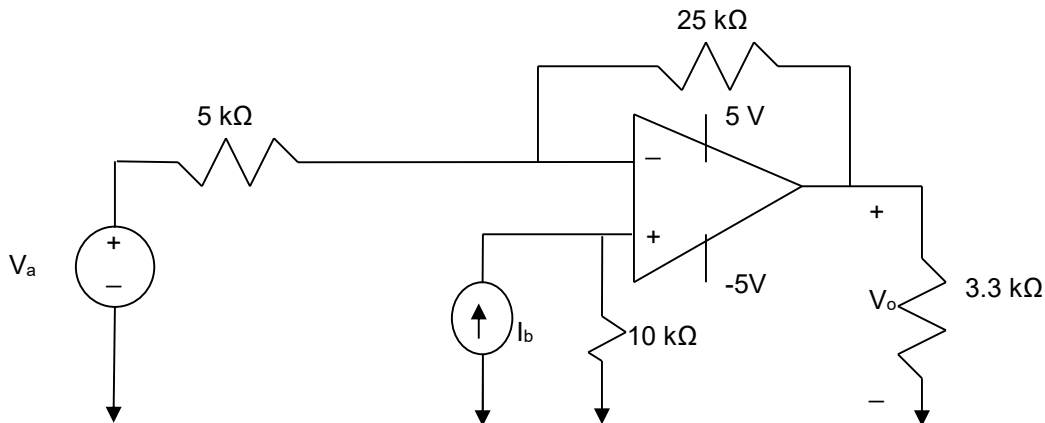- a) Find V_o in terms of V_a and I_b
- b) Calculate V_o for $V_a = 0.1 \text{ V}$ and $I_b = 2 \text{ mA}$




Solution:

a) KCL at $V_n \rightarrow (V_n - V_a)/5000 + (V_n - V_o)/25000 = 0$
 $V_n = V_p = 10000I_b$


$(10000 I_b - V_a)/5000 + (10000 I_b - V_o)/25000 = 0 \rightarrow V_o = 60000I_b - 5V_a$

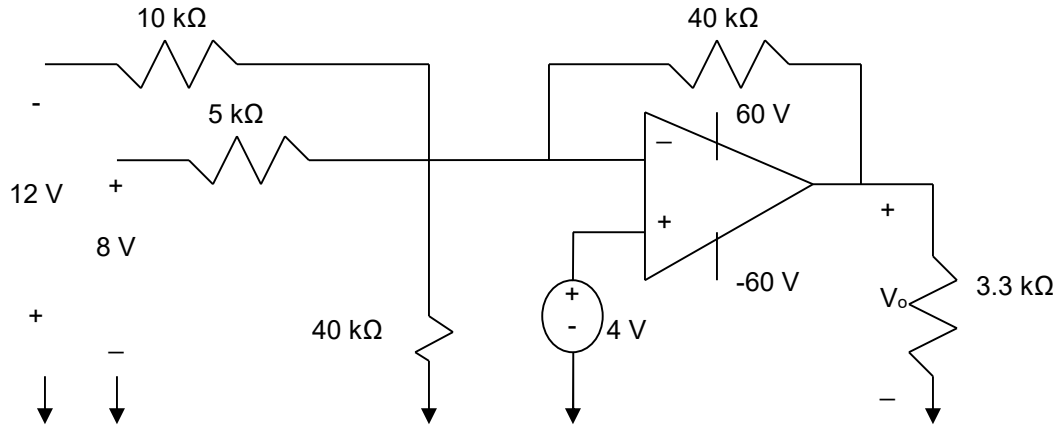b) $V_o = 5 \text{ V}$ (limited by the rail – saturated)

7Sf. For the following Op Amp circuit, Find V_o using an Ideal op Amp model.



Solution:

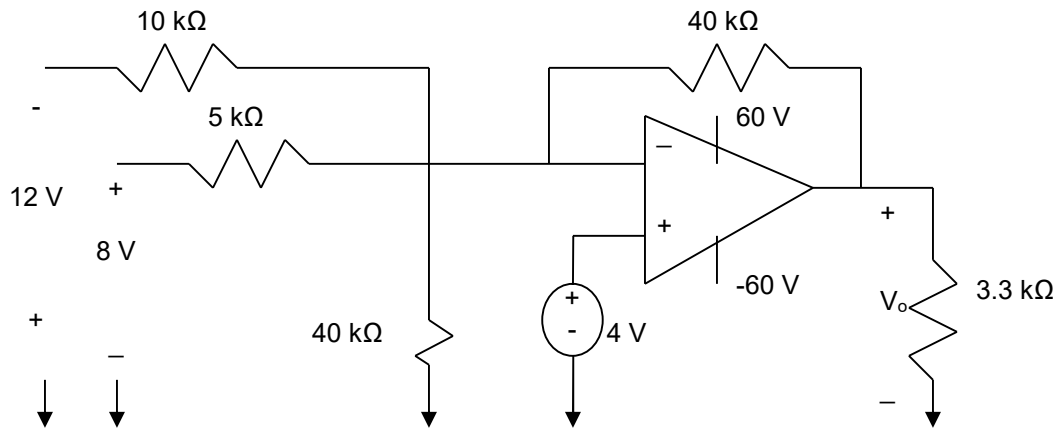

$$\text{KCL at Node } V_n \rightarrow \frac{V_n + 12}{10} + \frac{V_n - 8}{5} + \frac{V_n}{40} + \frac{V_n - V_o}{40} = 0$$

$$\text{Ideal Op Amp} \rightarrow I_p = I_n = 0 \rightarrow V_n = V_p = 4$$

$$\text{Apply to KCL equation} \rightarrow \frac{4 + 12}{10} + \frac{4 - 8}{5} + \frac{4}{40} + \frac{4 - V_o}{40} = 0$$


$$V_o = 40 \text{ V}$$

The output within the rail voltages...

8S. In the difference amplifier shown below, compute

- the differential mode gain
- the common mode gain

c) the CMRR

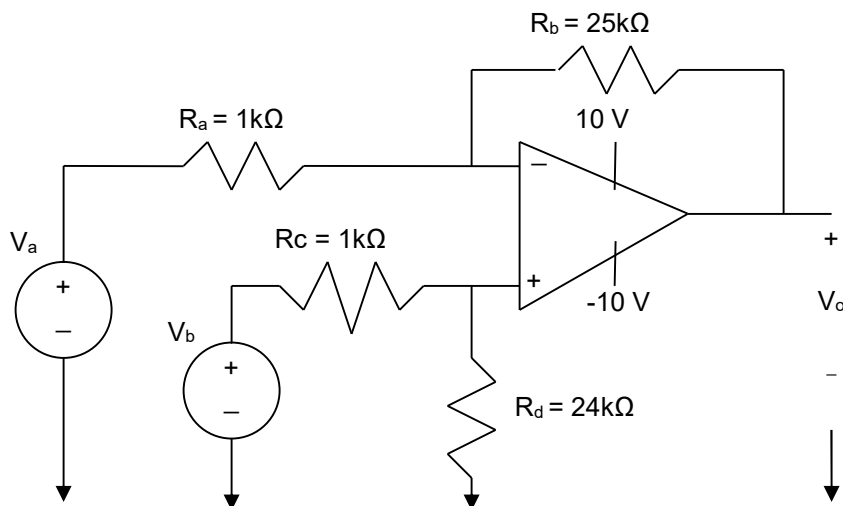

Solution:

a) Common Mode Gain = $A_{cm} = \frac{V_o}{V_{cm}} = \frac{R_a R_d - R_b R_c}{R_a (R_c + R_d)} = \frac{24 - 25}{1 * (1 + 24)} = -\frac{1}{25}$


b) Difference Mode Gain

$$A_{dm} = \frac{V_o}{V_{dm}} = \frac{R_d (R_a + R_b) + R_b (R_c + R_d)}{2 R_a (R_c + R_d)} = \frac{24(1 + 25) + 25(1 + 24)}{2 * 1 * (1 + 24)} = 24.98$$

c) Common Mode Rejection Ratio = CMRR = $\left| \frac{A_{dm}}{A_{cm}} \right| = \left| \frac{24.98}{-\frac{1}{25}} \right| = 624.5$


8U. In the difference amplifier shown below, compute

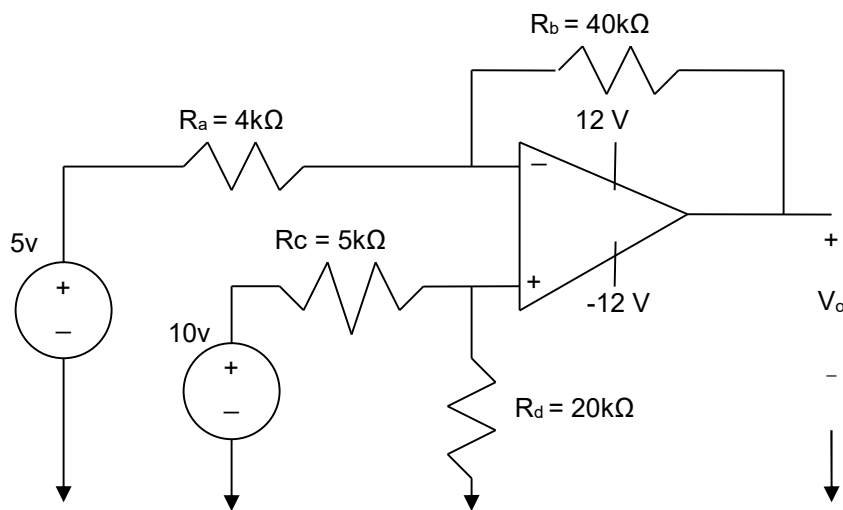- the differential mode gain
- the common mode gain
- the CMRR




Solution:

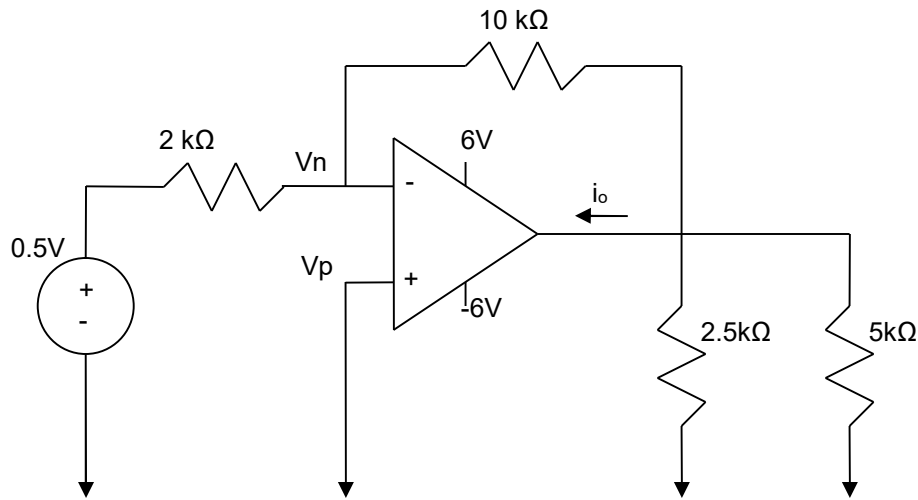9S. Find i_o in the following circuit using Op Amp DC Model where open loop gain, $A= 10,000$, Input resistance, R_i of $200\text{ k}\Omega$ and output resistance, R_o of $50\ \Omega$.



Solution:

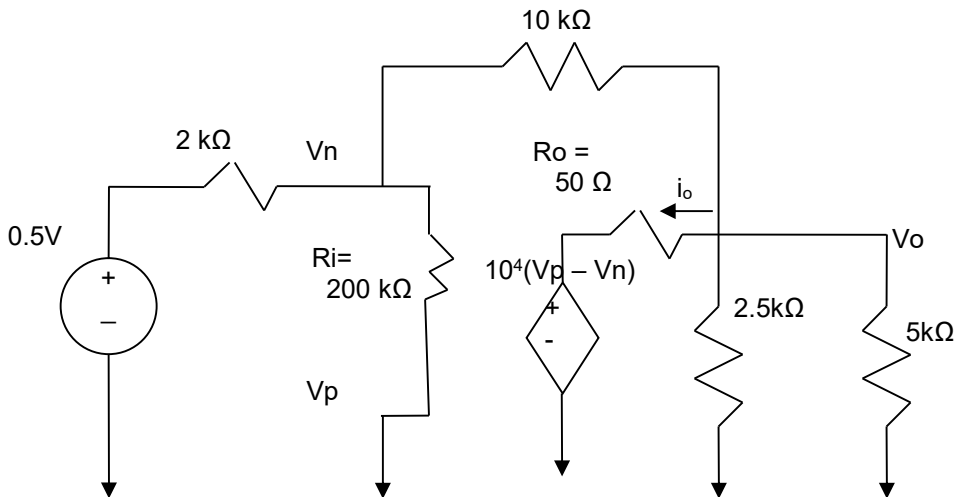redraw the circuit with Op Amp DC Mode and use Node Voltage to analyze the circuit:



3 essential nodes V_o , V_n & reference node.

$$\text{KCL at } V_n \rightarrow (V_n - 0.5)/2,000 + V_n/200,000 + (V_n - V_o)/10,000 = 0$$

$$\text{KCL at } V_o \rightarrow (V_o - V_n)/10,000 + V_o/5,000 + V_o/2,500 + (V_o - 10^4(-V_n))/50 = 0$$


Simplify the equations:

$$121V_n - 20V_o = -50$$

$$(2 \times 10^6 - 1)V_n - 207V_o = 0$$

Solve to find V_o & i_o

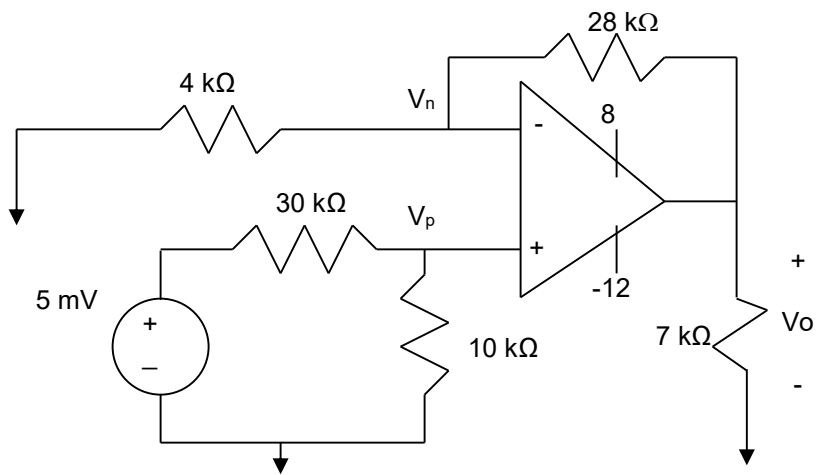9U. Find V_o in the following circuit using LM 324 Op Amp DC Model where open loop gain, $A= 10^5$, Input resistance, R_i of $2\text{ M}\Omega$ and output resistance, R_o of $75\ \Omega$.



Solution: