

# Fundamentals of Electrical Circuits - Chapter 11

1S. What is the phase sequence of each of the following sets of voltages?

- a)  $v_a = 208 \cos(\omega t + 27^\circ) \text{ V}$ ,  $v_b = 208 \cos(\omega t + 147^\circ) \text{ V}$ ,  $v_c = 208 \cos(\omega t - 93^\circ) \text{ V}$ .  
 b)  $v_a = 4160 \cos(\omega t - 18^\circ) \text{ V}$ ,  $v_b = 4160 \cos(\omega t - 138^\circ) \text{ V}$ ,  $v_c = 4160 \cos(\omega t + 102^\circ) \text{ V}$ .

**Solution:**

- a)  $\theta_b - \theta_a = +120^\circ$  and  $\theta_c - \theta_a = -120^\circ \rightarrow acb$  (negative) sequence  
 b)  $\theta_b - \theta_a = -120^\circ$  and  $\theta_c - \theta_a = +120^\circ \rightarrow abc$  (positive) sequence

1U. What is the phase sequence of each of the following sets of voltages?

- a)  $v_a = 250 \cos(\omega t - 58^\circ) \text{ V}$ ,  $v_b = 250 \cos(\omega t - 178^\circ) \text{ V}$ ,  $v_c = 250 \cos(\omega t + 62^\circ) \text{ V}$ .  
 b)  $v_a = 110 \cos(\omega t + 17^\circ) \text{ V}$ ,  $v_b = 110 \cos(\omega t + 137^\circ) \text{ V}$ ,  $v_c = 110 \cos(\omega t - 103^\circ) \text{ V}$ .

**Solution:**

2S. For each set of voltages, state whether or not the voltages from a balanced three-phase set. If the set is balanced, state whether the phase sequence is positive or negative. If the set is not balanced, explain why.

- a)  $v_a = 180 \cos(377t) \text{ V}$ ,  $v_b = 180 \cos(377t - 120^\circ) \text{ V}$ ,  $v_c = 180 \cos(377t - 240^\circ) \text{ V}$ .  
 b)  $v_a = 180 \sin(377t) \text{ V}$ ,  $v_b = 180 \sin(377t + 120^\circ) \text{ V}$ ,  $v_c = 180 \cos(377t - 120^\circ) \text{ V}$ .  
 c)  $v_a = -400 \sin(377t) \text{ V}$ ,  $v_b = 400 \sin(377t + 210^\circ) \text{ V}$ ,  $v_c = 400 \cos(377t - 30^\circ) \text{ V}$ .  
 d)  $v_a = 200 \cos(\omega t + 30^\circ) \text{ V}$ ,  $v_b = 201 \cos(\omega t + 150^\circ) \text{ V}$ ,  $v_c = 200 \cos(\omega t + 270^\circ) \text{ V}$ .  
 e)  $v_a = 208 \cos(\omega t + 42^\circ) \text{ V}$ ,  $v_b = 208 \cos(\omega t - 78^\circ) \text{ V}$ ,  $v_c = 208 \cos(\omega t - 201^\circ) \text{ V}$ .  
 f)  $v_a = 240 \cos(377t) \text{ V}$ ,  $v_b = 240 \cos(377t - 120^\circ) \text{ V}$ ,  $v_c = 240 \cos(397t + 120^\circ) \text{ V}$ .

**Solution:**

Part	Same Amplitude	Same Freq.	120° ΔPhase	abc or acb	Conclusion
a	Yes	Yes	Yes	abc	Balanced, Positive (abc) Sequence
b	Yes	Yes	No	acb	Unbalanced phase
c	Yes	Yes	No	None	Unbalanced phase
d	No	Yes	Yes	acb	Unbalanced amplitude
e	Yes	Yes	No	None	Unbalanced phase
f	Yes	No	Yes	abc	Unbalanced frequency

2U. For each set of voltages, state whether or not the voltages from a balanced three-phase set. If the set is balanced, state whether the phase sequence is positive or negative. If the set is not balanced, explain why.

- a)  $v_a = 180 \cos(29\pi t) \text{ V}$ ,  $v_b = 180 \cos(29\pi t + 120^\circ) \text{ V}$ ,  $v_c = 180 \cos(29\pi t - 120^\circ) \text{ V}$ .  
 b)  $v_a = 200 \sin(377t) \text{ V}$ ,  $v_b = (100 \cdot 2) \sin(377t - 120^\circ) \text{ V}$ ,  $v_c = 200 \cos(377t + 120^\circ) \text{ V}$ .  
 c)  $v_a = -400 \sin(377t + \pi/2) \text{ V}$ ,  $v_b = 400 \sin(377t - 150^\circ) \text{ V}$ ,  $v_c = 400 \cos(377t - 30^\circ) \text{ V}$ .  
 d)  $v_a = 200 \cos(\omega t + 30^\circ) \text{ V}$ ,  $v_b = 201 \cos(\omega t + 150^\circ) \text{ V}$ ,  $v_c = 200 \cos(\omega t + 270^\circ) \text{ V}$ .

**Solution:**

3S. The time-domain expressions for three line-to-neutral voltages at the terminals of a Y-Connected load are:

$$v_{AN} = 169.71 \cos(\omega t + 26^\circ) \text{ V}$$

$$v_{BN} = 169.71 \cos(\omega t - 94^\circ) \text{ V}$$

$$v_{CN} = 169.71 \cos(\omega t + 146^\circ) \text{ V}$$

What are the time-domain expressions for the three line-to-line voltages  $v_{AB}$ ,  $v_{BC}$  and  $v_{CA}$ ?

**Solution:**

$$V_{AN} = 169.71 \angle 26^\circ \rightarrow V_{AB} = \sqrt{3} V_{AN} \angle 30^\circ = \sqrt{3} 169.71 \angle 56^\circ = 293.95 \angle 56^\circ \rightarrow V_{AB}(t) = 293.95 \cos(\omega t + 56^\circ)$$

$$V_{BN} = 169.71 \angle -94^\circ \rightarrow V_{BC} = \sqrt{3} V_{BN} \angle 30^\circ = \sqrt{3} 169.71 \angle -64^\circ = 293.95 \angle -64^\circ \rightarrow V_{BC}(t) = 293.95 \cos(\omega t - 64^\circ)$$

$$V_{CN} = 169.71 \angle 146^\circ \rightarrow V_{CA} = \sqrt{3} V_{CN} \angle 30^\circ = \sqrt{3} 169.71 \angle 176^\circ = 293.95 \angle 176^\circ \rightarrow V_{CA}(t) = 293.95 \cos(\omega t + 176^\circ)$$

3U. The time-domain expressions for three line-to-neutral voltages at the terminals of a Y-Connected load are:

$$V_{AN} = 125 \cos(\omega t - 4^\circ) \text{ V}$$

$$V_{BN} = 125 \cos(\omega t - 124^\circ) \text{ V}$$

$$V_{CN} = 125 \cos(\omega t + 116^\circ) \text{ V}$$

What are the time-domain expressions for the three line-to-line voltages  $V_{AB}$ ,  $V_{BC}$  and  $V_{CA}$ ?


**Solution:**

4S. The magnitude of the line voltage at the terminals of a balanced Y-connected load is 660V. The load impedance is  $30.48 + j22.86 \Omega/\phi$ . The load is fed from a line that has an impedance of  $0.25 + j2 \Omega/\phi$ .

- a) What is the magnitude of the line current?
- b) What is the magnitude of the line voltage at the source?

**Solution:**

a)

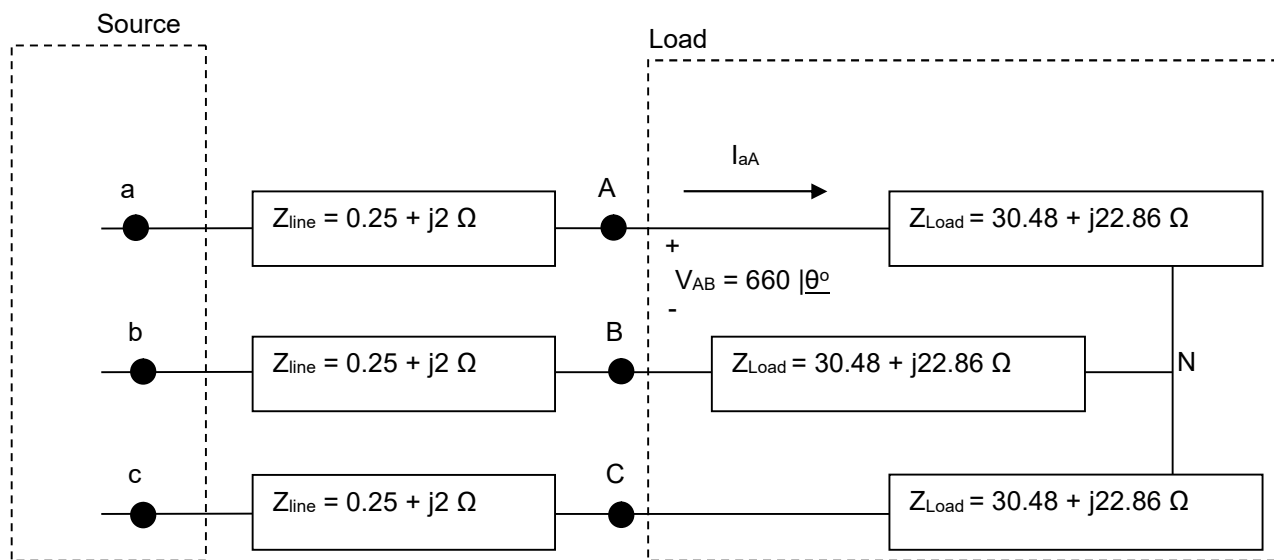

$$V_{AN} = \frac{|V_{AB}|}{\sqrt{3}} \angle 0 - 30^\circ = \frac{660}{\sqrt{3}} \angle -30^\circ = 381 \angle -30^\circ \text{ V}$$

$$I_{aA} = \frac{V_{AN}}{Z_{load}} = \frac{381 \angle -30^\circ}{30.48 + j22.86} = 3.92 - j9.20 = 10 \angle -66.87^\circ \text{ A}$$

Therefore  $|I_{aA}| = 10 \text{ A}$

b)

Apply KVL to find  $|V_{ab}| =$

$$V_{ab} = V_{aA} + V_{AB} + V_{Bb} = Z_{line} I_{aA} + V_{AB} + Z_{line} I_{Bb} = Z_{line} I_{aA} + V_{AB} - Z_{line} I_{bB}$$

$$V_{ab} = (0.25 + j2)(10 \angle -66.87^\circ) + 660 \angle 0^\circ - (0.25 + j2)(10 \angle -186.87^\circ) = 684.71 \angle 2.10^\circ$$

Therefore  $|V_{ab}| = 684.71V$


4U. The magnitude of the line voltage at the terminals of a balanced Y-connected load is 250V. The load impedance is  $150 + j200 \Omega/\phi$ . The load is fed from a line that has an impedance of  $0.1 + j.5 \Omega/\phi$ .

- What is the magnitude of the line current?
- What is the magnitude of the line voltage at the source?

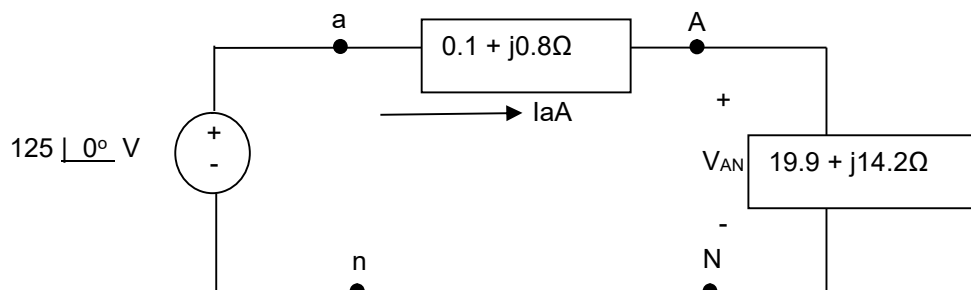**Solution:**

5S. The magnitude of the phase voltage of an ideal balanced three phase Y-connected source is 125V. The source is connected to a balanced Y-connected load by a distribution line that has an impedance of  $0.1 + j0.8 \Omega/\phi$ . The load impedance is  $19.9 + j14.2 \Omega/\phi$ . The phase sequence of the source is acb. Use the a-phase voltage of the source as the reference. Specify the magnitude and phase angle of the following quantities:

- the three line currents.
- the three line voltages at the source.
- the three phase voltages at the load.
- the three line voltages at the load.



**Solution:**

a) Find the a-phase line current from the above circuit

$$\text{KVL} \rightarrow I_{aA} = \frac{125}{(0.1 + j0.8 + 19.9 + j14.2)} = \frac{125}{20 + j15} = 4 - j3 = 5 \angle -36.87^\circ \text{ A}$$

Negative (acb) Phase Sequence  $\rightarrow$

$$I_{bB} = 5 \angle -36.87^\circ + 120^\circ \text{ A} = 5 \angle 83.13^\circ \text{ A}$$

$$I_{cC} = 5 \angle -36.87^\circ - 120^\circ \text{ A} = 5 \angle -156.87^\circ \text{ A}$$

b) Line Voltages at the source  $V_{ab}$ ,  $V_{bc}$ ,  $V_{ca}$

$$V_{an} = 125 \angle 0^\circ \text{ V} \quad \text{Phase Voltage}$$

$$V_{ab} = V_{an}(\sqrt{3} \angle -30^\circ) = 216.51 \angle -30^\circ \text{ V}$$

$$V_{bc} = 216.51 \angle -30^\circ + 120^\circ = 216.51 \angle 90^\circ \text{ V}$$

$$V_{ca} = 216.51 \angle -30^\circ - 120^\circ = 216.51 \angle -150^\circ \text{ V}$$

**c) Phase Voltages at the load**

$$V_{AN} = I_{aA} Z_L = (4 - j3)(19.9 + j14.2) = 122.2 - j2.9 = 122.23 \angle -1.36^\circ \text{ V} \quad \text{Phase Voltage}$$

$$V_{BN} = 122.23 \angle -1.36^\circ + 120^\circ = 122.23 \angle 118.64^\circ \text{ V}$$

$$V_{CN} = 122.23 \angle -1.36^\circ - 120^\circ = 122.23 \angle -121.36^\circ \text{ V}$$

**d) Line Voltages at the load**

Find the line voltage at a first & then using the fact that negative phase sequence to find b&c line voltages.

$$V_{AN} = 122.23 \angle -1.36^\circ \text{ V} \quad \text{Phase Voltage}$$

$$V_{AB} = V_{AN} (\sqrt{3} \angle -30^\circ) = 211.71 \angle -31.36^\circ \text{ V}$$

$$V_{BC} = 211.71 \angle -31.36^\circ + 120^\circ = 211.71 \angle 88.69^\circ \text{ V}$$

$$V_{CA} = 211.71 \angle -31.36^\circ - 120^\circ = 211.71 \angle -151.36^\circ \text{ V}$$

5U. The magnitude of the phase voltage of an ideal balanced three phase Y-connected source is 250 kV. The source is connected to a balanced Y-connected load by a distribution line that has an impedance of  $0.5 + j2.2 \Omega/\phi$ . The load impedance is  $19.5 + j7.8 \Omega/\phi$ . The phase sequence of the source is abc. Use the a-phase voltage of the source as the reference. Specify the magnitude and phase angle of the following quantities:


- a) the three line currents.
- b) the three line voltages at the source.
- c) the three phase voltages at the load.
- d) the three line voltages at the load.

**Solution:**

6S. A balanced  $\Delta$ -connected load has an impedance of  $60 + j45 \Omega/\phi$ . The load is fed through a line having an impedance of  $0.8 + j0.6 \Omega/\phi$ . The phase voltage at the terminals of the load is 480 V. The phase sequence is positive. Use  $V_{AB}$  as the reference.

- a) Calculate the three phase currents of the load.
- b) Calculate the three line currents.
- c) Calculate the three line voltages at the sending end of the line.

**Solution:**

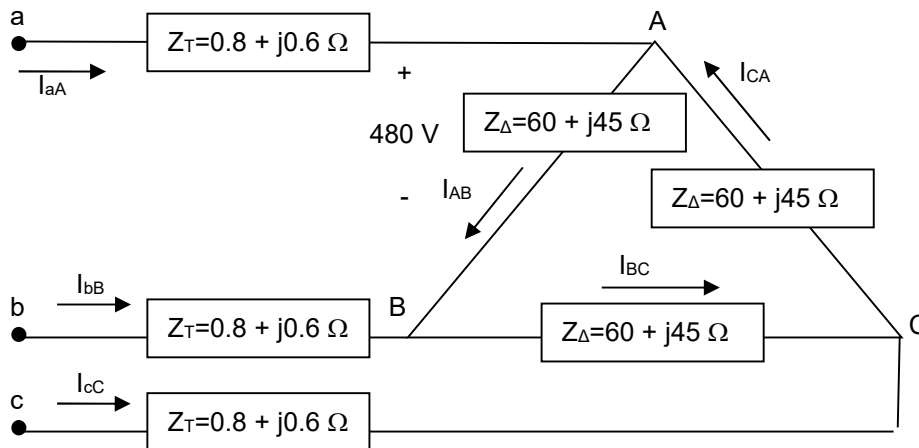

**a) Phase Currents**

$$I_{AB} = \frac{480}{60 + j45} = 6.4 \angle -36.87^\circ A$$

*abc sequence*

$$I_{BC} = 6.4 \angle -120 - 36.87^\circ = 6.4 \angle -156.87^\circ A$$

$$I_{CA} = 6.4 \angle +120 - 36.87^\circ = 6.4 \angle +83.13^\circ A$$

**b) Line Currents**

$$I_{aA} = \sqrt{3} \angle -30^\circ I_{AB} = 11.09 \angle -66.87^\circ A$$

*abc sequence*

$$I_{bB} = 11.09 \angle -120 - 66.87^\circ = 11.09 \angle -186.87^\circ A$$

$$I_{cC} = 11.09 \angle +120 - 66.87^\circ = 11.09 \angle 53.13^\circ A$$

**c) Line voltage from Sending side**

$$V_{ab} = [11.09 \angle -66.87^\circ][0.8 + j0.6] + 480 - [11.09 \angle -186.87^\circ][0.8 + j0.6] = 499.20 \angle 0^\circ V$$

*abc sequence*

$$V_{bc} = 499.20 \angle -120^\circ V$$

$$V_{ca} = 499.20 \angle 120^\circ V$$

6U. A balanced  $\Delta$ -connected load has an impedance of  $100 + j20 \Omega/\phi$ . The load is fed through a line having an impedance of  $0.5 + j2.5 \Omega/\phi$ . The phase voltage at the terminals of the load is 660 V. The phase sequence is negative. Use  $V_{AB}$  as the reference.


- Calculate the three phase currents of the load.
- Calculate the three line currents.
- Calculate the three line voltages at the sending end of the line.

**Solution:**

7S. A balanced three-phase distribution line has an impedance of  $1 + j8 \Omega/\phi$ . This line is used to supply three balanced three-phase loads that are connected in parallel. The Complex power at the three loads are  $L_1 = 120 \text{ KVA}$  at 0.96 pf lead,  $L_2 = 180 \text{ kVA}$  at 0.80 pf lag and  $L_3 = 100.8 \text{ kW}$  and 15.6 kVAR (magnetizing).

The magnitude of the line voltage at the terminals of the loads is  $2400\sqrt{3} V$ .

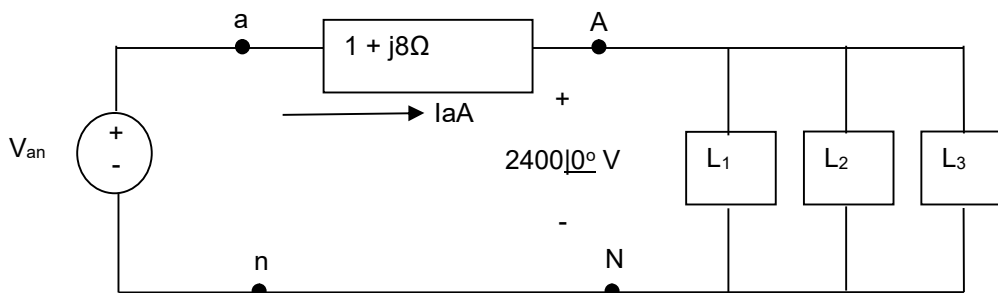- What is the magnitude of the line voltage at the sending end of the line?
- What is the percent efficiency of the distribution line with respect to average power?



**Solution:**

a)

$$|V_{AB}| = \sqrt{3} |V_{AN}| \rightarrow 2400\sqrt{3} = \sqrt{3} |V_{AN}| \rightarrow |V_{AN}| = 2400 \text{ Assume a is reference so phase is } 0$$

Load 1, PF=0.96 & lead so  $\theta < 0 \rightarrow \theta = -\cos^{-1}(0.96) = -16.3^\circ$   
 $S_{1/\phi} = 120,000\cos(-16.3^\circ) + j120,000\sin(-16.3^\circ) = 115,200 - j33,600 \text{ VA}$

Load 2, PF=0.80 & lag so  $\theta > 0 \rightarrow \theta = \cos^{-1}(0.80) = 36.9^\circ$   
 $S_{2/\phi} = 180,000\cos(36.9^\circ) + j180,000\sin(36.9^\circ) = 143,943 + j108,076 \text{ VA}$

Load 3  
 $S_{3/\phi} = 100,800 + j15,600 \text{ VA}$

Total Complex Power  
 $S_{T/\phi} = S_{1/\phi} + S_{2/\phi} + S_{3/\phi} = 360,000 + j90,000 \text{ VA}$

$$S_{T/\phi} = (I_{aA}^*)(V_{AN})$$

$$I_{aA}^* = \frac{360,000 + j90,000}{2400} = 150 + j37.5A$$

$$I_{aA} = 150 - j37.5A$$

$$V_{an} = (1+j8)(I_{aA}) + 2400 = 2850 + j1162.5 = 3077.97 \angle 22.19^\circ \text{ V}$$

$$|V_{ab}| = \sqrt{3} |V_{an}| = 5331.2 \text{ V}$$


b)

$$S_{g/\phi} = (I_{aA}^*)(V_{an}) = (150 - j37.5)(2850 + j1162.5) = 383,900 + j281,250 \text{ VA}$$

$$\% \text{efficiency} = \frac{\text{Load\_Real\_Power}}{\text{Source\_Real\_Power}} = \frac{360,000}{383,900} = 94\%$$

7U. A balanced three-phase distribution line has an impedance of  $2+j4 \Omega/\phi$ . This line is used to supply three balanced three-phase Y-connected loads that are connected in parallel. The Complex power at the three loads are  $L_1 = 200 \text{ KVA}$  at 0.5 pf lag,  $L_2 = 80 \text{ kVA}$  at 0.3 pf lead and  $L_3 = 300 \text{ kW}$  and  $100 \text{ kVAR}$  (magnetizing). The magnitude of the phase voltage at the load terminals is  $120 \text{ V}$ .

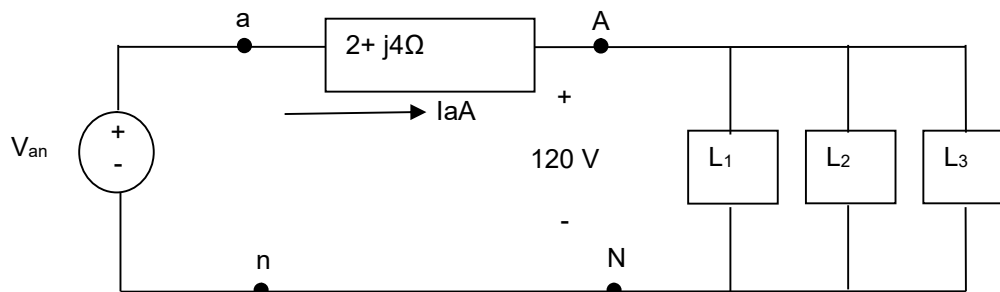- a) What is the magnitude of the line voltage at the sending end of the line?
- b) What is the percent efficiency of the distribution line with respect to average power?



**Solution:**

8S. The three pieces of computer equipment described below are installed as part of a computation center.

- \* DISK: 4.864 kW at 0.79 pf lag
- \* ZIP DRIVE: 17.636 kVA at 0.96 pf lag
- \* CPU: line current 73.8 A, 13.853 kVAR

Each piece of equipment is balanced three-phase load rated at 208 V line voltage. Calculate

- a) the magnitude of the line current supplying these three devices
- b) the power factor of the combined load.

**Solution:**

**a)**

Disk Load PF=0.79 & lag so  $\theta > 0 \rightarrow \theta = \cos^{-1}(0.79) = 37.8^\circ$   
 $S_d = 4864 + j4864(\tan 37.8^\circ) = 4864 + j3773 \text{ VA}$

Zip Load, PF=0.96 & lag so  $\theta > 0 \rightarrow \theta = \cos^{-1}(0.96) = 16.3^\circ$   
 $S_z = 17,636 \cos(16.3^\circ) + j17,636 \sin(16.3^\circ) = 16931 + j 4938$

CPU Load,

$$\text{Reactive Power} = Q_c = \sqrt{3} V_L I_L \sin(\theta)$$

$$13,853 = \sqrt{3}(208)(73.8) \sin(\theta) \rightarrow \sin \theta = 0.52 \quad \& \quad \cos \theta = 0.85 \quad \& \quad \tan \theta = 0.52/0.85$$

$$S_c = 13853(1 / \tan \theta) + j13,853 = 22,644 + j13,853$$

$$S_T = S_d + S_z + S_c = 44439 + j22564 \text{ VA}$$

$$S_{T/\phi} = (1/3)S_T = 14813 + j7521 \text{ VA} \quad \text{Magnitude of phase power}$$

$$S_{T/\phi} = V_{AN} I_{aA}^* = (208 / \sqrt{3}) I_{aA}^* \rightarrow I_{aA}^* = 123 + j63 \rightarrow I_{aA} = 123 - j63 = 138 \angle -27^\circ \text{ A (rms)}$$

**b) Power Factor of the combined load**

$$\theta = \tan^{-1}(22564/44439) = 27^\circ$$

$\theta > 0 \rightarrow$  lagging

$$\text{PF} = \cos(27) = 0.89 \text{ lagging}$$

8U. The three major components of an Electric car are listed below with their power profile:

- \* Motor: 800 W at 0.4 pf lag
- \* Instrument Panel: 50 VA at 0.8 pf lag
- \* Controllers, Wiring and connections: effective phase current of 2 A, 10 VAR

Each component group is fed by balanced three-phase source rated at 72 V effective phase voltage. Determine the following:

- a) magnitude of the line current supplying these three devices
- b) power factor for the combined load.

**Solution:**