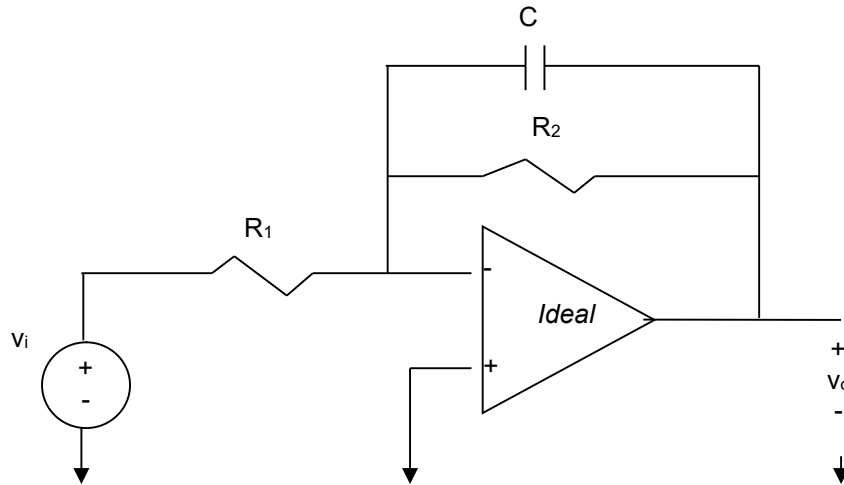


# Fundamentals of Electrical Circuits - Chapter 13

1S. Using the following circuit:




- a) Design a low pass filter with a passband gain of 10 dB and a cutoff frequency of 1 kHz. Assume a 750 nF capacitor is available.
- b) Draw the circuit diagram and label all components.


**Solution:**

- a) Gain = 10 dB =  $20 \log K \rightarrow K = 10^{0.5} = 3.16$   
For a low Pass Filter:  
 $K = R_2 / R_1 \rightarrow R_1 = R_2 / 3.16$   
 $\omega_c = 1 / (R_2 C) \rightarrow R_2 = 1 / ((2000\pi)(750 \times 10^{-9})) = 212.21 \Omega$   
 $R_1 = 212.21 / 3.16 = 67.15 \Omega$

b)

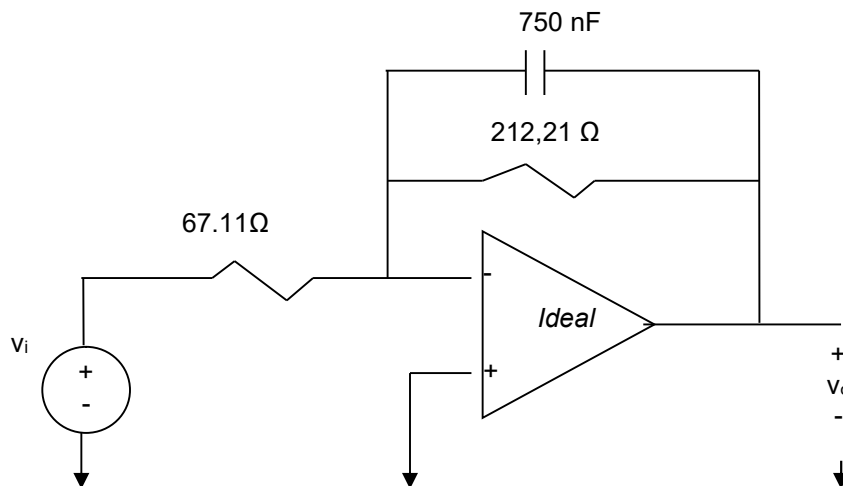


1U. Using the following circuit:

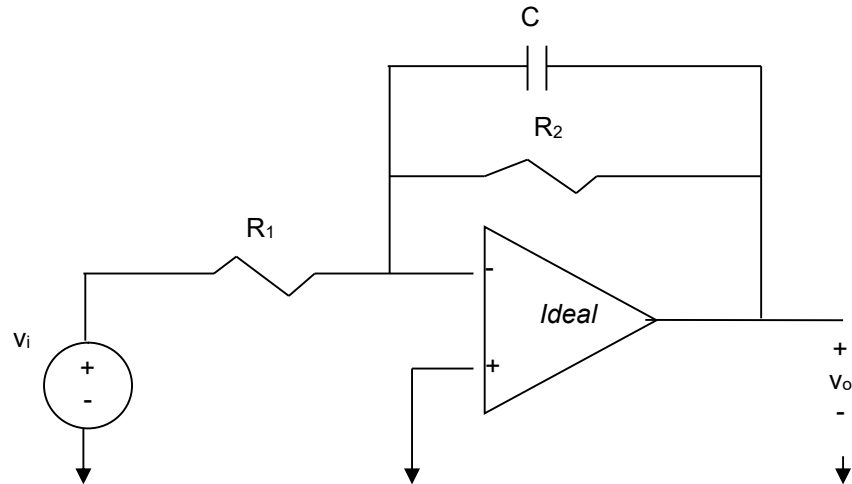

- Design a low pass filter with a passband gain of 40 dB and a cutoff frequency of 5 kHz. Assume only a 0.5 uF capacitor is available.
- Draw the circuit diagram and label all components.

**Solution:**

2S. Using the following circuit:

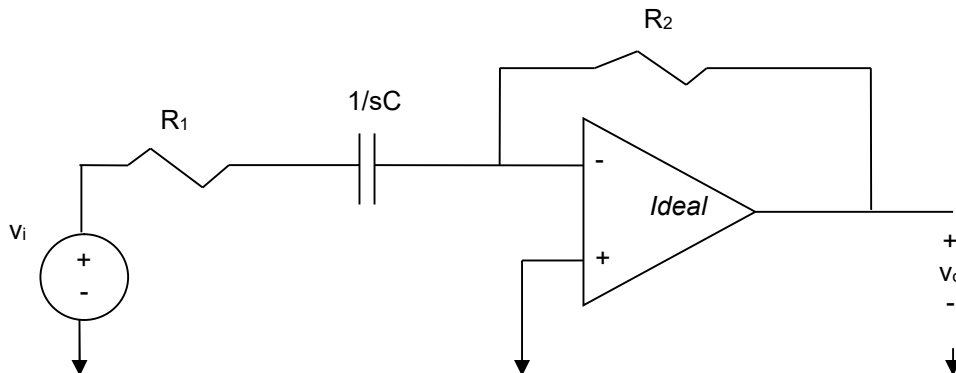


- Design a high pass filter with a cutoff frequency of 8 kHz and a passband gain of 14 dB. Use a 3.9 nF capacitor in the design.
- Draw a circuit diagram of the filter and label all the components.


**Solution:**

- Gain = 14 dB = 20 log K  $\rightarrow$   $K = 10^{(14/20)} = 5.01$   
For a high Pass Filter:  
 $K = R_2 / R_1 \rightarrow R_2 = 5.01R_1$   
 $\omega_c = 1 / (R_1 C) \rightarrow R_1 = 1 / ((16000\pi)(3.9 \times 10^{-9})) = 5101.12 \Omega$   
 $R_2 = (5101.12)(5.01) = 25,556.6 \Omega$

b)

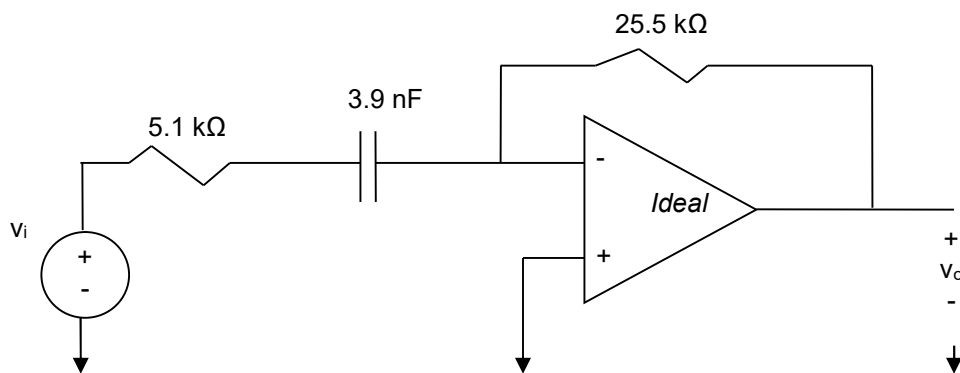

2U. Using the following circuit:

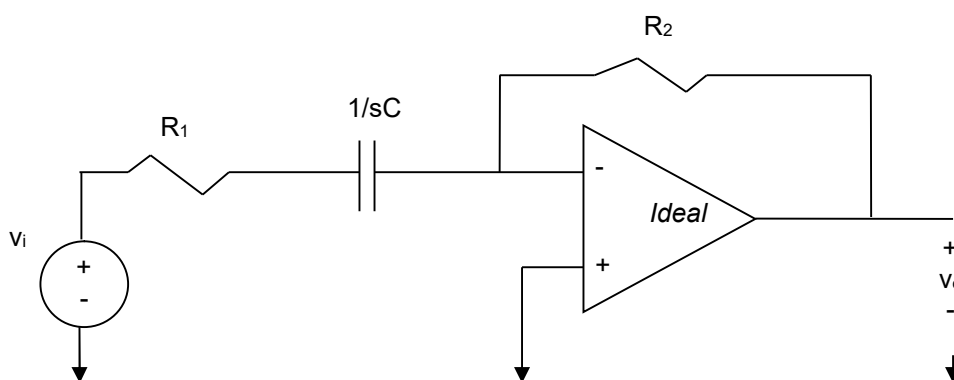

- Design a high pass filter with a cutoff frequency of 25 kHz and a passband gain of 60 dB. Use only a 2.5 pF capacitor in the design.
- Draw a circuit diagram of the filter and label all the components.


**Solution:**

3S. The voltage transfer function of the prototype bandpass filter for the following circuit is

$$H(s) = \frac{\left(\frac{1}{Q}\right)s}{s^2 + \left(\frac{1}{Q}\right)s + 1}$$

If the circuit is scaled in both component magnitude and frequency, the scaled transfer function is
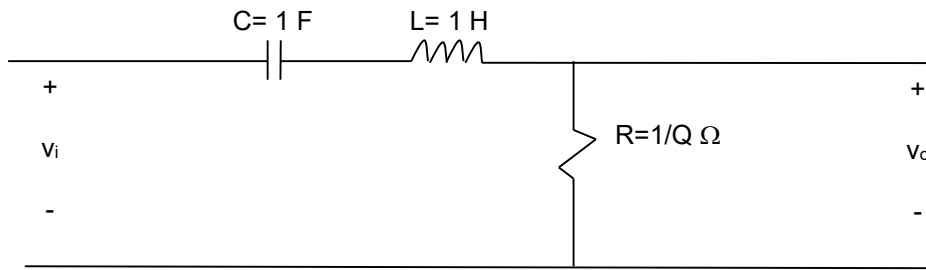
$$H(s) = \frac{\left(\frac{1}{Q}\right)\left(\frac{s}{k_f}\right)}{\left(\frac{s}{k_f}\right)^2 + \left(\frac{1}{Q}\right)\frac{s}{k_f} + 1}$$



- Specify the component values for the above prototype passive bandpass filter if the quality factor of the filter is 20.
- Specify the component values for the band pass filter described above if the quality factor is 20; the center, or resonant frequency is 40 krad/s; and the impedance at resonance is 5 k Ω.
- Draw a circuit diagram of the scaled filter and label all the components.

**Solution:**

- $L = 1 \text{ H}$  ,  $C = 1 \text{ F}$  ,  $R = 1/Q = 1/20 = 0.05 \text{ } \Omega$
- At resonance the Capacitor and Inductor cancel each others effect such that  $H(s) = 1$  in other words  $Z_{eq} = R' = 5000$  therefore:

Component Scaling Factor,  $K_c = R'/R = 5000/0.05 = 100,000$

Frequency Scaling Factor,  $K_f = \omega_o' / \omega_o$

We have  $\omega_o' = 40,000 \text{ rad/s}$  but need to find  $\omega_o$

Since we know the above band pass filter's transfer function is:

$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_o^2}$$

$$\beta = \frac{\omega_o}{Q} \Rightarrow H(s) = \frac{\frac{\omega_o}{Q} s}{s^2 + \frac{\omega_o}{Q} s + \omega_o^2}$$

Comparing this equation with the one given in the problem state, we can conclude that:  
 $\omega_o = 1$  Therefore:


Frequency Scaling Factor,  $K_f = \omega_o' / \omega_o = 40,000$

$R' = K_c R = (0.05)(100,000) = 5 \text{ K}\Omega$

$L' = (K_c/K_f) L = 100,000/40,000 = 2.5 \text{ H}$

$C' = C / (K_c K_f) = 1/(40,000)(100,000) = 250 \text{ pF}$

c)

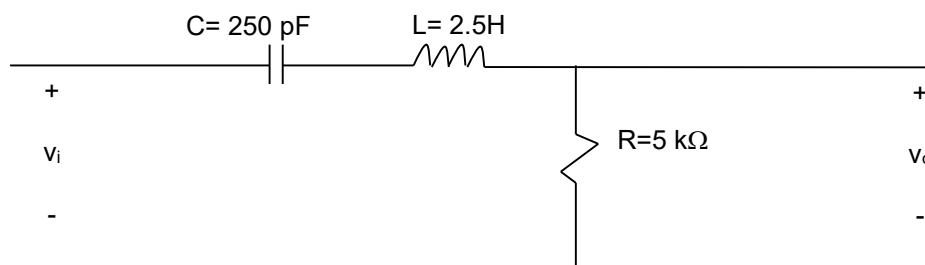


3U. The voltage transfer function of the prototype bandpass filter for the following circuit is

$$H(s) = \frac{\left(\frac{1}{Q}\right)s}{s^2 + \left(\frac{1}{Q}\right)s + 1}$$

If the circuit is scaled in both component magnitude and frequency, the scaled transfer function is
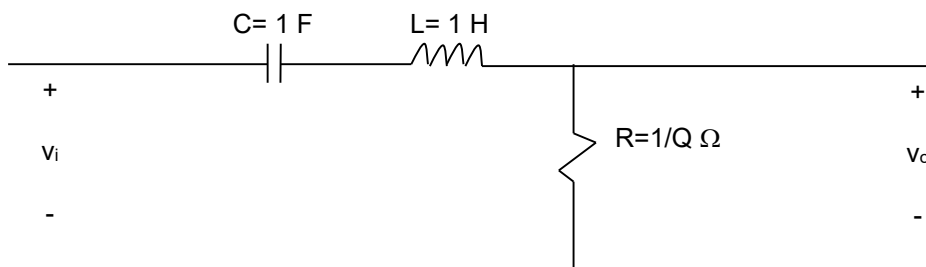
$$H(s) = \frac{\left(\frac{1}{Q}\right)\left(\frac{s}{k_f}\right)}{\left(\frac{s}{k_f}\right)^2 + \left(\frac{1}{Q}\right)\frac{s}{k_f} + 1}$$



- Specify the component values for the above prototype passive bandpass filter if the quality factor of the filter is 60.
- Specify the component values for the band pass filter described above if the quality factor is 60; the center, or resonant frequency is 50 krad/s; and the impedance at resonance is 10 k Ω.
- Draw a circuit diagram of the scaled filter and label all the components.

**Solution:**


4S. The voltage transfer function of the prototype bandpass filter for the following circuit is

$$H(s) = \frac{\left(\frac{1}{Q}\right)s}{s^2 + \left(\frac{1}{Q}\right)s + 1}$$

If the circuit is scaled in both component magnitude and frequency, the scaled transfer function is

$$H(s) = \frac{\left(\frac{1}{Q}\right)\left(\frac{s}{k_f}\right)}{\left(\frac{s}{k_f}\right)^2 + \left(\frac{1}{Q}\right)\frac{s}{k_f} + 1}$$

and its  $\omega_0 = 1$  rad/sec.

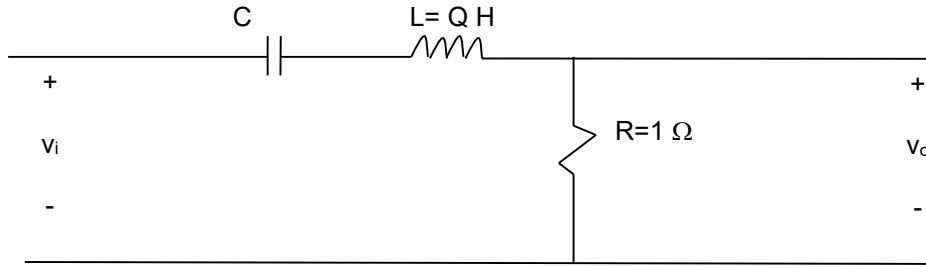

- What is the value of C in the prototype filter circuit?
- What is the transfer function of the proto-type filter?
- Use the alternative prototype circuit just described to design a passive bandpass filter that has a quality factor of 16, a center frequency of 25 krad/s, and an impedance of 10kΩ at resonance.
- Draw a diagram of the scaled filter and label all the components.
- Use the relationship shown to write the transfer function of the scaled circuit.

**Solution:**

a) bandpass filter  $\rightarrow \omega_o^2 = 1/LC \rightarrow 1 = 1/LC \rightarrow C = 1/L \rightarrow C = 1/Q$

b) Since we know the above band pass filter's transfer function is:

$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_o^2}$$

$$\beta = \frac{\omega_o}{Q} = \frac{1}{Q} \Rightarrow H(s) = \frac{\frac{1}{Q} s}{s^2 + \frac{1}{Q} s + 1}$$


c)  $R=1 \Omega, R'=10 \text{ k}\Omega, Q=16$   
 $L=Q = 16 \text{ H}, C = 1/L = 0.0625 \text{ F}$   
 Frequency Scaling Factor,  $K_f = \omega_o' / \omega_o = 25,000$   
 Component magnitude Scaling Factor,  $K_c = R'/R = 10,000/1 = 10,000$

$$R' = K_c R = 10 \text{ k}\Omega$$

$$L' = (K_c/K_f) L = (10,000/25,000) (16) = 6.4 \text{ H}$$

$$C' = C / (K_c K_f) = 0.0625 / (10,000)(25,000) = 250 \text{ pF}$$

d)

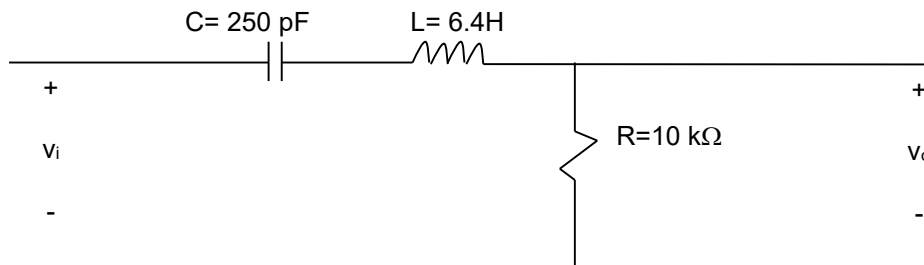

e)

$$H(s) = \frac{\left(\frac{\omega_o'}{Q}\right)s}{s^2 + \left(\frac{\omega_o'}{Q}\right)s + \omega_o'^2} = \frac{\left(\frac{25000}{16}\right)s}{s^2 + \left(\frac{25000}{16}\right)s + 25000^2}$$


4U. The voltage transfer function of the prototype bandpass filter for the following circuit is

$$H(s) = \frac{\left(\frac{1}{Q}\right)s}{s^2 + \left(\frac{1}{Q}\right)s + 1}$$

If the circuit is scaled in both component magnitude and frequency, the scaled transfer function is

$$H(s) = \frac{\left(\frac{1}{Q}\right)\left(\frac{s}{k_f}\right)}{\left(\frac{s}{k_f}\right)^2 + \left(\frac{1}{Q}\right)\frac{s}{k_f} + 1}$$

and its  $\omega_o = 10$  rad/sec.

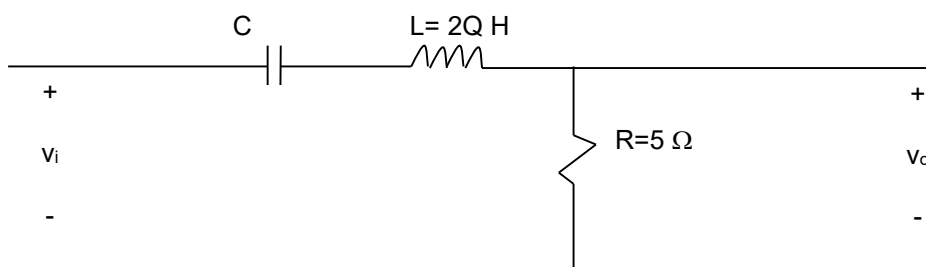

- What is the value of C in the prototype filter circuit?
- What is the transfer function of the proto-type filter?
- Use the alternative prototype circuit just described to design a passive bandpass filter that has a quality factor of 40, a center frequency of 50 krad/s, and an impedance of 10kΩ at resonance.
- Draw a diagram of the scaled filter and label all the components.
- Use the relationship shown to write the transfer function of the scaled circuit.

**Solution:**

5S. Design a unity-gain bandpass filter, using a cascade connection, to give a center frequency of 200 Hz and a bandwidth of 1000 Hz. Use 5 uF capacitors. Specify  $f_{c1}$ ,  $f_{c2}$ ,  $R_L$ , and  $R_H$ .

**Solution:**

$$K = 1$$

$$\omega_o = 2\pi f_o = 400\pi$$

$$\beta = 2\pi (1000) = 2000\pi$$

To find the cut off frequency  $\omega_{c1}$  and  $\omega_{c2}$  use the following two equations:

$$\beta = \omega_{c2} - \omega_{c1} = 2000\pi$$

$$\omega_o^2 = \omega_{c1} \omega_{c2} = (400\pi)^2$$

Find  $\omega_{c2}$  in-term of  $\omega_{c1}$  from equation 2 and plug it back into equation 1

$$\omega_{c1}^2 + 2000 \pi \omega_{c1} - (400\pi)^2 = 0$$

$$\omega_{c1} = -1000\pi \pm \sqrt{10^6 \pi^2 + 4(400\pi)^2} = -1000\pi(1 \pm \sqrt{1.16})$$

Since negative does not make sense, the only valid answer is  $\omega_{c1} = 242.01 \text{ rad / s}$

$$\text{Therefore } \omega_{c2} = 2000\pi + \omega_{c1} = 6525.19 \text{ rad / s}$$

which means  $f_{c1} = 38.52 \text{ Hz}$  and  $f_{c2} = 1038.52 \text{ Hz}$

Since this is a two stage Bandpass filter we know:

The low pass filter Stage

$$\omega_{c2} = \frac{1}{R_L C_L} = 6525.19 \Rightarrow R_L = \frac{1}{(6525.19)(5 \times 10^{-6})} = 30.65 \Omega$$

The high pass filter Stage

$$\omega_{c1} = \frac{1}{R_H C_H} = 242.01 \Rightarrow R_H = \frac{1}{(242.01)(5 \times 10^{-6})} = 826.43 \Omega$$

---

5U. Design a unity-gain bandpass filter, using a cascade connection, to give a center frequency of 400 kHz and a bandwidth of 600 kHz. Use 10 pF capacitors. Specify  $f_{c1}$ ,  $f_{c2}$ ,  $R_L$ , and  $R_H$ .

**Solution:**

---

6S. Design a parallel bandreject filter with a center frequency of 1000 rad/s, a bandwidth of 4000 rad/s, and a passband gain of 6. Use 0.2 uF capacitors and specify all resistor values.

**Solution:**

$$K = 6$$

$$\omega_o = 1000 \text{ rad/s}$$

$$\beta = 4000 \text{ rad/s}$$

$$C = 0.2 \text{ uF}$$

To find the cut off frequency  $\omega_{c1}$  and  $\omega_{c2}$  user the following two equations:

$$\beta = \omega_{c2} - \omega_{c1} = 4000$$

$$\omega_o^2 = \omega_{c1} \omega_{c2} = 10^6$$

Find  $\omega_{c2}$  in-term of  $\omega_{c1}$  from equation 2 and plug it back into equation 1

$$\omega_{c1}^2 + 4000 \omega_{c1} - 10^6 = 0$$

$$\omega_{c1} = -2000 \pm 1000\sqrt{5}$$

Since negative does not make sense the only valid answer is  $\omega_{c1} = 236.07 \text{ rad / s}$

$$\text{Therefore } \omega_{c2} = 4,000 + \omega_{c1} = 4236.07 \text{ rad / s}$$

Since this is a two stage Bandreject filter we know:

The low pass filter Stage

$$\omega_{c1} = \frac{1}{R_L C_L} = 236.07 \Rightarrow R_L = \frac{1}{(236.07)(2 \times 10^{-7})} = 21,180.2 \Omega$$

The high pass filter Stage




$$\omega_{c2} = \frac{1}{R_H C_H} = 4236.07 \Rightarrow R_H = \frac{1}{(4236.07)(2 \times 10^{-7})} = 1180.34 \Omega$$

$$K = R_f / R_i = 6 \rightarrow \text{if } R_i = 10 \text{ k}\Omega \text{ then } R_f = 60 \text{ k}\Omega$$

6U. Design a parallel bandreject filter with a center frequency of 20 M rad/s, a bandwidth of 4 Mrad/s, and a passband gain of 20. Use 1 nF capacitors and specify all resistor values.

**Solution:**

7S. Using the following circuit:

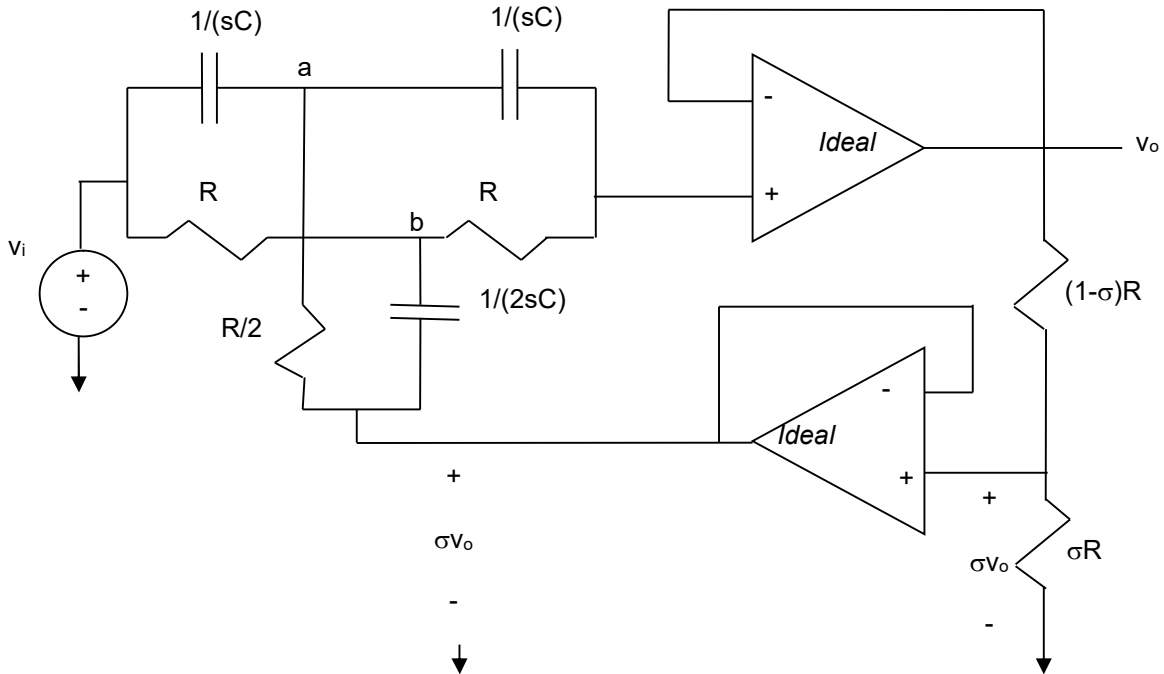

$$\text{Given: } H(s) = \frac{s^2 + \omega_o^2}{s^2 + \beta s + \omega_o^2} \quad \text{where } \omega_o^2 = \frac{1}{R^2 C^2}, \quad \beta = \frac{4(1-\sigma)}{RC}, \quad \sigma = 1 - \frac{1}{4Q}$$

- design a narrow-band bandreject filter having a center frequency of 1 kHz and a quality factor of 20. Base the design on  $C=15 \text{ nF}$ .
- Draw the circuit diagram of the filter and label all component values on the diagram.
- What is the scaled transfer function of the filter?

**Solution:**

- Given:  $\omega_o = 2000\pi$ ;  $Q = 20$  and  $C=15 \text{ nF}$

$$\omega_o = \frac{1}{RC} \Rightarrow R = \frac{1}{2000\pi(15 \times 10^{-9})} = 10610.3 \Omega$$


$$\sigma = 1 - \frac{1}{4Q} = 1 - 1/80 = 0.9875 \Rightarrow (1-\sigma)R = 133 \Omega \quad \& \quad \sigma R = 10478 \Omega$$

- b) Just plug in the value in the above circuit
- c) To get to scaled transfer function:  
 $K_f = \omega_o'/\omega_o = 2000\pi / 1 = 2000\pi \rightarrow \omega_o = \omega_o'/2000\pi$

$$\beta = \frac{4(1-\sigma)}{RC}, = \frac{4(1-0.9875)}{1/2000\pi} = 100\pi$$

$$H(s) = \frac{(s/2000\pi)^2 + 1}{(s/2000\pi)^2 + 100\pi(s/2000\pi) + 1} = \frac{s^2 + 4 \times 10^6 \pi^2}{s^2 + 2 \times 10^5 \pi^2 s + 4 \times 10^6 \pi^2}$$


7U. Using the following circuit:

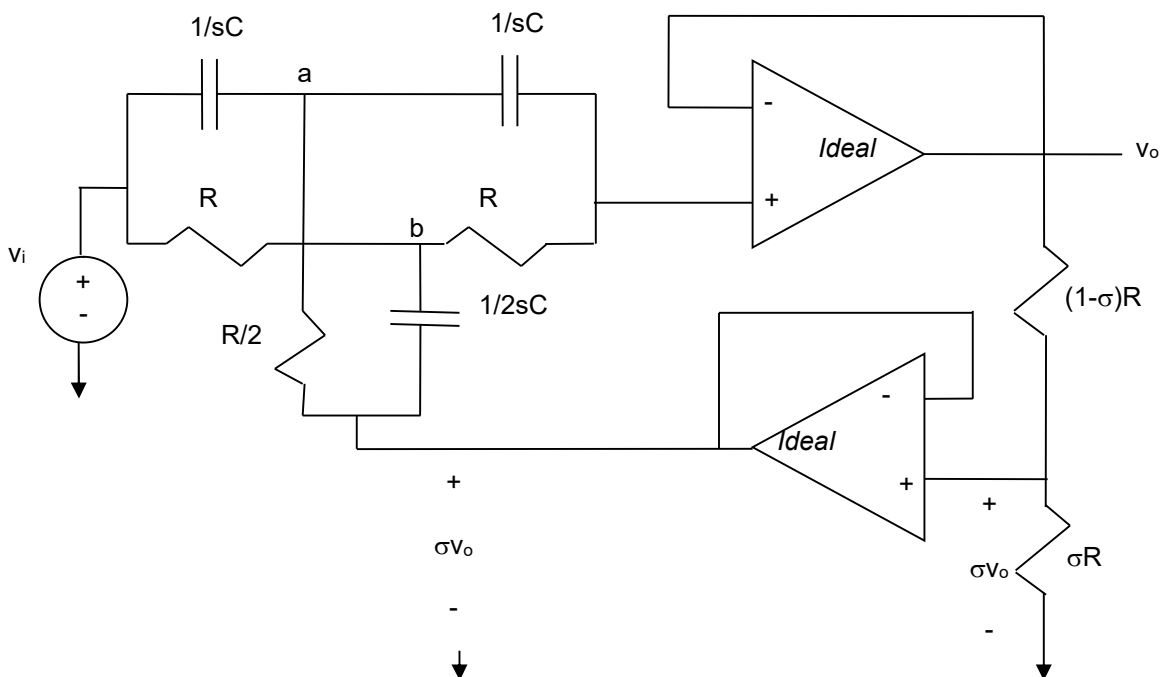

**Given:**  $H(s) = \frac{s^2 + \omega_o'^2}{s^2 + \beta s + \omega_o^2}$  where  $\omega_o'^2 = \frac{1}{R^2 C^2}$ ,  $\beta = \frac{4(1-\sigma)}{RC}$ ,  $\sigma = 1 - \frac{1}{4Q}$

- a) design a narrow-band bandreject filter having a center frequency of 5 kHz and a quality factor of 20. Use only C=10 nF in your design.
- b) Draw the circuit diagram of the filter and label all component values on the diagram.
- c) What is the scaled transfer function of the filter?

8S. Using the following circuit

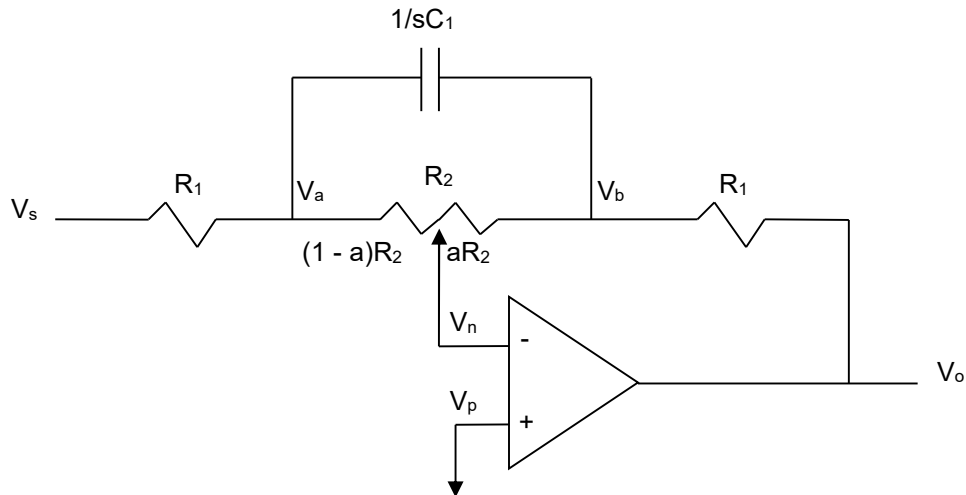

design a volume control circuit to give a maximum gain of 20 dB and a gain of 17 dB at a frequency of 40 Hz. Use an 11.1 kΩ resistor and a 100 kΩ potentiometer. Test your design by calculating the maximum gain at  $\omega=0$  and the gain at  $\omega=1/R_2C_1$  using the selected values of  $R_1$ ,  $R_2$ , and  $C_1$ .

$$\text{Given: } H(s) = \frac{V_o}{V_s} = \frac{-(R_1 + \alpha R_2 + R_1 R_2 C_1 s)}{R_1 + (1 - \alpha) R_2 + R_1 R_2 C_1 s}, \quad \omega_c = 1/\alpha R_2 C_1 \quad \text{"Low Pass Filter"}$$

Note: to derive the above transfer function, write KCL for nodes  $V_n$ ,  $V_a$  and  $V_b$  (Assume Ideal Op Amp)

### Solution:

for a low pass filter at  $\omega = 0$  we have Maximum gain and also  $\alpha = 1$  we get a gain of 20 dB  $\rightarrow$

$$|H(j\omega)|_{\max} = \frac{R_1 + R_2}{R_1}$$

$$20 \log\left(\frac{R_1 + R_2}{R_1}\right) = 20 \text{ dB} \Rightarrow \frac{R_1 + R_2}{R_1} = 10 \Rightarrow R_2 = 9R_1$$

Picking  $R_1 = 11.1 \text{ k}\Omega \rightarrow R_2 = 99.9 \text{ k}\Omega$

note that 17 dB is 3 dB lower than max which means 40 hz is the cut off frequency therefore  $\omega_c = 1/R_2 C_1 \rightarrow C_1 = 1/((100 \times 10^3)(80\pi)) = 39.79 \text{ nF}$

Testing Phase


Using the standard parts and given values  $\rightarrow C = 39 \text{ nF}$  and  $R_1 = 11.1$  and  $R_2 = 100 \text{ K}$

$$\text{at max } (\omega=0, \alpha=1) \rightarrow 20 \log |H(j\omega)|_{\max} = 20 \log\left(\frac{11.1+100}{11.1}\right) = 20.01 \text{ dB}$$

$\omega = 1/R_2 C_1 = 1/(10^5 \times 39 \times 10^{-9}) = 256.41 \text{ rad/s}$  &  $\alpha = 1$

$$20 \log |H(j256.41)| = 20 \log \left| \frac{-(R_1 + \alpha R_2 + R_1 R_2 C_1 j 256.41)}{R_1 + (1 - \alpha) R_2 + R_1 R_2 C_1 j 256.41} \right| = 20 \log(7.11) = 17.04 \text{ dB}$$

8U. Using the following circuit

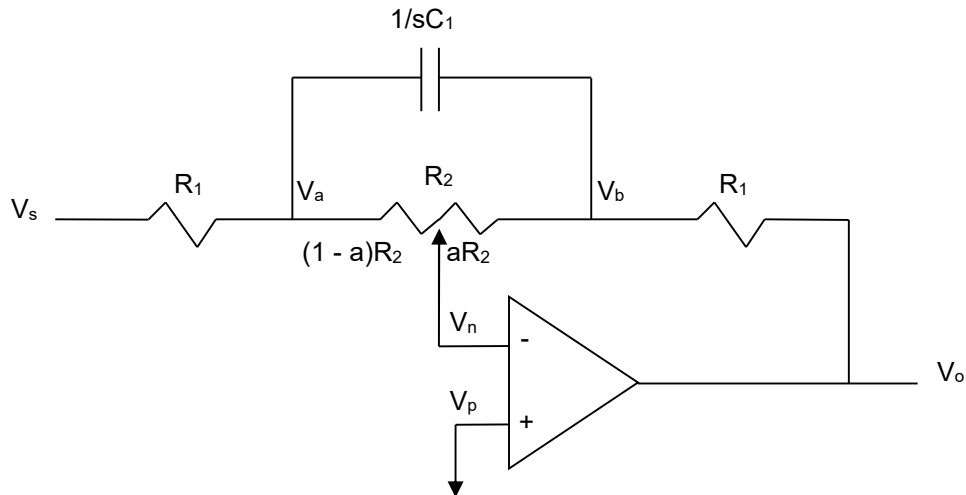


design a bass volume control circuit that has a maximum gain of 13.98 dB that drops off 3 dB at 50 Hz.

$$\text{Given: } H(s) = \frac{V_o}{V_s} = \frac{-(R_1 + \alpha R_2 + R_1 R_2 C_1 s)}{R_1 + (1 - \alpha) R_2 + R_1 R_2 C_1 s}, \quad \omega_c = 1/R_2 C_1 \quad \text{"Low Pass Filter"}$$

Note: to derive the above transfer function, write KCL for nodes V<sub>n</sub>, V<sub>a</sub> and V<sub>b</sub> (Assume Ideal Op Amp)

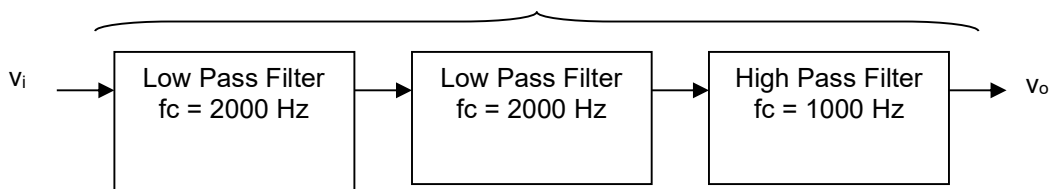**Solution:**

9S. What are the filter type and cut off frequencies ( $\omega_{c1}$  &  $\omega_{c2}$ ) of the system represented by the following block diagram? Explain your answers.




**Solution:**


$$n=2 \text{ stage low pass filter} \rightarrow \omega_{LCn} = \left( \sqrt[2]{\sqrt{2} - 1} \right) \omega_{c1} = \left( \sqrt[2]{\sqrt{2} - 1} \right) (2000)(2\pi) = 2574\pi$$

$$n=1 \text{ stage high pass filter} \rightarrow \omega_{Hc} = (1000)(2\pi) = 2000\pi$$

$$A_{dB} = 20 \log |H(s)|$$

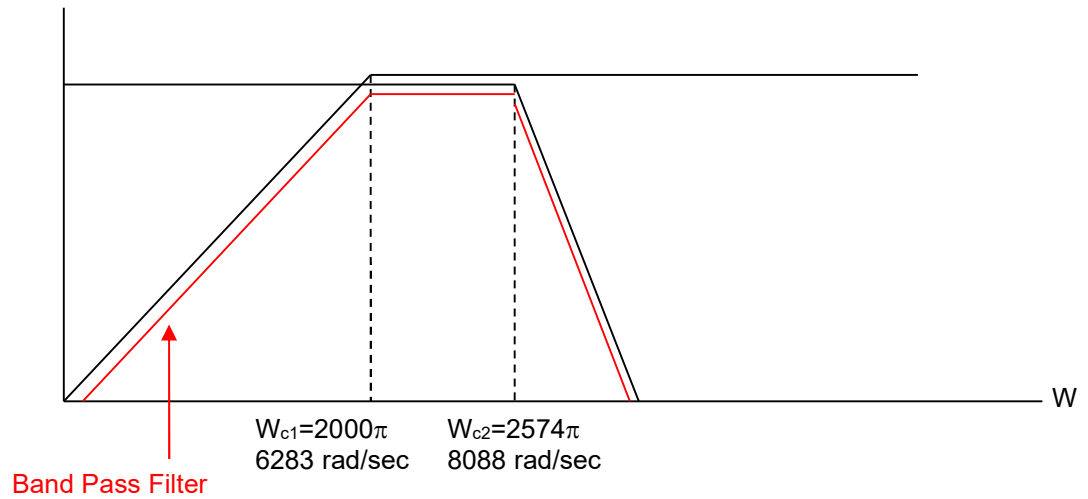

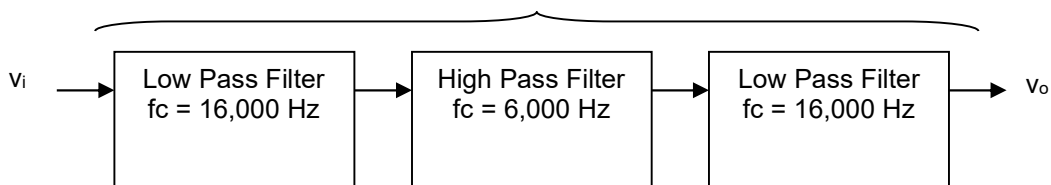9U. What are the filter type and cut off frequencies ( $w_{c1}$  &  $w_{c2}$ ) of the system represented by the following block diagram? Explain your answers.



**Solution:**